

Single Phase AC Systems i.e. Basic Terminology

- First power distribution system was a DC system → invented by Edison.
DC → not suitable for longer distances.
- AC → popular because of transformer.
- An AC waveform → periodic waveforms which alternates.
- Power system → very high voltage, less power loss
 - Generation
 - Transmission
 - Distribution } done as three phase AC power
- Basic terminology:
 - Periodic waveform → repeats after certain time interval.
 - Time period → taken time to complete one cycle (T)
 - Frequency → no. of cycle comp. in 1 sec.
 $(f) = 1/T$
- A pure AC waveform → +ve area matched by equal -ve area. Avg. value = 0.
- AC waveform with DC component!
DC component → constant amplitude

Sinusoidal wave can be expressed as function of angle or time.
Accd one cycle completes in $(2\pi)^c$ or T sec.

time (t)	angle (θ)
0	0
$T/4$	$\pi/2$
$T/2$	π
$3T/4$	$3\pi/2$
T	2π
1	$2\pi/T$
t	$(2\pi/T)t$

Mathematical representation: $E = E_m \sin(\omega t)$
 $e(t) = E_m \sin(\omega t \pm \phi)$ → If there exists phase difference
 $\omega = 2\pi$ or $2\pi f$

T

$$\theta = \omega t, \omega = \theta/t \text{ rad/s}$$

1. for sinusoidal function of frequency 50Hz,
find (i) Half time period (ii) angular frequency

Ans. (i)

$$T = \frac{1}{f}$$

$$T = \frac{1}{50}$$

$$T/2 = 1/100 = 0.01 \text{ sec}$$

$$2\pi f = 2 \times 3.14 \times 50 = 314 \text{ rad/s}$$

2. Max. value of sinusoidal AC of frequency 50Hz is 25A. Write eqn for Ims. Determine value at 3ms & 14ms.

Ans.:

$$I_{\max} = 25A$$

$$i(t) = I_{\max} \sin \omega t \rightarrow \text{Instantaneous eqn}$$

$$P(t=3\text{ms}) = 25 \sin(314 \times 3 \times 10^{-3})$$

$$= 25 \sin(54^\circ)$$

$$= 20.225 \text{ A}$$

$$P(t=14\text{ms}) = 25 \sin(314 \times 14 \times 10^{-3})$$

$$= -23.77 \text{ A}$$

→ Avg. value of sinusoidal function :

Avg. value of AC waveform $f(t)$ of given

$$f_{avg} = \frac{1}{T} \int_0^T f(t) dt$$

$$f_{avg} = \frac{1}{T} \int_0^T A \sin \omega t dt$$

$$f_{avg} = \frac{A}{T} \left[\frac{-\cos \omega t}{\omega} \right]_0^T$$

$$f_{avg.} = \frac{A}{\omega T} [-\cos \omega t]_0^T$$

$$f_{avg.} = \frac{A}{\omega T} [1 - \cos \omega T]$$

$$f_{avg.} = \frac{A}{2\pi} \left[1 - \frac{\cos 2\pi}{2} \right] \quad \begin{array}{l} \omega = 2\pi \\ \cos 2\pi = 1 \end{array}$$


$$f_{avg.} = 0$$

NOTE: Net area during one period = 0; $\therefore f_{avg} = 0$.

→ Effective/RMS value of AC function :

$E_{AC} \rightarrow$ Energy consumed by resistor
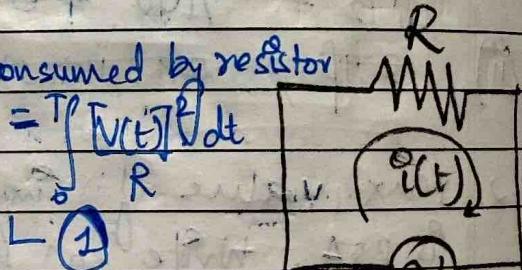
$$E_{AC} = \int_0^T P(t) dt = \int_0^T \frac{V(t)^2}{R} dt$$



For DC source,

$$E_{DC} = \frac{V^2 \cdot T}{R} \quad (\text{time doesn't vary}) \quad t=0; t=T$$

L ②

(power \times time \Rightarrow energy)

$$E_{AC} = E_{DC} \quad [\text{Power developed by AC & DC source is considered same}]$$

from (1) & (2),

$$\frac{T}{R} \int [V(t)]^2 dt = \frac{V^2 \cdot T}{R}$$

$$\Rightarrow V_{rms} = \sqrt{\frac{1}{T} \int [V(t)]^2 dt} \quad (3)$$

→ Effective/RMS value of sine wave:

Consider sinusoidal voltage $V(t) = V_m \sin(\omega t)$

Sub. (4) in (3),

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T (V_m \sin \omega t)^2 dt}$$

$$V_{rms} = \sqrt{\frac{V_m^2 T}{T} \int_0^T \sin^2(\omega t) dt}$$

$$V_{rms} = \sqrt{\frac{V_m^2 T}{T} \int_0^T (1 - \cos 2\omega t) \frac{dt}{2}}$$

$$V_{rms} = \sqrt{\frac{V_m^2 T}{2T} \int_0^T 1 - \cos 2\omega t dt}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{2T} \left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^T}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{2T} \left[(T - 0) - \frac{\sin 2\pi x T}{2\pi} - 0 \right]}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{2T} [(T - 0) - 0 - 0]} \quad [\omega = 2\pi/T] \quad [\sin(4\pi) = 0]$$

$$V_{rms} = \sqrt{\frac{V_m^2 \times T}{2T}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

→ Phase Lag & Phase lead :

$$f_1(\theta) = A \sin(\omega t) \rightarrow \text{reference wave}$$

$$f_2(\theta) = A \sin(\omega t - \pi/4) \rightarrow \text{Lag reference wave by } \pi/4$$

$$f_3(\theta) = A \sin(\omega t + \pi/4) \rightarrow \text{Lead reference wave by } \pi/4.$$

$f_2(\theta)$ lags $f_3(\theta)$ by $\pi/2$.

Q - Write an eqn to represent the following sine waves of 50 Hz frequency. (i) Sinusoidal current with RMS value 10A & starting at 5ms.

(ii) Sinusoidal current with peak value 20A & starting at -2.5 ms. Also, comment on the phase relation b/w them.

Ans:

Given: $f = 50\text{Hz}$

Angle 1: $\phi = \omega t_1 = 2\pi f t_1 = 2 \times 3.14 \times 50 \times 5 \times 10^{-3} = \frac{\pi}{2}$

~~Angle 1~~ $i_1(t) = I_m \sin(\omega t + \phi)$

$$i_1(t) = 10 \times 1.414 \times \sin(100\pi t - \pi/2)$$

$$i_1(t) = 14.14 \sin(100\pi t - \pi/2) \text{ A}$$

Angle 2: $\phi_2 = \omega t_2 = 2\pi f t_2 = 2\pi \times 50 \times -2.5 \times 10^{-3} = -\pi/4$


$$i_2(t) = \cancel{I_m} \sin(100\pi t + \pi/4)$$

$$i_2(t) = \cancel{20} \sin(100\pi t + \pi/4)$$

i_2 leading i_1 by $3\pi/4$ [$I_m = \text{peak}$]

→ Concept of Phasor:

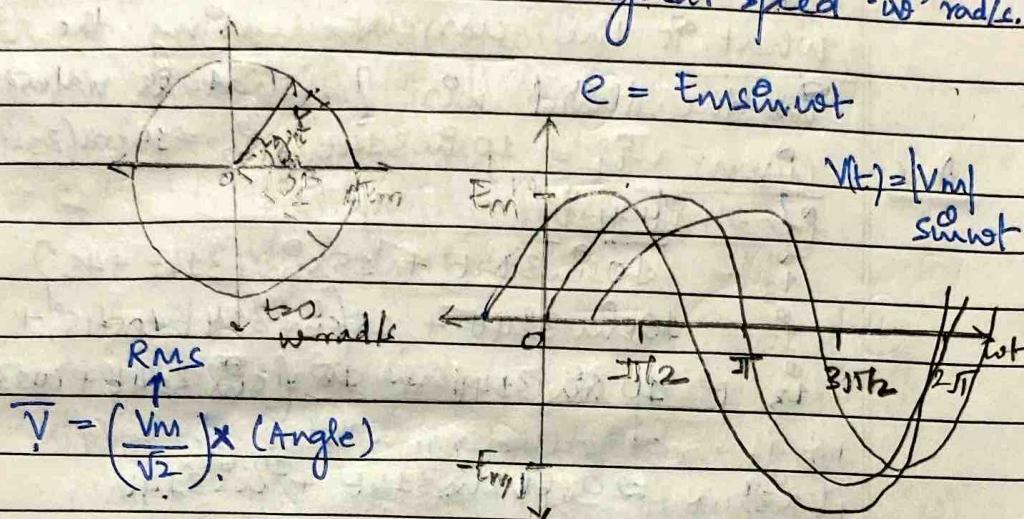Let us consider a rotating crank length E_m lying at 0° position at $t=0$ & rotating anti-clockwise at an angular speed ' ω ' rad/s.




Q- Represent in phasor diagram.

$$(a) f_1(t) = 100 \sin(100\pi t) \rightarrow F_1 = 100/\sqrt{2} \times 10^\circ$$

$$f_2(t) = 200 \sin(200\pi t + 60) \rightarrow F_2 = 200/\sqrt{2} \times 120^\circ$$
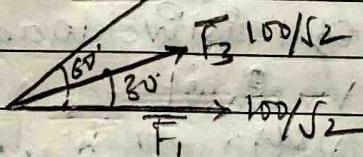
$$f_3(t) = 100 \cos(-100\pi t - 60) \rightarrow F_3 = 100/\sqrt{2} \times 30^\circ$$



→ Complex no. → $A + jB \rightarrow$ rectangular
 $r \angle \theta \rightarrow$ polar form

$$r = \sqrt{A^2 + B^2}, \theta = \tan^{-1}(B/A)$$

$$A = r \cos \theta, B = r \sin \theta$$

- Addition and subtraction of phasors → rectangular form
- Multiplication of phasors → $r_1 \times r_2 \angle \theta_1 + \theta_2$
- Division of phasors → $r_1/r_2 \angle \theta_1 - \theta_2$

- Q- There are three conducting wires connected to form a junction. The currents flowing into the junction in two wires are $i_1 = 10 \sin 314t$ A & $i_2 = 15 \cos(314t - 45^\circ)$ A. What is the current leaving the junction in the third wire? What is its value at $t=0$?

Ans:

Given: $i_1 = 10 \sin 314t$, $i_2 = 15 \cos(314t - 45^\circ)$

$$\begin{aligned} i_3 &= i_1 + i_2 \\ i_3 &= 10 \sin 314t + 15 \sin(314t + 45^\circ) \\ i_3 &= 10 \sin 314t + 15 \left(\sin 314t \cos 45^\circ + \cos 314t \sin 45^\circ \right) \\ i_3 &= 10 \sin 314t + \frac{15}{\sqrt{2}} (\sin 314t + \cos 314t) \\ i_3 &= 20 \cdot 6 \times \sin 314t + \frac{10 \cdot 6}{\sqrt{2}} \cos 314t \end{aligned}$$

OR:

$$i_1 = 10 / \sqrt{2} \angle 0^\circ, \quad i_2 = 15 / \sqrt{2} \angle 45^\circ$$

$$i_3 = i_1 + i_2$$

$$i_3 = 16.3879 \angle -27.2357^\circ$$


→ Response of resistive load to sinusoidal supply

$$V(t) = V_m \sin \omega t$$

$$i(t) = \frac{V(t)}{R}$$

$$i(t) = \frac{V_m \sin \omega t}{R}$$

$$i(t) = \frac{V_m}{R} \sin \omega t$$

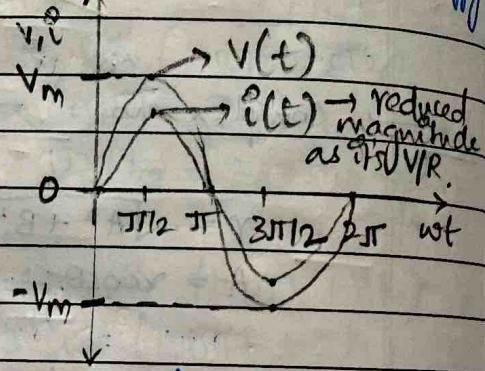

Phase angle difference (ϕ) for pure resistive circuit: $\phi = 0^\circ$

Phasor: $\vec{V} = \frac{V_m}{\sqrt{2}} \angle 0^\circ$; $\vec{i} = \frac{I_m}{\sqrt{2}} \angle 0^\circ$

Impedance $Z = \frac{\vec{V}}{\vec{i}} = \frac{V_m / \sqrt{2} \angle 0^\circ}{I_m / \sqrt{2} \angle 0^\circ} = R$

Phasor diagram: Always in phase in pure R circuit.

$$\vec{i} = I_m / \sqrt{2} \quad \vec{V} = V_m / \sqrt{2}$$

→ Inductor & concept of inductance:

Inductor → Obtained by winding the conductor into a coil.

A current carrying coil with magnetic field around it. Expressed in flux (Φ).

$$\Phi = \frac{\text{Magnetomotive Force}}{\text{Reluctance}} = \frac{N \cdot I}{S} \text{ wb}$$

$$S = \frac{l}{NA}$$

μ = permeability

$\Phi_{\text{mag.}} \propto i$ in inductor coil

$N\Phi \propto i$, where $N\Phi$ → flux linkages (λ)

$$\lambda = Li$$

↳ Inductance of the coil

$$\Rightarrow L = \frac{\lambda}{i} \quad \text{or} \quad L = \frac{N\Phi}{i}$$

L is measured in Henry's (H).

Voltage across terminals of inductor \propto rate of change of flux linkages.

$$V(t) \propto \frac{d(\lambda)}{dt}$$

$$V(t) = \frac{L \frac{d\Phi}{dt}}{dt}$$

$$\lambda(t) = \frac{1}{L} \int V(t) dt$$

$$\lambda(t) = \frac{1}{L} \int V_{\text{rms}} \sin \omega t dt$$

$$I(t) = \frac{V_m}{L} \left[-\frac{\cos \omega t}{\omega} \right]$$

$$I(t) = \frac{V_m}{\omega L} [-\cos \omega t] = \frac{V_m}{\omega L} [\sin(\omega t - \pi/2)]$$

$$i(t) = \frac{V_m}{X_L} \sin(\omega t - \pi/2)$$


$$q(t) = I_m \sin(\omega t - \pi/2) \quad (\because X_L = \omega L)$$

Inductive reactance

Phasor

$$\bar{V} = \frac{V_m}{\sqrt{2}} [0^\circ]$$
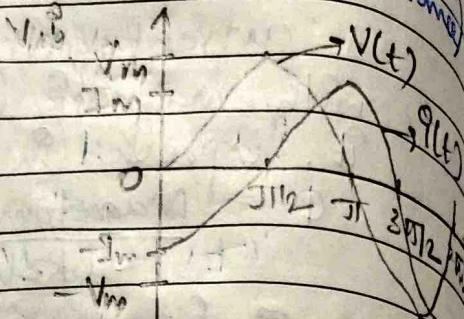
$$\bar{I} = \frac{I_m}{\sqrt{2}} [-90^\circ]$$




In pure inductive circuit, current lags voltage by angle $\pi/2(90^\circ)$.

$$\text{Impedance} \rightarrow Z = \frac{\bar{V}}{\bar{I}} = \frac{V_m / \sqrt{2}}{I_m / \sqrt{2}} = \frac{V_m}{I_m} [0^\circ] = X_L [0^\circ]$$

$$Z = X_L [90^\circ] \quad \text{or} \quad Z = jX_L$$

Phasor diagram:

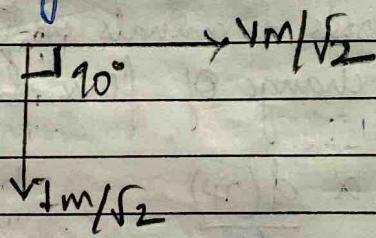

→ Capacitor & concept of Capacitance:

Capacitor → obtained by placing dielectric medium b/w conducting plates.

$$C = \frac{A\epsilon_0}{d} \text{ Farad}$$

$A \rightarrow$ Area of plates (m^2)

$d \rightarrow$ distance b/w plates (m)

$\epsilon_0 \rightarrow$ permittivity of dielectric medium (F/N)

The charge on the plates of capacitor & its voltage across its terminals.

$$q(t) \propto V(t)$$

$$q(t) = C \cdot v(t) - ①$$

$$\dot{q}(t) = \frac{d(q(t))}{dt}$$

$$\dot{q}(t) = \frac{d(Cv(t))}{dt}$$

$$q(t) = C \frac{d(V(t))}{dt}$$

$$q(t) = C \frac{d(V_m \sin(\omega t))}{dt}$$

$$q(t) = C V_m \omega \cos(\omega t)$$

$$q(t) = \frac{V_m}{(1/\omega C)} \sin(\omega t + \pi/2)$$

$$q(t) = \frac{V_m}{X_C} \sin(\omega t + \pi/2)$$

$$q(t) = I_m \sin(\omega t + \pi/2)$$


$\therefore X_C = \frac{1}{\text{capacitive } \omega C}$
 $\because I_m = V_m/X_C$ [reactance]

Phasor

$$\bar{V} = \frac{V_m}{\sqrt{2}} 10^\circ$$

$$\bar{I} = \frac{I_m}{\sqrt{2}} 90^\circ$$

Phasor diagram:

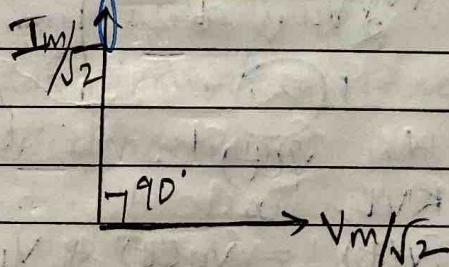

$$Z = \frac{\bar{V}}{\bar{I}} = \frac{V_m/\sqrt{2} 10^\circ}{I_m/\sqrt{2} 90^\circ} = X_C (0^\circ - 90^\circ)$$

$$Z = X_C / -90^\circ \quad \text{or} \quad Z = -j X_C$$

In pure capacitive circuit, current leads voltage by $\pi/2$

Q- A capacitor of capacitance 100 nF is connected across an AC voltage source $100 \sin(100\pi t)\text{ V}$. Determine:

(i) Capacitive reactance

(ii) Impedance

(iii) Instantaneous expression of current.

Ans: (i) $X_C = \frac{1}{\omega C}$

$$X_C = \frac{10^4 / 2}{100\pi} = 100/\pi$$

$$X_C = 31.84 \Omega$$

(ii) $Z = -jX_C = -j \cdot 31.84 \Omega$

(iii) ~~$I(t) = I_m \sin(\omega t + \pi/2)$~~

$$I(t) = \frac{V_m}{X_C} \sin(\omega t + \pi/2)$$

$$I(t) = \frac{100 \sin(100t + \pi/2)}{31.84}$$


$$I(t) = 3.14 \sin(100t + \pi/2)$$

Phasor Diagram :-

$$\bar{I} = \frac{3.14}{\sqrt{2}} \angle 10^\circ$$

$$\bar{V} = 100/\sqrt{2} \angle 10^\circ$$

→ Series R-L Circuit,

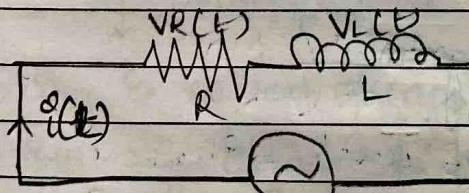

Apply KVL,

$$V(t) = V_R(t) + V_L(t)$$

$$\bar{V} = \bar{V}_R + \bar{V}_L$$

$$\bar{V}_R = \bar{I} R$$

$$\bar{V}_L = \bar{I}(jX_L)$$

$$\bar{V} = \bar{I}(R + jX_L)$$


$$Z = \frac{\bar{V}}{\bar{I}} = (R + jX_L)$$

$$|\bar{Z}| = \sqrt{R^2 + X_L^2}$$

$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$


In series circuit, Impedance angle = Phase angle.

Phasor diagram:

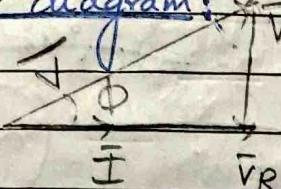

$$\phi = \tan^{-1} \left(\frac{V_L}{V_R} \right)$$

→ Series R-C circuit:

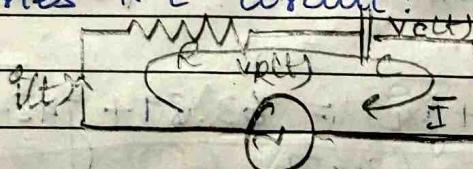

Apply KVL,

$$\bar{V}(t) = V_R(t) + V_C(t)$$

$$\bar{V} = \bar{V}_R + \bar{V}_C$$

$$\bar{V}_R = \bar{I}R$$

$$\bar{V}_C = \bar{I}(-jX_C)$$

$$\bar{V} = \bar{I}(R - jX_C)$$


$$\bar{Z} = \frac{\bar{V}}{\bar{I}} = (R - jX_C)$$

$$|\bar{Z}| = \sqrt{R^2 + X_C^2}$$

$$\phi = \tan^{-1} \left(\frac{X_C}{R} \right)$$

Impedance angle = Phase angle.

Phasor diagram:

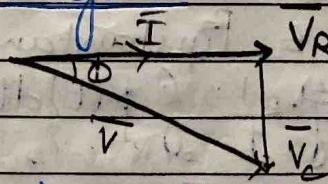

$$\phi = -\tan^{-1} \left(\frac{V_C}{V_R} \right)$$

-ve because voltage lagging behind current

Q - When a resistor & an inductor in series are connected to 240V, a current of 3A flows lagging 37° behind the supply voltage, while the voltage across inductor is 171V. Find resistance of resistor, the reactance & reactance of inductor. Find the power factor of the circuit.


Ans:

Given:

$$Z = \frac{V}{I}$$

$$Z = \frac{240}{3}$$

$$\frac{3}{1-37^\circ}$$

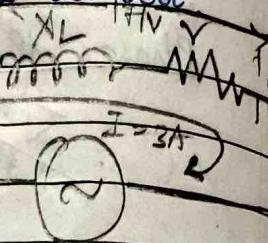

$$V = 240V$$

$$Z = 80 \angle 37^\circ$$

$$Z = (R + jY + jX_L) = 63.89 + j48.14$$

$$R + Y = 63.89$$

$$X_L = jX_L = \frac{V_{\text{inductor}}}{I_{\text{current}}} = \frac{171}{3} = 57$$

$$\sqrt{Y^2 + X_L^2} = 57$$

$$Y = \sqrt{57^2 + (48.14)^2}$$

$$Y = 30.52 \Omega$$

$$R + Y = 63.89 \Omega$$

$$R = 33.37 \Omega$$

Power factor : $\cos \phi = R/Z$
(series circuits)

$$\cos \phi = 63.89$$

80

$$\cos \phi = 0.798 \text{ (lagging)}$$

→ Power in AC Circuits:

(Case 1): $V(t) \cdot I(t) = P_{\text{instantaneous}}$

$$\text{Resistive load } P_{\text{avg}} = \frac{1}{T} \int_0^T p(t) dt$$

$$P_{\text{avg}} = \frac{1}{T} \int_0^T v(t) \cdot i(t) dt$$

$$P_{\text{avg}} = \frac{V_m I_m}{T} \int_0^T \sin^2 \omega t dt$$

$$V(t) = V_m \sin \omega t$$

$$i(t) = I_m \sin \omega t$$

$$P_{avg} = \frac{V_m I_m}{2} = V_{rms} I_{rms}$$

In resistive load, instantaneous power $p(t)$ is always +ve because, resistor consumes the power given to it by source.

Resistor dissipates power but doesn't generate.

Case 2: Pure Inductive load

$$v(t) = V_m \sin(\omega t), \quad \theta(t) = \theta_m \sin(\omega t - 90^\circ)$$

$$p(t) = v(t) \cdot \dot{\theta}(t)$$

$P_{avg} = 0$ here, as inductor can store energy

Case 3: Pure Capacitive load

$$v(t) = V_m \sin(\omega t), \quad \theta(t) = \theta_m \sin(\omega t + 90^\circ)$$

$$p(t) = v(t) \cdot \dot{\theta}(t)$$

$$P_{avg} = 0$$


$$Z = R + jX_L$$

$$\text{Active/Real power (P)} = VI \cos\phi (\text{watt})$$

$$\text{Reactive Power (Q)} = VI \sin\phi (\text{VAR})$$

$$\text{Apparent Power (S)} = \sqrt{P^2 + Q^2} (\text{kVA})$$

$$= VI (\text{VA | kVA | MVA})$$

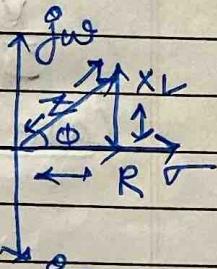

NOTE: Conventionally, Inductive reactive power $\rightarrow +ve$
Capacitive reactive power $\rightarrow -ve$.

$$\text{Power factor} = P/S = \cos\phi$$

$$\text{For series AC circuits, power factor} = \frac{R}{|Z|}$$

Q- Series RL circuit is connected to sinusoidal

voltage source $v(t) = 100 \sin(\omega t) \text{ V}$. It draws current of $10 \sin(\omega t - 60^\circ) \text{ A}$.

Determine: (i) Active, Reactive & Apparent power
(ii) Power factor of circuit

Ans: $V(t) = 100 \sin \omega t \text{ V}$

$I(t) = 10 \sin(\omega t - 60^\circ) \text{ A}$


$P = VI \cos \phi = 250 \text{ W}$

$Q = VI \sin \phi = 433.01 \text{ VAR}$

$S = VI = 500 \text{ VA}$

$\cos \phi = \frac{V}{I} = 0.5 \text{ (lag)}$

→ **LCR circuit:**

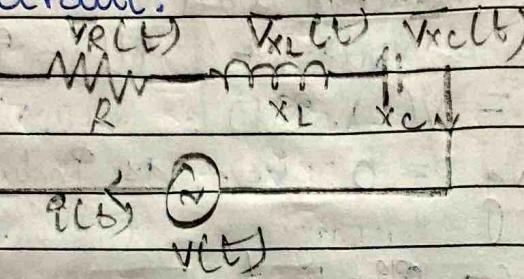

$$\bar{V} = V(t) = V_R(t) + V_{XL}(t) + V_{XC}(t)$$

$$\bar{I} = I(t) = \frac{V_R(t)}{R} + \frac{V_{XL}(t)}{jX_L} + \frac{V_{XC}(t)}{-jX_C}$$

$$Z = R + jX_L - jX_C$$

$$\frac{\bar{V}}{\bar{I}} = Z = R + j(X_L - X_C)$$

$$\text{or } Z = \sqrt{R^2 + (X_L - X_C)^2} / \tan(X_L - X_C / R)$$

Case 1: $X_L > X_C$ Phasor: $\bar{V}_L > \bar{V}_C$

$$|I_{XL}| > |I_{XC}|$$

$$\phi = \tan^{-1} \left(\frac{|V_L|}{|V_C|} \right)$$

Behaves like RL - Circuit

Case 2: $X_L < X_C$

$$|I_{XL}| < |I_{XC}|$$

$$\phi = \tan^{-1} \left(\frac{|V_L|}{|V_C|} \right)$$

$$\phi = \tan^{-1} \left(\frac{|V_L|}{|V_C|} \right) \text{ for negative } V_C$$

Behaves like RC - Circuit

Case 3: $X_L = X_C \rightarrow$ Series Resonance condition


$$|I_{XL}| = |I_{XC}|$$

$$V_L = V_C$$

Behaves like ~~pure~~ series/pure resistive circuit

Phasor:

$$\phi = 0^\circ$$

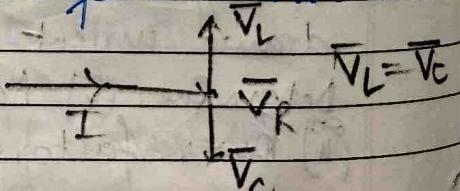

Q. Series RLC circuit draws current of 20A when connected to 200V, 50Hz supply. If total active power drawn from source is 500W & circuit behaves effectively like inductive circuit (series RL) determine: (i) Power factor, (ii) L if $C = 100 \times 10^{-9} F$

Ans: (i) $I = 20A$

$$\frac{V}{I} = 200V$$

$$f = 50\text{Hz}$$

$$S = \bar{V} \bar{I} = 4000\text{VA}$$

$$P = 500\text{W} \text{ (given)}$$

$$(i) \text{Power factor} = \frac{P}{S} = \frac{500}{4000} = 0.125 \text{ (by)}$$

$$(ii) |Z| = \frac{\bar{V}}{\bar{I}} = \frac{200}{20} = 10\Omega$$

$$P = I^2 R.$$

$$500 = 20 \times 20 \times R$$

$$R = 1.25\Omega$$

$$w = 2\pi f$$

$$w = 100\pi$$

$$X_C = \frac{1}{wC}$$

$$X_C = \frac{100}{100\pi} = 31.8\Omega$$

$$Z^2 = R^2 + (X_L - X_C)^2$$

$$\sqrt{Z^2 - R^2} = X_L - X_C$$

$$\sqrt{100 - (1.25)^2} + X_C = X_L$$

$$9.96 + 31.8 = X_L$$


$$X_L = 41.72\Omega$$

$$X_L = wL$$

$$L = \frac{41.72}{100\pi}$$

$$L = 132.86 \text{ mH}$$

→ RL & RC ||el Circuit:

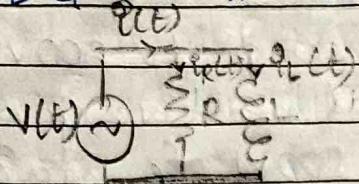

Parallel R-L circuit

Apply KCL,

$$\oint \Phi(t) = \Phi_R(t) + \Phi_L(t)$$

Phasor: $\bar{I} = \bar{I}_R + \bar{I}_L$

$$\frac{\bar{I}}{\bar{V}} = \frac{1}{R} + j\frac{1}{X_L}$$

$$\frac{\bar{I}}{\bar{V}} = \frac{1}{R} + j\frac{1}{X_L}$$

$$Y = 1/\bar{Z} = \bar{I}/\bar{V}$$

↓
Admittance (inverse of impedance)

$$G = 1/R$$

↓
conductance (inverse of resistance)

$$B_L = 1$$

$$\downarrow X_L$$

Inductive Susceptance (inverse of inductive reactance)

$$(Y) = G - jB_L$$

↓ unit: ohm⁻¹ or mho, siemens (S)

$$B_C = 1/X_C = W_C, \quad jB_C = j/X_C = jW_C$$

↓
Capacitive Susceptance



$$Y = G + jB_C$$

$$Y_{magnitude} = \sqrt{G^2 + B_C^2} / \tan^{-1}(-B_C/G)$$

In ||el circuit, total admittance Φ_C equals to the sum of individual branch admittances

Phasor diagram:
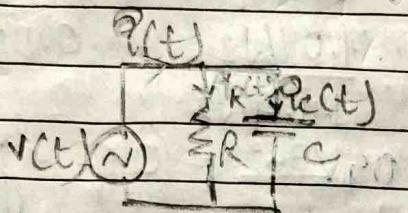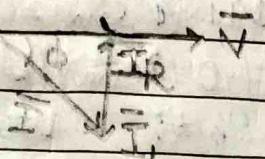
$$\phi = -\tan^{-1} \left(\frac{\bar{I}_L}{\bar{I}_R} \right)$$



Parallel R-C Circuit

Apply KCL,

$$Q(t) = Q_R(t) + Q_C(t)$$


Phasor: $\bar{I} = \bar{I}_R + \bar{I}_C$

$$\bar{I} = \frac{\bar{V}}{R} + \frac{\bar{V}}{jX_C}$$

$$\bar{Y} = G + jB_C$$

$$\text{Magnitude} = \sqrt{G^2 + B_C^2} / \tan^{-1}(B_C/G)$$

Phasor diagram:

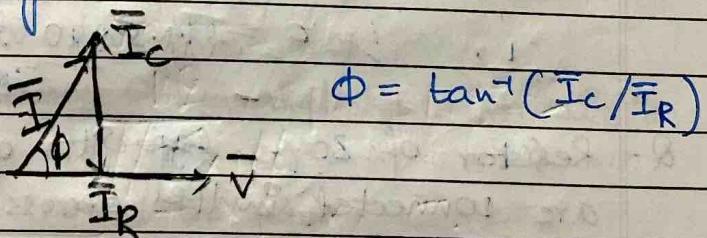

NOTE: Phase angle of network Q_C equal to Impedance angle or negative of admittance angle.

Q - Terminal voltage & current for Π net circuit are $141.4 \sin(2000t + \phi)$ & $7.07 \sin(2000t + 36^\circ)$. Obtain simplest two element Π net circuit which would have the above relationship.

Ans:

$$V(t) = 141.4 \sin 2000t \text{ V}$$

$$I(t) = 7.07 \sin(2000t + 36^\circ) \text{ A}$$

$$|Y| = \frac{|I|}{|V|} = \frac{7.07/\sqrt{2}}{141.4/\sqrt{2}} = 0.05 \text{ S}$$

$$Y_{\text{magnitude}} = 0.05 \angle 36^\circ = (0.04 + j0.029) \text{ S}$$

$$G = 0.04 \text{ S}$$

$$R = 25 \Omega \quad (V_A)$$

$$B_C = 0.029 \text{ S}$$

$$X_C = \frac{1}{0.029} \quad (1/B_C)$$

$$\frac{1}{w_C} = \frac{1}{0.029}$$

$$2 \times 3.14 \times C = 0.029$$

$$C = 14.5 \times 10^{-6} \text{ F}$$

Q - Resistor of 30Ω , capacitor of unknown value are connected in Π net across $110V, 50\text{Hz}$ supply combination draws current of 5A from the supply. Find unknown capacitance.

Ans:

$$\frac{1}{Y} = \frac{1}{|I|} / |V|$$

$$\frac{1}{Y} = \frac{1}{5} / \frac{110}{22}$$

$$Y = 0.045 \text{ S}$$

~~$$\frac{1}{Y} = \frac{1}{R} + \frac{1}{jw_C} \Rightarrow G = \frac{1}{R} = 0.0333 \text{ S}$$~~

$$B_C = \sqrt{Y^2 - G^2}$$


$$B_E = 0.0306 \text{ S.}$$

$$B_C = W_C$$

$$\frac{0.0306}{100\pi} = C$$

$$C = 97.38 \times 10^{-6} F$$

→ Analysis of 1st R-L-C circuit:

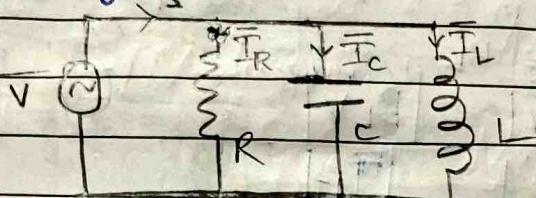

Apply KCL,

$$\bar{I} = \bar{I}_R + \bar{I}_L + \bar{I}_C \quad \dots \quad (1)$$

$$\bar{I}(t) = \bar{Q}_R(t) + \bar{Q}_L(t) + \bar{Q}_C(t)$$

$$\bar{I}_R = \bar{V}/R = \bar{V}G$$

$$\bar{I}_L = \bar{V}/jX_L = \bar{V}(-jBL) \quad \Rightarrow \quad (2)$$

$$\bar{I}_C = \bar{V}/jX_C = \bar{V}(jBC)$$

$$(2) \text{ in } (1) \Rightarrow \bar{I} = \bar{V}G + \bar{V}(-jBL) + \bar{V}(jBC)$$

$$\bar{I} = \bar{V}(G - jBL + jBC)$$

$$\bar{Y} = \frac{\bar{I}}{\bar{V}} = G + j(B_C - B_L)$$

Admittance of parallel RLC circuit is:

$$|Y| = \sqrt{G^2 + (B_C - B_L)^2}$$


$$\phi = \tan^{-1} \left(\frac{B_C - B_L}{G} \right)$$

Case 1: $B_C < B_L$

$$|B_C \bar{V}| < |B_L \bar{V}|$$

$$|\bar{I}_C| < |\bar{I}_L|$$

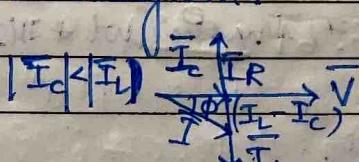Circuit effectively behaves as 1st RL circuit
Phasor diagram:



$$\phi = \tan^{-1} \left(\frac{\bar{I}_C - \bar{I}_L}{\bar{I}_R} \right)$$


as phi should be negative from diagram

Case 2: $B_C > B_L$

$$|B_C \bar{V}| > |B_L \bar{V}|$$

$$|\bar{I}_C| > |\bar{I}_L|$$

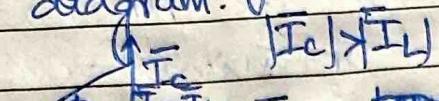Circuit effectively behaves as \uparrow RC circuit
Phasor diagram:



$$\tan \phi = \frac{|I_C|}{|I_L|}$$

$\phi \rightarrow +ve$ from diagram


Case 3: $B_C = B_L$

$$|B_C \bar{V}| = |B_L \bar{V}|$$


$$|\bar{I}_C| = |\bar{I}_L|$$

Circuit effectively behaves as pure resistive circuit. (Parallel resonance condition)

Phasor diagram:

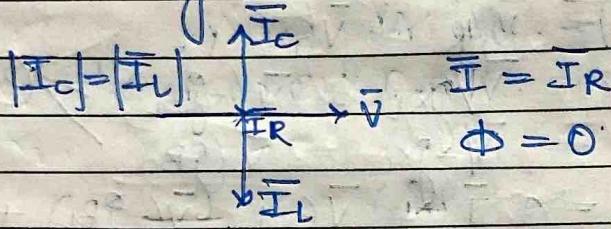

→ Power:

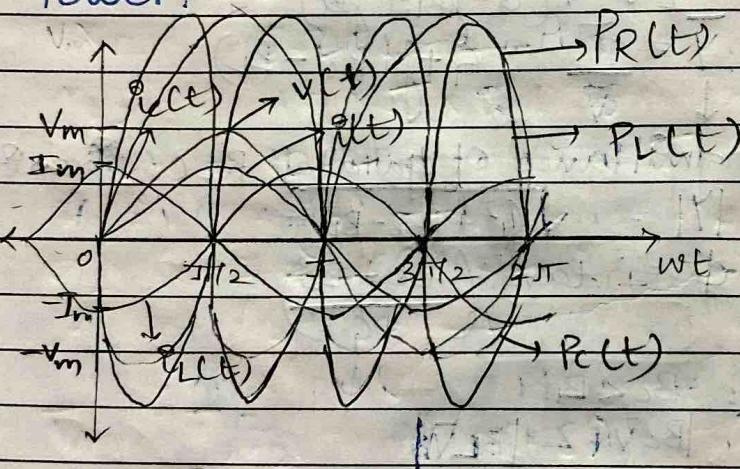

$$V(t) = V_m \sin \omega t$$

$$Q_L(t) = I_m \sin \omega t$$

$$P_L(t) = I_m^2 R \sin^2(\omega t - \pi/2)$$

$$Q_C(t) = I_m^2 L (\sin \omega t + \pi/2)$$

Q- Three circuit elements $R = 2.5 \Omega$, $X_L = 4 \Omega$, $X_C = 10 \Omega$ are connected in parallel, reactances = 50 Hz.

(a) Determine admittance of each element & obtain input admittance.

(b) If circuit is connected across 10V, 50Hz AC source, determine the current in each branch & total output input current.

Ans: (Given: $R = 2.5 \Omega$, $X_L = 4 \Omega$, $X_C = 10 \Omega$.)

$$(a) G = 1/R = 1/2.5 = 0.4 S$$

$$\frac{g}{j}B_L = \frac{1}{jX_L} = j\left(\frac{1}{4}\right) = -j(0.25) S$$

$$\frac{g}{j}B_C = \frac{1}{jX_C} = j\left(\frac{1}{10}\right) = j(0.1) S$$

Total admittance $Y = G + g(B_C - B_L)$

$$Y = [0.4 + g(0.1 - 0.25)] S$$

$$Y = [0.4 - g(0.15)] S$$

$$(b) \bar{I}_R = \bar{V}G$$

$$\bar{I}_L = \bar{V}(-jB_L)$$

$$\bar{I}_C = \bar{V}(jB_C)$$

$$\bar{I}_R = 10 \times \frac{1}{4} = 4 A$$

$$\bar{I}_L = 10 \times 0.25 \angle -90^\circ = 2.5 \angle -90^\circ A$$

$$\bar{I}_C = 10 \times 0.1 \angle 90^\circ = 1 \angle 90^\circ A$$

$$\bar{I} = \bar{I}_R + \bar{I}_L + \bar{I}_C$$

$$\bar{I} = \bar{V}(Y)$$

$$\bar{I} = 10 [0.4 - g(0.15)] A$$

$$\bar{I} = 4 - 1.5^\circ A$$


$$\bar{I} = 4.27 \angle -20.55^\circ A$$

→ Analysis of Series - Parallel Circuit:

Series - Parallel AC circuit → few elements connected in series & few in parallel.

Q - In the circuit shown, what voltage of 50 Hz frequency is to be applied across A & B that will cause current 10A to flow in the capacitor. Also, draw phasor diagram representing the circuit.

Ans:

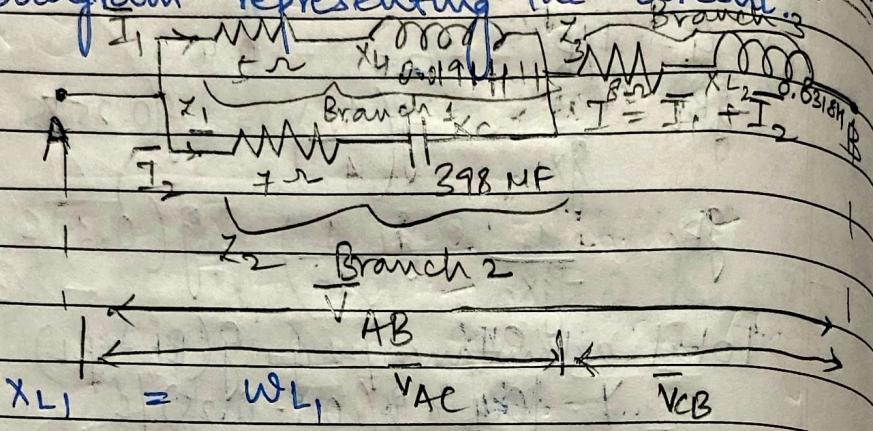

$$X_{L_1} = \omega L_1 \quad V_{AC} \quad V_{CB}$$

$$X_{L_1} = 100 \times \pi \times 0.0191$$

$$X_{L_1} = 6 \Omega$$

$$X_C = \frac{1}{\omega C}$$

$$X_C = 8 \Omega$$

$$X_{L_2} = 100 \times \pi \times 0.0218$$

$$X_{L_2} = 10 \Omega$$

$$Z_1 = (5 + j6) \Omega$$

$$Z_2 = (7 - 8j) \Omega$$

$$Z_3 = (8 + 10j) \Omega$$

$$V_{AC} = I_2 Z_2 = 10 (-8j)$$

$$\bar{V}_{AC} = 106.301 \angle -48.81^\circ V$$

$$I_1 = \frac{\bar{V}_{AC}}{Z_1} = \frac{106.301 \angle -48.81^\circ}{(5 + j6)}$$

$$I_1 = 13.61 \angle 99^\circ A$$

$$\text{Total current } I = I_1 + I_2$$


$$I = (13.61 \angle 99^\circ + 10 \angle -8^\circ) A$$

$$\bar{V}_{CB} = \bar{I} Z_2 = 199.47 \angle -8.31^\circ V$$

Total voltage $\bar{V}_{AB} = \bar{V}_{AC} + \bar{V}_{CB}$

$$\begin{aligned}\bar{V}_{AB} &= (106.3 \angle -48.81^\circ) + (199.3 \angle -8.31^\circ) \\ \bar{V}_{AB} &= 288.68 \angle -22.15^\circ V\end{aligned}$$

Phasor diagram:

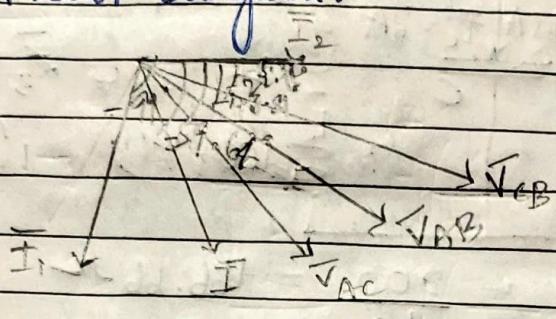

Q- When 220V AC supply is applied across terminals A & B of circuit shown, total power input is 3.25 kW, & total current 20A, lag. Find the complex expressions for current through Z_1 & Z_2 , taking V_{AC} as reference

Ans:

Given:

$$\bar{V}_{AB} = 220 \angle 0^\circ V$$

$$P = 3.25 \text{ kW}$$

$$\bar{I} = 20 \text{ A}$$

$$\cos \phi = \frac{P}{VI} = \frac{3.25 \times 10^3}{220 \times 20} = 0.738 \text{ (lag)}$$

$$\phi = -42.38^\circ$$

$$\bar{V}_{AB} = \bar{V}_{AC} + \bar{V}_{CB}$$

$$\bar{V}_{CB} = \bar{I} \times Z_2$$

$$\therefore \bar{V}_{CB} = 223.60 \angle 21^\circ V$$


$$\bar{V}_{AC} = \bar{V}_{AB} - \bar{V}_{CB} = 80.91 \angle -82^\circ V$$

$$\bar{I}_1 = \frac{\bar{V}_{AC}}{Z_1} = 3.92 \angle -15.7^\circ A$$

$$\bar{I}_2 = \bar{I} - \bar{I}_1 = 21.78 \angle -33.1^\circ A$$

Q- A voltage of 200V is applied to pure resistor, pure capacitor (C) & lossy inductor coil with resistance of 100Ω , all of them connected in parallel. Total current 2.45A, while component currents are 1.5A, 2A, ~~2~~ 1.2A respectively. Find total power factor & power factor of coil. Also find total active & reactive power.

Ans:

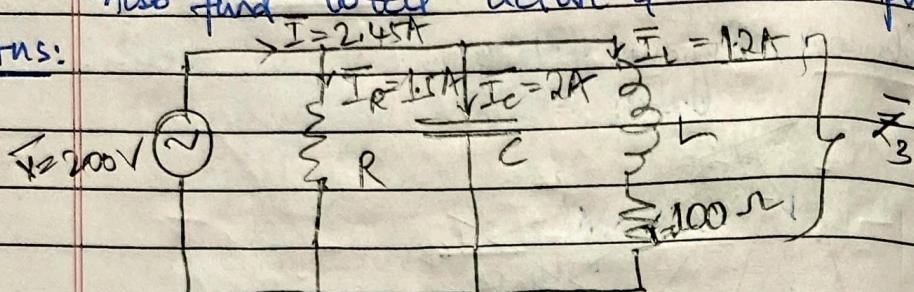

$$\bar{Z}_3 = \frac{\bar{V}}{\bar{I}_L} = \frac{200}{1.2} = 166.66 \Omega$$

$$\cos \phi_3 = \frac{V}{Z_3} = \frac{100}{166.66} = 0.6 \text{ (lag)}$$

$$\phi_3 = \cos^{-1}(0.6) \text{ (lag)}.$$

$$\phi_3 = -53.128^\circ$$

$$\bar{I} = \bar{I}_R + \bar{I}_C + \bar{I}_L$$

$$\bar{I} = 1.5 \angle 0^\circ + 2 \angle 90^\circ + 1.2 \angle -53.128^\circ$$

$$\bar{I} = 2.45 \angle 25.10^\circ \text{ A}$$


$$\text{Power factor: } \cos \phi = \cos(25.10^\circ) = 0.905$$

~~$\cos \phi = 0.905$~~ (Clear)

$$\text{Active power: } \bar{V} \bar{I} \cos \phi = 443.45 \text{ W}$$

$$\text{Reactive power: } \bar{V} \bar{I} \sin \phi = 207.85 \text{ VAR}$$

Q- Load connected across an AC supply consists of a heating load of 15kW, motor load of 40kVA at 0.6 lag & a load of 20kW at 0.8 lag. Calculate the total power drawn from the supply and its power factor. What would be the kVAR rating of a capacitor to bring power factor to unity & how must the capacitor be connected?

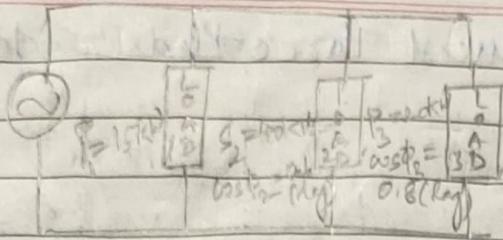Ans:

Load 1: $P_1 = 15 \text{ kW}$

$$\cos\phi_1 = 0$$

$$S_1 = 15 \text{ kVA}$$

Load 2: $S_2 = 40 \text{ kVA}$

$$\cos\phi_2 = 0.6$$

$$P_2/S_2 = \cos\phi_2$$

$$P_2 = 24 \text{ kW}$$

$$S_2 = \sqrt{P_2^2 + Q_2^2}$$

$$Q_2 = \sqrt{S_2^2 - P_2^2}$$

$$Q_2 = 32 \text{ kVAR}$$

Load 3: $P_3 = 20 \text{ kW}$

$$\cos\phi_3 = 0.8$$

$$S_3 = P_3/\cos\phi_3$$

$$S_3 = 25 \text{ kVA}$$

$$Q_3 = \sqrt{S_3^2 - P_3^2}$$

$$Q_3 = 15 \text{ kVAR}$$

$$P_T = P_1 + P_2 + P_3$$

$$P_T = (15 + 24 + 20) \text{ kW}$$

$$P_T = 59 \text{ kW}$$

$$Q_T = \cancel{(0 + 32 + 15)} \text{ kVAR}$$

$$Q_T = 47 \text{ kVAR}$$

~~$$S_T = (15 + 40 + 25) \text{ kVA}$$~~

~~$$S_T = 80 \text{ kVA}$$~~

$$S_T = \sqrt{P_T^2 + Q_T^2}$$

$$S_T = 75.432 \text{ kVA}$$

At $\cos\phi = 1$, $\phi = 0$, Power factor = 1.

Add capacitor Q_m in parallel to circuit