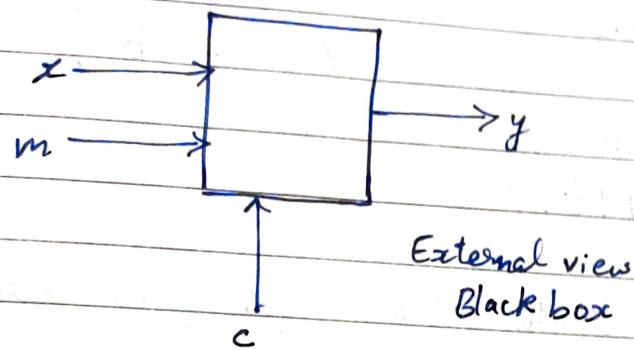



8th August, 2023

DDCO

e.g.: $y = mx + c$



e.g.:

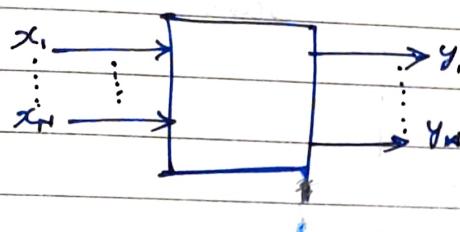


$$y = f(x)$$

SOP POS


Boolean Functions

$$y = a \cdot b$$

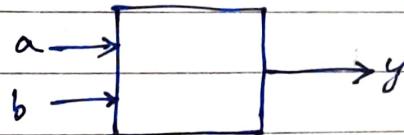

$$y = f(a, b)$$

T.T		y
a	b	
0	0	0
0	1	0
1	0	0
1	1	1

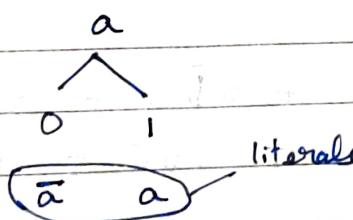

\bar{a}	\bar{b}	y
\bar{a}	b	0
\bar{a}	\bar{b}	0
a	\bar{b}	0
a	b	1

SOP \rightarrow check for 1 (min terms) $a \cdot b$

POS \rightarrow check for 0 (max terms)

$$y = \bar{a}\bar{b} + ab$$

$$y = m_2 + m_3$$

	a	b	y
0	\bar{a}	\bar{b}	0
1	\bar{a}	b	0
2	a	\bar{b}	1
3	a	b	1


$$\text{SOP } y = \sum m(2, 3)$$

$$\text{POS } y = T' M(0, 1)$$

q. Construct truth table for full adder


	2^2	2^1	2^0	2^2	2^1	Sum	carry
	A	B	C	a	b		C_{out}
C.in	0	0	0	0	0	0	0
0	0	0	0	0	1	1	0
1	0	0	1	0	0	1	0
2	0	1	0	1	0	1	0
3	0	0	1	0	1	0	1
4	0	1	1	0	0	1	0
5	1	0	0	0	1	0	1
6	1	0	1	1	0	0	1
7	1	1	1	1	1	1	1

External view

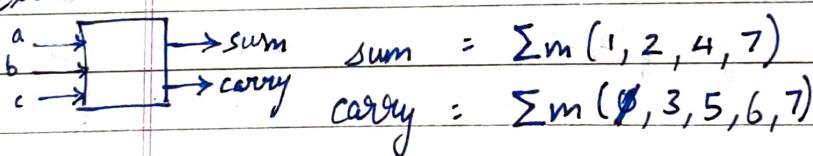

$$\text{sum} = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc$$
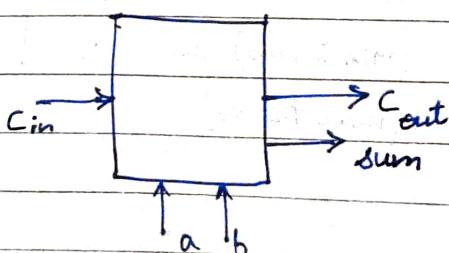
$$\text{carry} = \bar{a}bc + a\bar{b}c + ab\bar{c} + abc$$




$$S_i = a_i \oplus b_i \oplus C_{i-1}$$

PAS : Power Area Speed

a b c

Logic diagram (a) "Internal view"

$A \oplus Y$
and OR
Inverter

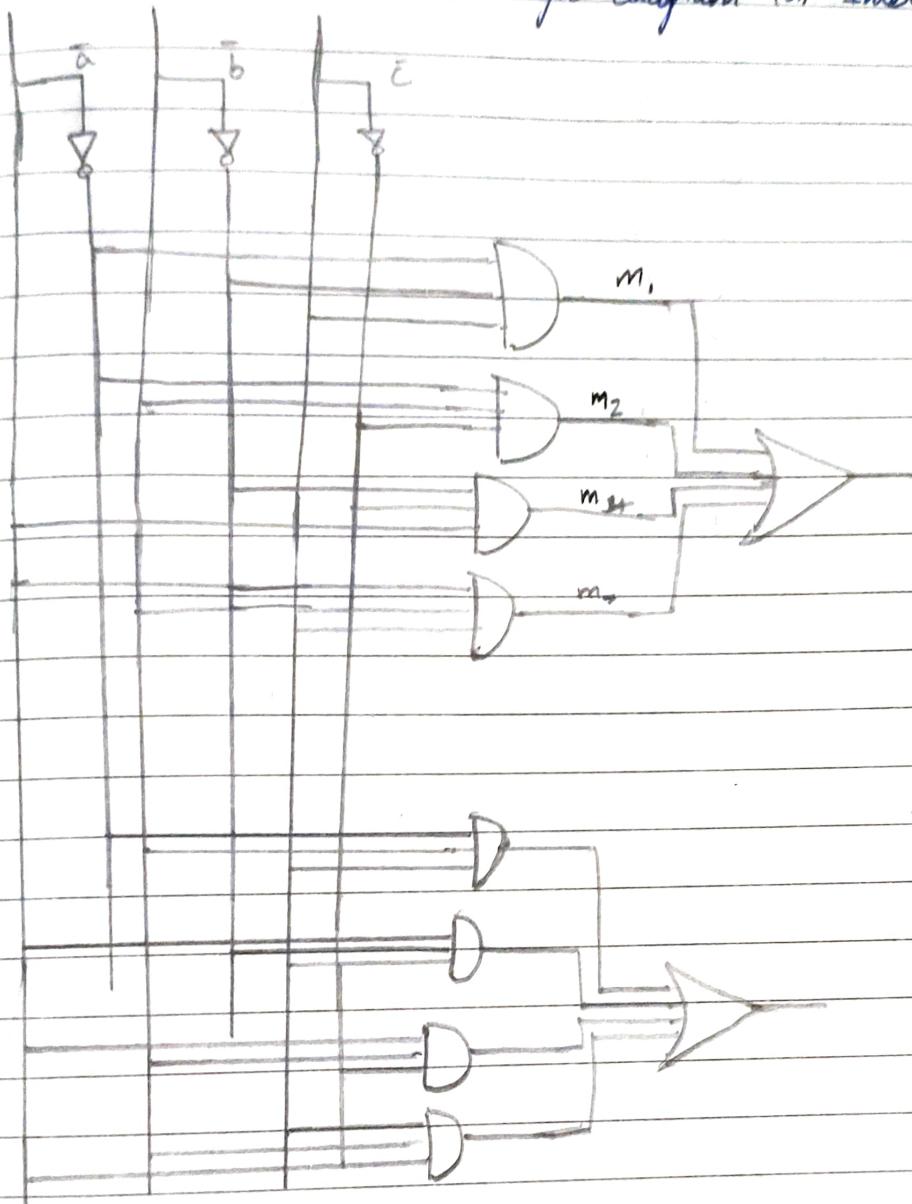

q: Construct internal view for full subtractor.

10th August, 2023

UNIT-1 Number System And Logic Gates

* I/P Binary

width $\rightarrow N$

no. of fast cases $\rightarrow 2^N$

range $\rightarrow 0$ to $2^N - 1$

* I/P Hexadecimal : N (no. of digits)
 10^N

0 to $10^N - 1$

scaling $\Rightarrow X \times 16^{\frac{N}{2}}$

left shift right shift

\rightarrow Binary Addition

$$0111_2 + 0101_2$$

$$\begin{array}{r} 0111 \\ + 0101 \\ \hline 1100 \end{array}$$

q) Implement $y_1 = a+b$; $y_2 = a-b$

i) $a=8$; $b=9$

ii) $a=5$; $b=15$

iii) $a=15$; $b=5$

11th August, 2023

Signed Numbers

4bit
Binary

N

2^N

0 to $2^N - 1$

4

16

0 → 15

0000 → 1111

8 4 2 1

2's complement

0 0000

10000

1 0001

1111

2 0010

1110

3 0011

1101

4 1000

1000

5 1001

1001

6 1010

1010

7 1011

1011

8 0100

0100

9 0101

0101

10 0110

0110

11 0111

0111

12 1100

1100

13 1101

1101

14 1110

1110

15 1111

1111

$$\begin{array}{r} 1111 \\ 1111 \\ + \quad 1 \\ \hline 10000 \end{array} \quad \begin{array}{r} 1110 \\ 1111 \\ + \quad 1 \\ \hline 1111 \end{array} \quad \begin{array}{r} 1101 \\ 1110 \\ + \quad 1 \\ \hline 1110 \end{array}$$

$$\begin{array}{r} 1100 \\ + \quad 1 \\ \hline 1101 \end{array} \quad \begin{array}{r} 0111 \\ + \quad 1 \\ \hline 1000 \end{array}$$

*Boat
Race*

2's complement range

$$\begin{array}{ll} -8 & \text{to} & +7 \\ -2^{N-1} & \text{to} & 2^{N-1} - 1 \end{array}$$

Sign / Magnitude

$$N = 4$$

$$2^N - 1 \quad (0 \text{ overlapping})$$

$$-7 \text{ to } +7$$

$$-2^{N-1} + 1 \text{ to } 2^{N-1} - 1$$

$$N = 5$$

	width	no. of possible test cases	range (min - max)
unsigned	5	32	0 - 31
2's	5	32	-16 to +15
sign	5	31	-15 to +15

q. Compute a) $5_{10} - 3_{10}$
b) $3_{10} - 5_{10}$ using 4 bit 2's complement

Sol. $5 + (-3)$

$$\begin{array}{r} 0101 \\ + 1101 \\ \hline 10010 \end{array} \quad \begin{array}{r} 0000 \\ + 1100 \\ \hline 1110 \end{array}$$

carry not related for subtraction

3 - 5

$S \rightarrow 0 \ 1 \ 0 \ 1$

$0 \ 0 \ 1 \ 1$

$$\begin{array}{r} + 1 \ 0 \ 1 \ 1 \\ \hline 1 \ 1 \ 1 \ 0 \end{array}$$

(14)

$$\begin{array}{r} 1 \ 0 \ 1 \ 0 \\ + 1 \ 1 \ 1 \\ \hline 1 \ 1 \ 0 \ 1 \ 1 \end{array}$$

$0 \ 0 \ 0 \ 1$

$$\begin{array}{r} + 1 \\ \hline 0 \ 0 \ 1 \ 0 \end{array}$$

q. $y_1 = a + b$ and $y_2 = a - b$

i) $a = 35$
 $b = 26$

ii) $a = -35$
 $b = 26$

i) $32 \ 16 \ 8 \ 4 \ 2 \ 1$
 $35 \rightarrow 1 \ 0 \ 0 \ 0 \ 1 \ 1$
 $26 \rightarrow 0 \ 1 \ 1 \ 0 \ 1 \ 0$

$$a + b = \cancel{1} \ 1 \ 0 \ 0 \ 1$$

$$1 \ 1 \ 1 \ 1 \ 0 \ 1$$

$$a - b = 35 + (-26)$$

$$\begin{array}{r} 1 \ 0 \ 0 \ 1 \ 0 \ 1 \\ + 1 \ 1 \ 1 \ 1 \ 0 \ 1 \\ \hline 1 \ 0 \ 0 \ 1 \ 1 \ 0 \end{array}$$

$$\begin{array}{r} 1 \ 0 \ 0 \ 0 \ 1 \ 1 \\ 1 \ 0 \ 0 \ 1 \ 1 \ 0 \\ \hline 1 \ 0 \ 0 \ 1 \ 0 \ 0 \ 1 \\ \hline \text{carry} \end{array}$$

17th August, 2023

Logical minimization : K-Map

$$\rightarrow y = f(a, b, c) \quad [\text{eg. of 3 variables}] \quad (8 \text{ test cases} = 8 \text{ cells})$$

a	b	c	min term (m)	max term (M)	Y
0	0	0	$\bar{a}\bar{b}\bar{c}$	$a+b+c$	0
1	0	0	$\bar{a}\bar{b}c$	$a+b+\bar{c}$	0
2	0	1	$\bar{a}b\bar{c}$	$a+\bar{b}+c$	0
3	0	1	$\bar{a}bc$	$a+\bar{b}+\bar{c}$	1
4	1	0	$a\bar{b}\bar{c}$	$\bar{a}+b+c$	1
5	1	0	$a\bar{b}c$	$\bar{a}+b+\bar{c}$	0
6	1	1	$ab\bar{c}$	$\bar{a}+\bar{b}+c$	1
7	1	1	abc	$\bar{a}+\bar{b}+\bar{c}$	1

$$Y = \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$

$$Y = m_3 + m_4 + m_6 + m_7$$

$$= \sum (m_3, m_4, m_6, m_7)$$

$$= \sum_m (3, 4, 6, 7)$$

Soln. @ source


Ans:

NOT : 3


AND : 4 \rightarrow (3 i/p)

OR : 1 \rightarrow (4 i/p)

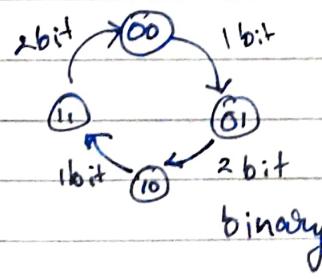only 1 bit difference in two consecutive no. = gray code
bit flipping



⑥

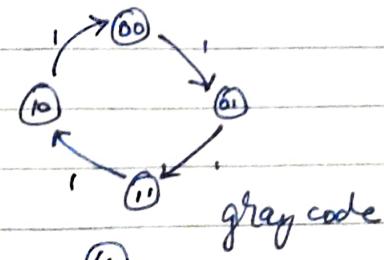

④

Bin	gray
(00)	0
(01)	1
(10)	2
(11)	3

a	00	01	11	10
0	$\bar{a}\bar{b}c$	$\bar{a}bc$	$\bar{a}bc$	$\bar{a}\bar{b}c$
1	$\bar{a}b\bar{c}$	$\bar{a}b^c$	abc	$a\bar{b}c$

$$\bar{a}bc + \bar{a}b^c + a^2 = bc$$

$$\bar{a}bc + b\bar{a}^2 + a^2 = bc$$

grouped	0	0	1	3	2
1, 5 can be grouped $\bar{a}b^c + a\bar{b}^c$	1	4	5	7	6

$$abc + ab\bar{c} = ab$$

grouping ① 1-cell

$\bar{a}bc, \bar{a}\bar{b}c, abc, ab\bar{c}$: Implicants (I)

② 2-cell $bc, ab, a\bar{c}$: prime Implicants (PI)
 $y = bc + ab + a\bar{c}$


③ $bc, a\bar{c}$ Essential Prime Implicants (EPI)
 $y = bc + a\bar{c}$ no overlapping

g	a	b	c	y
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

$$y = \bar{a}\bar{b}c + \bar{a}bc + a\bar{b}\bar{c} + a\bar{b}c + ab\bar{c} + abc$$

1 3 4 5 6 7

$$y = \sum_m(1, 3, 4, 5, 6, 7)$$

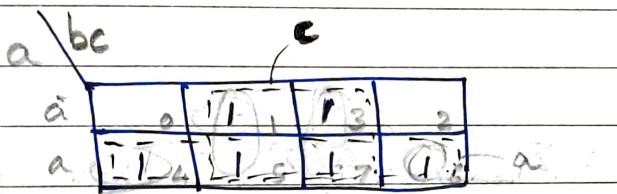

grouping: 1-cell : $\bar{a}\bar{b}c, \bar{a}bc, a\bar{b}\bar{c}, a\bar{b}c, ab\bar{c}, abc$

2-cell : $\bar{a}c, a\bar{b}, ac, ab, a\bar{c}, \bar{b}c, bc$

4-cell : a, c

EPI 2-cell : $\bar{a}c, ac, a\bar{c}$

EPI 4-cell : a, c

$$y = a + c$$

1357

$$\begin{aligned}
 & \bar{a}\bar{b}\bar{c} \\
 & + \bar{a}bc \\
 & + a\bar{b}c \\
 & + abc
 \end{aligned}$$

q. Construct K-map for sum and carry of full adder.

a	b	c	sum	carry
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

sum $y = \Sigma_m(1, 2, 4, 7)$ carry $y = \Sigma_n(3, 5, 6, 7)$

0	1	3	1
1	4	5	6

Sum

grouping 1-cell : $y = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc$

Carry : $y = \bar{a}bc + a\bar{b}c + ab\bar{c} + abc$

grouping 1-cell

0	1	3	2
4	5	7	6

EPI is same as PI

$$is \ abc + \bar{a}bc$$

$$+ ab\bar{c} + abc$$

$$\rightarrow 6 \\ 26 \quad \bar{a}b\bar{c} + ab\bar{c}$$

q:

0	0	1	0	1
1	0	1	1	1

$$\text{grouping 1 cell: } y = \bar{a}\bar{b}c + \cancel{a\bar{b}\bar{c}} +$$

$$y = \bar{a}\bar{b}c + \bar{a}bc + a\bar{b}c + abc + abc$$

2 cell

$$y = \bar{b}c + ac + ab + b\bar{c} \quad PI$$

$$PI \quad y = \bar{b}c + ac + b\bar{c}$$

$$\cancel{\bar{y}\bar{z} + \bar{y}z + y\bar{z} + yz} \\ \cancel{y(\bar{z}+z) + y(z+\bar{z})}$$

$$01 - \bar{a}\bar{b}$$

$$0\bar{a}b\bar{c}$$

$$1\bar{a}b\bar{c}$$

$$4a\bar{b}\bar{c}$$

$$5a\bar{b}c$$

$$01$$

$$45$$

$$67$$

0	1	00	01	11	10
0	1	11	10	01	00
0	1	10	01	11	10
1	0	11	10	01	00

grouping

$$\Sigma(0, 1, 2, 4, 5, 6, 7)$$

$$1 \text{ cell} \quad y = \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + \bar{a}b\bar{c} + \cancel{a\bar{b}\bar{c}} + \cancel{a\bar{b}c},$$

$$+ \cancel{ab\bar{c}} + \cancel{abc}$$

2 cell

$$y = \bar{a}\bar{b} + ab + ac + ab + b\bar{c}$$

4 cell

$$y = \bar{b}, a$$

$$PI \ 2 \text{ cell} \quad y = \bar{a}\bar{b} + \bar{a}b + ab + b\bar{c}$$

18th August, 2023

→ k-maps [4 variables]

eg: $f(a, b, c) = \sum_m (1, 2, 5, 6, 7)$

		bc						
		00	01	11	10			
		0	0	1	0	3	1	2
		1	0	1	1	1	1	1
			bc	ac	bc			ab

$$PI = \bar{b}c, ac, b\bar{c}, ab$$

$$EPI = \bar{b}c, ac, b\bar{c}$$

RPI = ab (shared EPI's)

(Redundant PI)

$$\text{minimal exp: } y = \bar{b}c + ac + b\bar{c}$$

eg: $\sum_m (0, 1, 5, 6, 7)$

		bc			
		10	11	13	12
		0	1	1	1
		1	1	1	1

$$PI : \underbrace{\bar{a}\bar{b}, ac, ab, b\bar{c}}_{EPI} \underbrace{\bar{b}}_{RPI}$$

⊗ q. $\sum_m (0, 1, 3, 4, 6, 7)$

list out PI & EPI for 2 cells grouping 4 cells grouping separately

2 cell grouping

a \ bc	00	01	11	10
00	1 ₀	1 ₂	1 ₃	1 ₂
01	1 ₄	1 ₅	1 ₇	1 ₆

$$PI: \bar{b}\bar{c}, bc, b\bar{c}, (\bar{a}b, ab, \bar{a}\bar{c}, a\bar{c})$$

$$EPI: \bar{b}\bar{c}, bc, b\bar{c}$$

RPI: remaining 4 terms

4 cell grouping

1		1	1
		1	0

$$y = b + \bar{c}$$

$$q4. \Sigma_m(1, 3, 5, 7)$$

$$q5. \Sigma_m(0, 4, 5)$$

$$q6. \Sigma_m(0, 2, 4, 6, 7)$$

$$q7. \Sigma_m(2, 3, 5, 7)$$

} Find minimal sdn.

Ans: 4.

a \ bc	00	01	11	10
0	0 ₀	1 ₁	1 ₃	0 ₂
1	0 ₄	1 ₅	1 ₇	0 ₆

$$y = c + \bar{a}b$$

5.

a \ bc

a \ bc	00	01	11	10
0	1 ₀	.	1 ₃	1 ₂
1	1 ₄	1 ₅	1 ₇	1 ₆

$$y = \bar{b}\bar{c} + ab$$

6.

	00	01	11	10
0	1	0	1	2
1	4	5	1	6

$$y = \bar{c} + ab$$

7. TM(2,3,5,7)

	00	01	11	10
0	1	0	3	2
1	4	5	7	6

$$y = \bar{a}\bar{b} + \bar{b}\bar{c} + a\bar{c}$$

$$\rightarrow f(a, b, c, d) = \sum_m (5, 6, 7, 8, 9, 10, 11, 13, 14, 15)$$

ab \ cd bd bc grouping all 16 will give 1

	00	01	11	10	
00	0 ₀	0 ₁	0 ₃	0 ₂	
01	0 ₄	1 ₅	1 ₇	1 ₆	
11	0 ₁₂	1 ₁₂	1 ₁₅	1 ₁₄	
10	1 ₈	1 ₉	1 ₁₀	1 ₁₁	

(1, 2, 4, 5, 6, 7, 8, 9, 10, 11, 13, 14, 15) $y = bd + bc + \bar{a}\bar{b}$

$$g: \sum_m (3, 4, 5, 7, 9, 13, 14, 15)$$

ab \ cd $\bar{a}cd$

	00	01	11	10	
$\bar{a}\bar{b}$ 00	0	.	1	2	bd
$\bar{a}\bar{b}$ 01	1	4	5	6	
ab 11 abc	12	13	15	16	abc
$a\bar{b}$ 10	8	19	11	10	

acd

$$y = bd + \bar{a}cd + abc + a\bar{c}d + \bar{a}b\bar{c}$$

redundant

Q1 + Q2

Q3, Q4
Q5, Q6

q3: $\Sigma_m(0, 1, 2, 4, 5, 8, 9, 10, 11)$

$ab \backslash cd$	00	01	11	10
$\bar{c}\bar{d}$	0_0	1	3	1_2
$\bar{c}d$	1_4	1_5	7	6
$c\bar{d}$	1_2	1_3	1_8	1_4
$c d$	1_8	1_9	1_{10}	1_9

$$y = \bar{a}\bar{c} + \bar{a}\bar{b} + \bar{b}\bar{d}$$

q.3. $\Sigma_m(4, 5, 6, 9, 13, 14)$

q.4. $\Sigma_m(0, 1, 4, 5, 7, 8, 9, 11, 12, 13, 15)$

q.5. $\Sigma_m(1, 5, 6, 7, 8, 9, 13, 15)$

Ans 3.

$ab \backslash cd$	$\bar{c}\bar{d}$	$\bar{c}d$	$c\bar{d}$	$c d$
$\bar{a}\bar{b}\bar{c}$	0	1	3	2
$\bar{a}\bar{b}$	1_4	1_5	7	1_6
$a\bar{b}$	0_{12}	1_{13}	1_5	1_{14}
$a\bar{b}$	8	1_9	1_{11}	1_0

$a\bar{c}d$

4.

\bar{c}	1_0	1_1	3	2
	1_4	1_3	1_7	6
	1_{12}	1_{13}	1_{15}	1_4
	1_8	1_9	1_1	1_0

$b\bar{d}$

$a\bar{d}$

5.

$\bar{a}b$	$\bar{a}\bar{d}$	$\bar{c}d$	
0	1	3	2
4	5	7	6
12	13	15	14
18	19	11	10

$\bar{a}b\bar{c}$

$\bar{a}b\bar{c}\bar{d}$

$\bar{a}\bar{b}c$

$\bar{a}\bar{b}cd$

q. 6. $f(a, b, c, d) = \bar{a}\bar{b}d + bcd + ab\bar{d} + b\bar{c}\bar{d}$

$m(1, 3, 4, 7, 9, 11, 12, 15)$


h/w q7. $f = a + \bar{c}$

q8. $f = \bar{a} + bd + ad$

q9. $f = \bar{a} + \bar{b}d + ac\bar{d}$


21st August, 2023

K-Maps (with don't care)

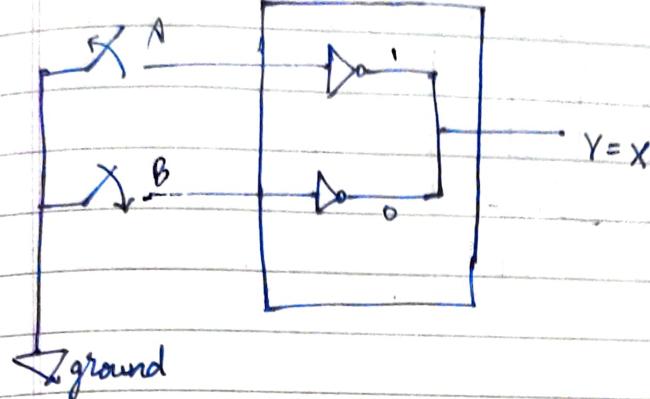


Z: floating value, anything b/w 0 & 1
X: 0/1.

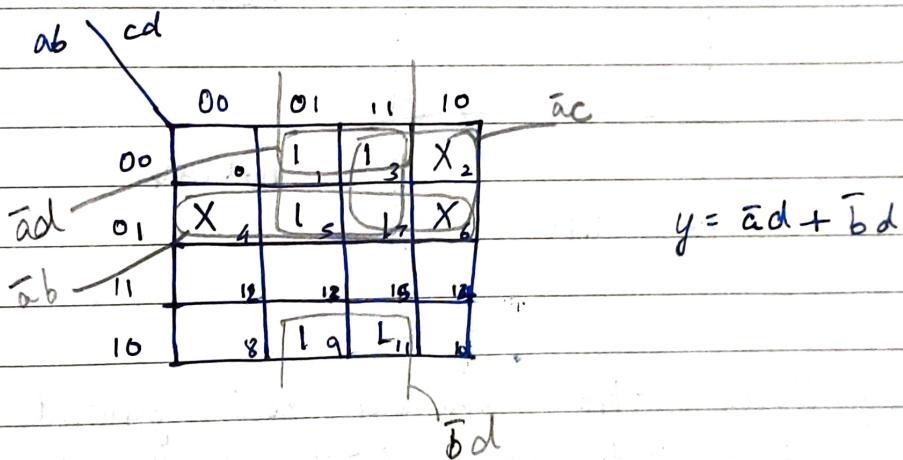q. $f = \sum_m (1, 2, 3, 5, 7, 9, 11) + d(2, 4)6$
don't care terms



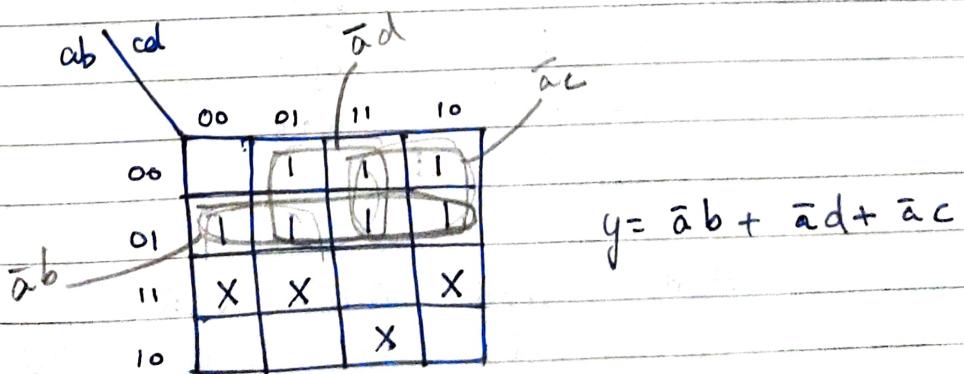q. $f = \sum_m (1, 2, 3, 4, 5, 6, 7) + d(11, 12, 13, 14)$



q: $\sum m(9, 10, 11) + d(12, 15)$


ab \ cd	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	X ₁₂	X ₁₃	X ₁₅	X ₁₄
10	8	9	11	10

ab\cd ab\c

Karnaugh maps

0	0000	0	
:	:	Valid	
:		9	
:		10	don't care
15	1111	15	

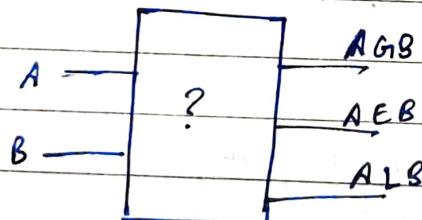q: Design 1-bit comparator and generate 3 o/p values indicating $A > B$, $A < B$, $A = B$




A	B	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

2-bit



(A > B) (A = B) (A < B)

A, A ₀	B, B ₀	A > B	A = B	A < B
0 0	0 0	0	1	0
	0 1	0	0	1
	1 0	0	0	1
	1 1	1	1	1
0 1	0 0	1	0	0
	0 1	0	1	0
	1 0	0	0	1
	1 1	0	0	1
1 0	0 0	1	0	0
	0 1	1	0	0
	1 0	0	1	0
	1 1	0	0	1
1 1	0 0	1	0	0
	0 1	1	0	0
	1 0	1	0	0
	1 1	0	1	0

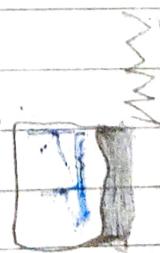

22nd August, 2023

Adder, Subtractor - 1

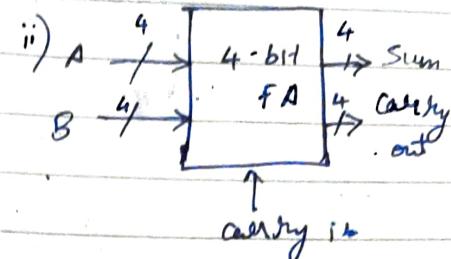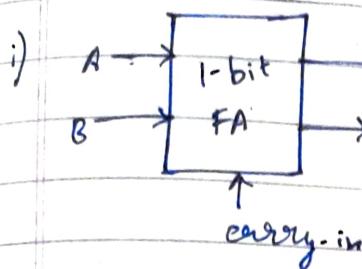

$$\text{eg: } y = A + B$$

$\downarrow \quad \downarrow$
4-bit 4-bit

$A_3 A_2 A_1 A_0$



$B_3 B_2 B_1 B_0$

$A_3 A_2 A_1 A_0$

$B_3 B_2 B_1 B_0$

$A[3:0]$

$B[3:0]$

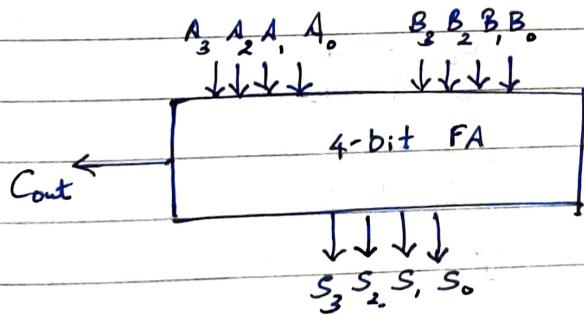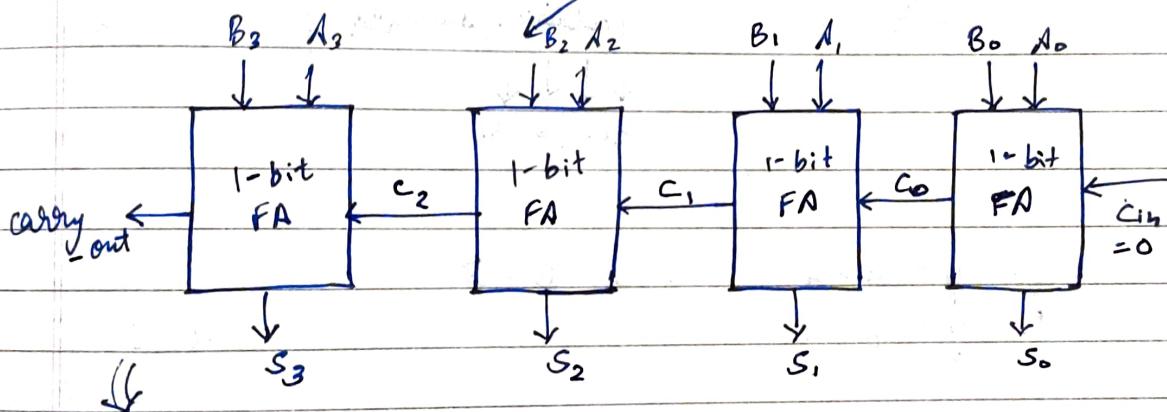


structural
modelling

XOR	P	Q	Y
	0	0	0

$$\text{if } P=0 ; Q=0/1 \\ y=Q \quad \textcircled{1}$$


0	1	1
1	0	1
1	1	0
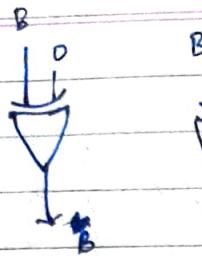
$$P=1; \\ y=\bar{Q} \quad \textcircled{2}$$



$$\begin{array}{r}
 A_3 \quad A_2 \quad A_1 \quad A_0 \\
 B_3 \quad B_2 \quad B_1 \quad B_0 \\
 + \qquad \qquad \qquad \qquad 0 \\
 \hline
 \end{array}$$
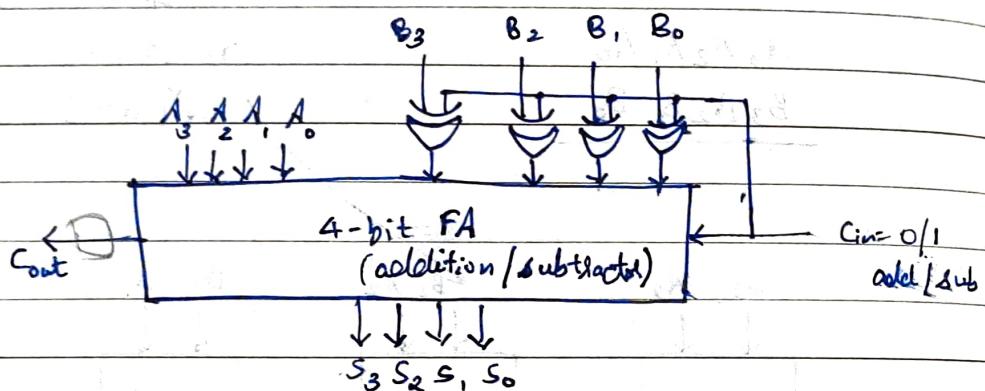
$$\begin{array}{c} A_3 \ A_2 \ A_1 \ A_0 \\ \bar{B}_3 \ \bar{B}_2 \ \bar{B}_1 \ \bar{B}_0 \end{array} \left. \begin{array}{l} \text{ } \\ \text{ } \\ \text{ } \\ + \end{array} \right\} 2's \ complement \text{ of } B \ (-B) \quad y = A - B$$



$$91. \quad y = B + A \quad A = 5; \quad B = 3$$

$$y = B - A$$

$$y = B + A$$

i/p 1 $B_3 B_2 B_1 B_0$

i | P 2 A₃ A₂ A₁ A₀

$$i \mid b_3 \quad C_{in} = 0$$

$$\begin{array}{r}
 \text{C}_2 \quad \text{C}_1 \quad \text{C}_0 \\
 \textcircled{1} \quad \textcircled{1} \quad \textcircled{1} \\
 \hline
 0 \quad 0 \quad 1 \quad 1 \\
 \hline
 0 \quad 1 \quad 0 \quad 1 \\
 \hline
 + \qquad \qquad \qquad 0 \\
 \hline
 \underbrace{0} \quad \underbrace{1 \quad 0 \quad 0 \quad 0}_{S_3 \quad S_2 \quad S_1 \quad S_0} \\
 \hline
 C_{out}
 \end{array}$$

$$y = B + (-A)$$

$$\begin{array}{cccccc} & \swarrow & 0 & 0 \\ \cancel{0} & 0 & 0 & 1 & 1 \end{array}$$

$\begin{pmatrix} 1 & 0 & 1 & 0 \end{pmatrix} \rightarrow$ (is comp of A using x_{01})

Since its 0
we should
neglect

+ |

(-2) by taking 2's comp. of ans.

$$\begin{array}{r} -A \\ -B \\ -A + (-B) \end{array}$$

(1) $A = -5$

$$2. A = -5$$

$$B = 3$$

$$\begin{array}{r} 3 \rightarrow 0 \ 0 \ 1 \ 1 \\ 5 \rightarrow 0 \ 1 \ 0 \ 1 \end{array}$$

$$y = B + A$$

$$\begin{array}{r} 0 \ 0 \ 1 \ 1 \\ 1 \ 0 \ 1 \ 1 \\ \hline 1 \ 1 \ 1 \ 0 \end{array} \quad \begin{array}{r} 1 \ 0 \ 1 \ 0 \\ + 1 \\ \hline 1 \ 0 \ 1 \ 1 \end{array} \rightarrow -5$$

$$y = B - A$$

$$\begin{aligned} y &= B + (-A) \\ &= 3 + (-(-5)) \end{aligned}$$

$$\begin{array}{r} 0 \ 0 \ 1 \ 1 \\ + 0 \ 1 \ 0 \ 1 \\ \hline 1 \ 0 \ 0 \ 0 \end{array}$$

$$A = -5 \Rightarrow 1 \ 0 \ 1 \ 1$$

$$-A = 5 \Rightarrow$$

$$\begin{array}{r} 0 \ 1 \ 0 \ 0 \\ + 1 \\ \hline 0 \ 1 \ 0 \ 1 \end{array}$$

$$\begin{array}{r} 3 \ 0 \ 0 \ 1 \ 1 \\ 5 \ 0 \ 1 \ 0 \ 0 \\ \hline 1 \ 0 \end{array}$$

$$\begin{array}{r} + 1 \ 0 \ 1 \ 1 \\ \hline 0 \ 1 \ 0 \ 0 \ 0 \end{array}$$


(14)

$$\begin{array}{r} 1 \ 1 \ 1 \ 0 \\ 0 \ 0 \ 0 \ 1 \\ + 1 \\ \hline 0 \ 0 \ 1 \ 0 \end{array}$$

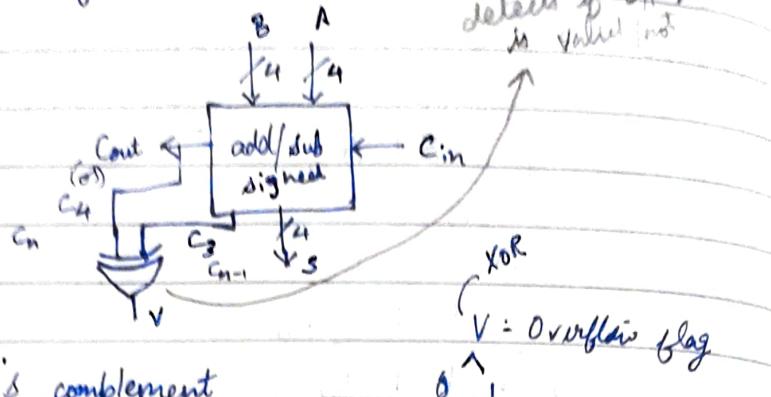(42)

24-th August, 2023 signed 4-bit adder with range -8 to +7
 # adder / sub overflow - 2

signed
 2^3 complement
 $(-8 \text{ to } +7)$



Decimal 2's complement

System

0	0 0 0 0	C _n	C _{n-1}	V
1	0 0 0 1			
2	0 0 1 0	0	0	NO
3	0 0 1 1	0	1	YES
4	0 1 0 0	1	0	YES
5	0 1 0 1	1	1	NO
6	0 1 1 0			
7	0 1 1 1			
-8	1 0 0 0			
-7	1 0 0 1			
-6	1 0 1 0			
-5	1 0 1 1			
-4	1 1 0 0			
-3	1 1 0 1			
-2	1 1 1 0			
-1	1 1 1 1			

i) (+2) and (-4)

$c_4 \ c_3 \ c_2 \ c_1$

(-2) 0 0 1 0

(-4) 1 1 0 0

+
 1 1 1 0

$c_3 = 0$

$c_4 = 0$

$V = 0$

ii) (-3) and (-2)

$$\begin{array}{r} \textcircled{1} \textcircled{1} \quad 0 \quad 0 \\ (-3) \quad 1 \quad 1 \quad 0 \quad 1 \\ (-2) \quad 1 \quad 1 \quad 1 \quad 0 \\ + \\ \hline \times 1 \quad 0 \quad 1 \quad 1 \end{array}$$

$c_3 = 1$
 $c_4 = 1$
 $V = 0$

iii) (+7) and (+6)

$$\begin{array}{r} \textcircled{1} \textcircled{1} \quad 1 \quad 0 \\ (+7) \quad 0 \quad 1 \quad 1 \quad 1 \\ (+6) \quad 0 \quad 1 \quad 1 \quad 0 \\ + \\ \hline \checkmark 0 \quad 1 \quad 1 \quad 0 \quad 1 \end{array}$$


$c_3 = 1$
 $c_4 = 0$
 $V = 1$

iv) (-7) and (-6) but we have 2's complement system so invalid

$$\begin{array}{r} \textcircled{1} \textcircled{0} \quad 0 \quad 0 \\ (-7) \quad 1 \quad 0 \quad 0 \quad 1 \\ (-6) \quad 1 \quad 0 \quad 1 \quad 0 \\ + \\ \hline 0 \quad 0 \quad 1 \quad 1 \end{array}$$

$c_3 = 0$
 $c_4 = 1$
 $V = 1$

Multiplexers / Mux

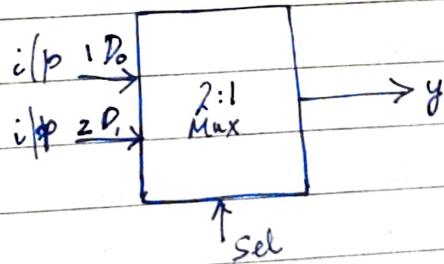

if 0 $y = i_1/p_1$
 1 $y = i_2/p_2$

TT	sel	D_0	D_1	y
0	0	0	0	0
0	0	1	0	0
0	1	0	0	1
0	1	1	0	1
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

if $s=0$
 $y = D_0$

if $s=1$
 $y = D_1$

sel	D_0	D_1	00	01	11	10
0	0	0	0	0	1	1
1	0	1	1	1	0	0

sel. D_1

$$y = \text{sel} \cdot D_1 + \overline{\text{sel}} \cdot D_0 \quad (\text{minimal exp})$$

reduced TT

(50%:

sel	D_0	D_1	y
0	0	0	0
1	1	1	1


does not matter

50% MEV
 mfp entered
 Variables

sel	y
0	D_0
1	D_1

$$y = \text{sel} \cdot D_0$$

$$y = \text{sel} \cdot D_1$$

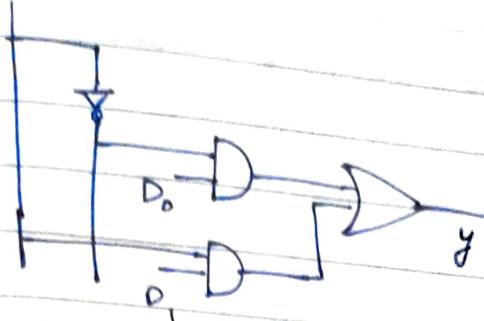


Mux circuit using 2-level implementation

$\rightarrow a \rightarrow y = a$ Buffer

* Tri state Buffer


E: enable

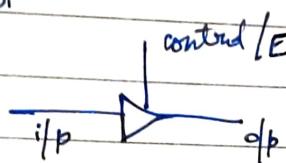

E	o/p
1	I/P
0	Z


Z: high impedance / floating value

Mux circuit using Tri state buffer

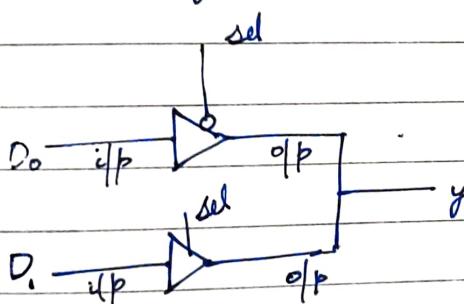

E	I/P	O/P
1	0	0
1	1	1
0	0	Z
0	1	Z

$\rightarrow 4:1$

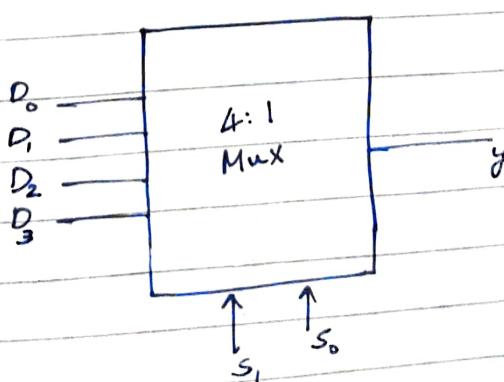


25th August, 2023

Logic implementation using Mux


q1. $y = A \cdot B$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

i) using 4:1 Mux

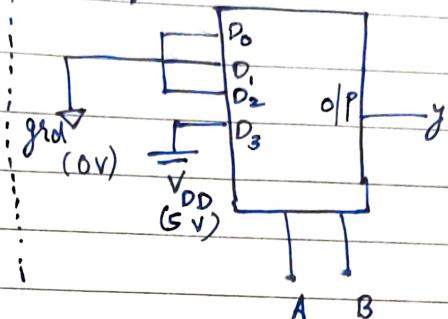

ii)

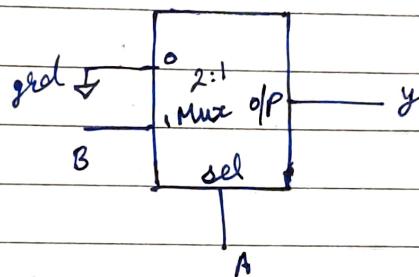



q2. implement a 2i/P xor gate using

i) 4:1 Mux

ii) 2:1 Mux

$y = A \oplus B$


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

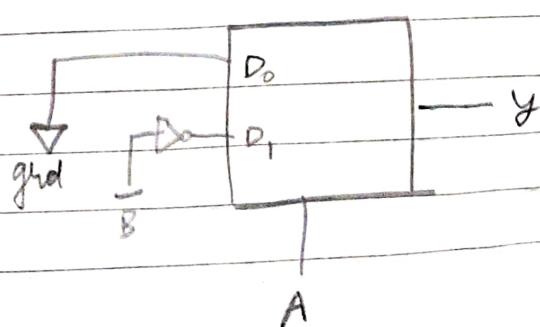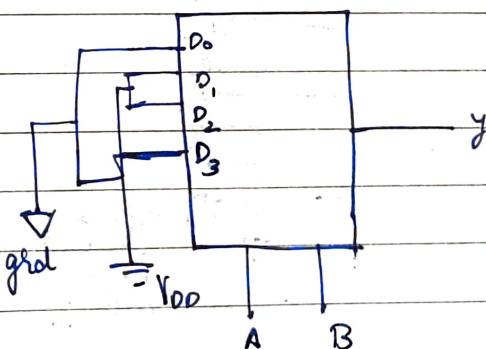


eg.3: Implement 1-bit full-adder sum and carry expression using 8:1 and 4:1 Mux.

	A	B	C _{in}	sum	carry	
0	0	0	0	0	0	B
1	0	0	1	1	0	D ₁
2	0	1	0	1	0	C _{in}
3	0	1	1	0	1	D ₃
4	1	0	0	1	0	C _{in}
5	1	0	1	0	1	D ₅
6	1	1	0	0	1	D ₇
7	1	1	1	1	1	B

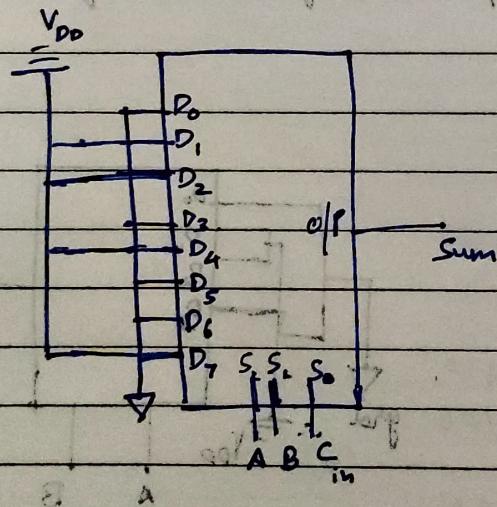
$$8:1 \text{ sum } f = \sum m(1, 2, 4, 7)$$




carry

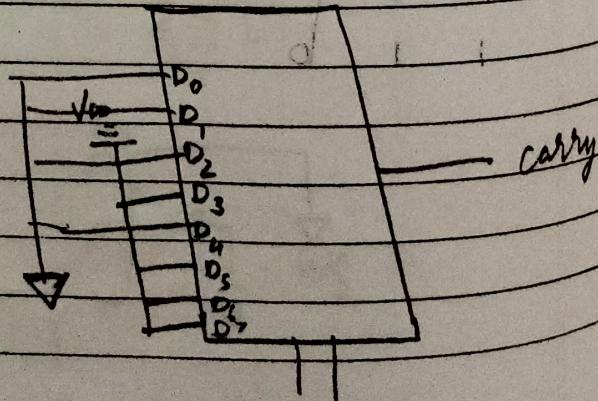

4.1 sum:

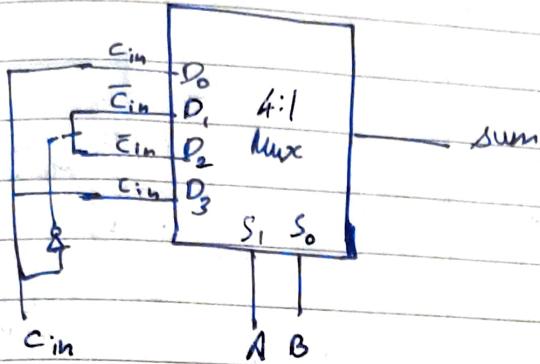


carry:

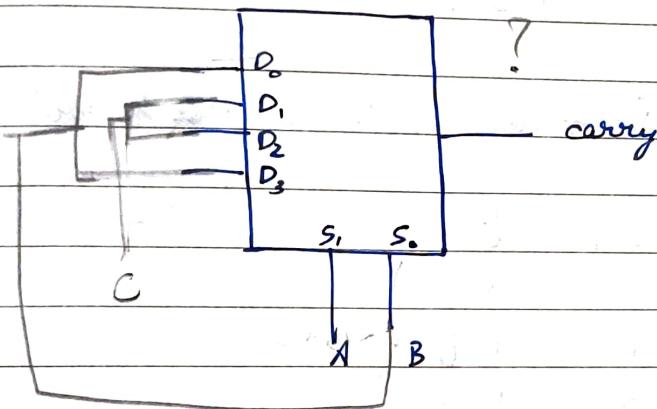

q4 Implement the given SOP $y = \bar{a}b + \bar{a}\bar{b}c + ab$
using 8:1 & 4:1 Mux

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

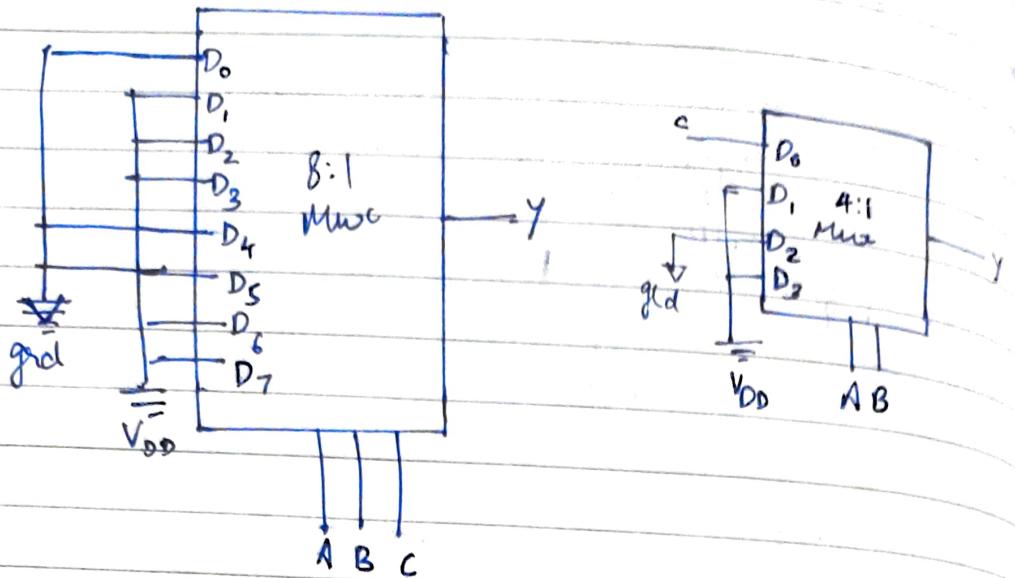


$$Q5. \quad y = \bar{a}b + \bar{a}\bar{b}c + ab \quad (\text{using } 2:1 \text{ Mux & additional hardware})$$

a	b	c _{in}	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$y = B + C$

$y = B$

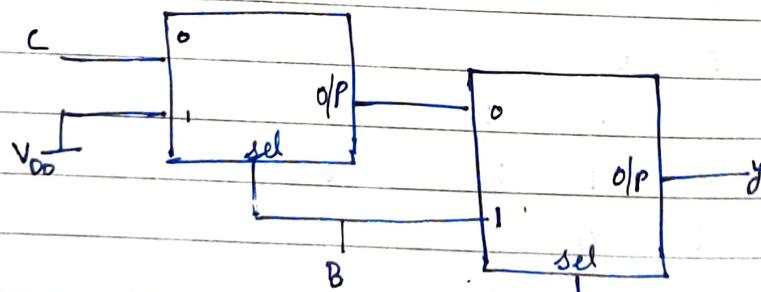


B	C	O/P
0	0	0
0	1	1
1	0	1
1	1	1

29th August, 2023

Decoders

mapping i/p to decimal equivalent

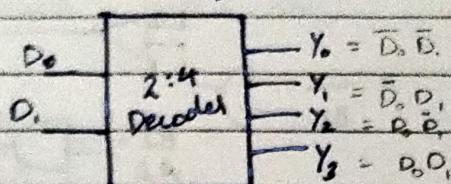

decoders

2:4

3:8

4:

$N: 2^N$

i/p o/p

Max

2:1




4:1

8:1

$2^n: 1$

D ₀	D ₁	Y ₀	Y ₁	Y ₂	Y ₃	
0	0	0	1	0	0	0000
1	0	1	0	1	0	1111
2	1	0	0	0	1	1111
3	1	1	0	0	0	1111

2-level
int

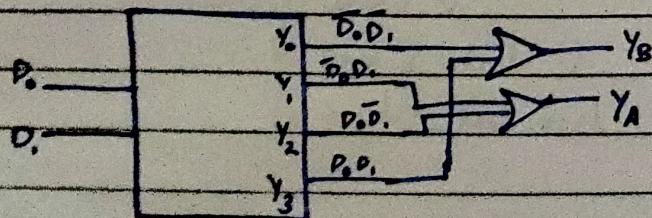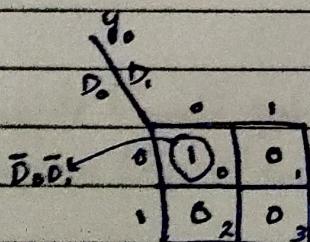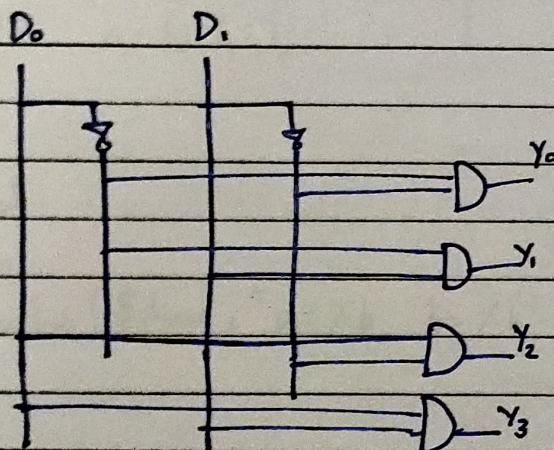

$$Y_3 \Rightarrow 2i/p \text{ AND}$$

$$Y_1 + Y_2 \Rightarrow 2i/p \text{ XOR}$$

$$\bar{D}_0 D_1 + D_0 \bar{D}_1$$

$$Y_A = D_0 \oplus D_1$$


$$Y_3 \Rightarrow 2i/p \text{ NAND}$$

$$Y_0 + Y_3 = 2i/p \text{ XNOR}$$

$$Y_B = \frac{\bar{D}_0 \bar{D}_1}{D_0 \oplus D_1}$$



$$= \frac{\bar{D}_0 \bar{D}_1}{D_0 \oplus D_1}$$

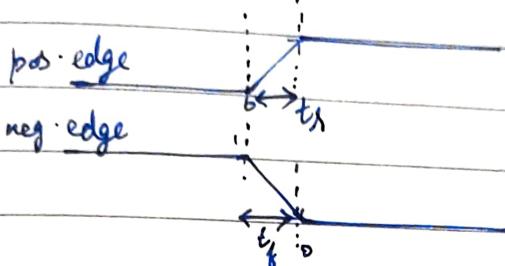* changing value from 0 to 1 : Positive edge (rise time) (t_{rise})



0 } static
1 } value




0 → 1 } Dynamic
1 → 0 } Values

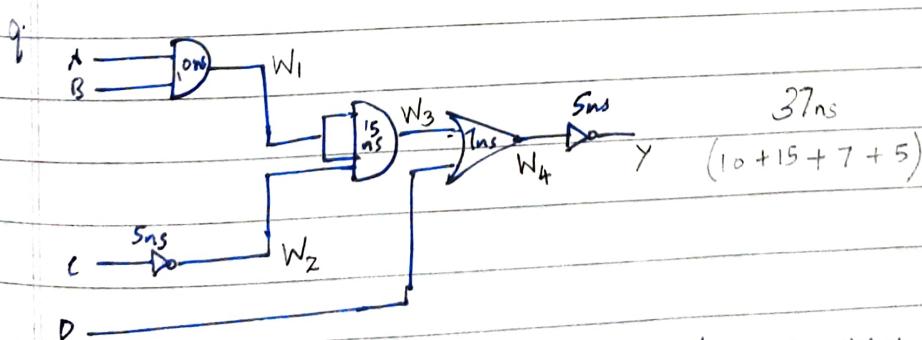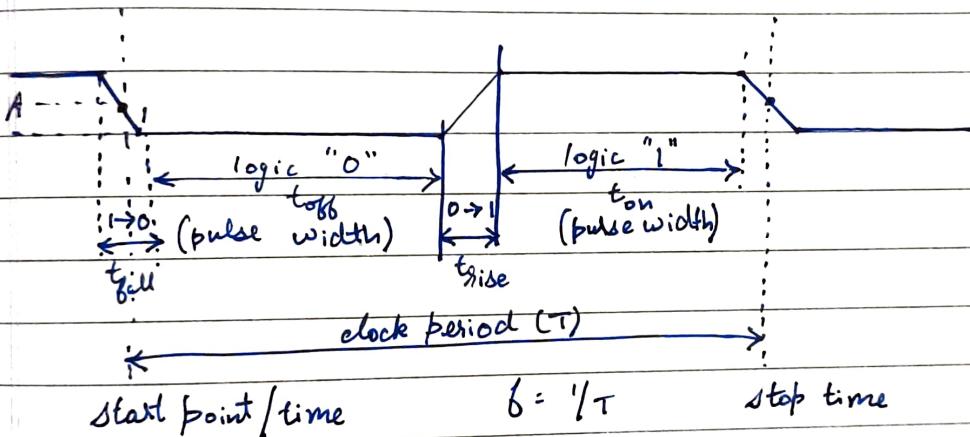

For the given circuit find out propagation delay.

31st August, 2023

Sequential Logic / Block

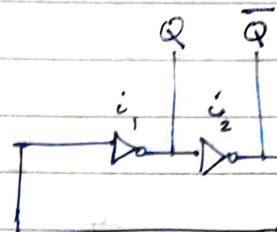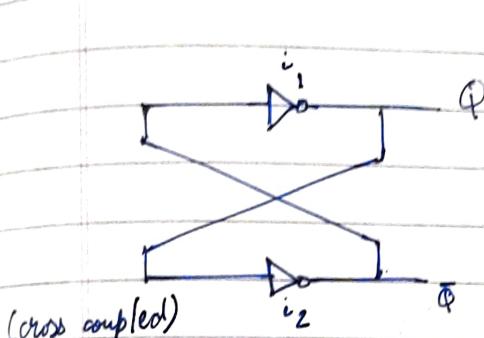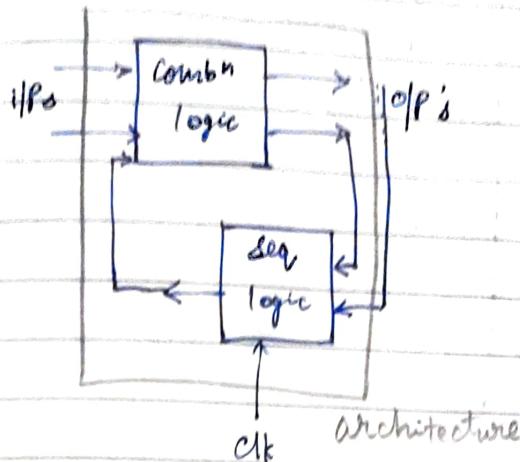


(connected back to back)


Bistable element

(a) 1-bit storage element


→ Latch

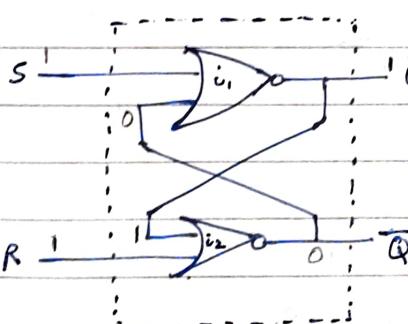

1. SR - latch
(using not)

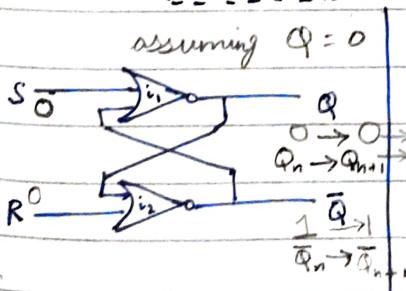

assuming $Q = 0$

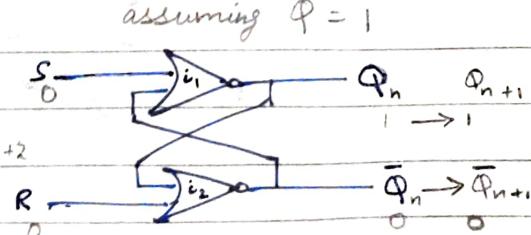

assuming $Q = 1$

Q_n : current state
 Q_{n+1} : next state


i_1, i_2 not

0	0	1
0	1	0
1	0	0
1	1	0

1) SR


	S	R	Q_n	Q_{n+1}	
①	0	0	0	0	No change
②	0	1	0	1	Set
③	1	0	0	0	Reset
④	1	1	0	X	Invalid

2. D - Latch

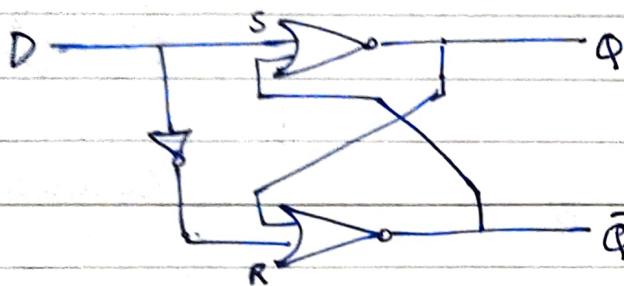


D	Q_n	Q_{n+1}	
0	0	1	Set
1	1	1	
1	0	0	Reset
1	0	0	

3. T - Latch

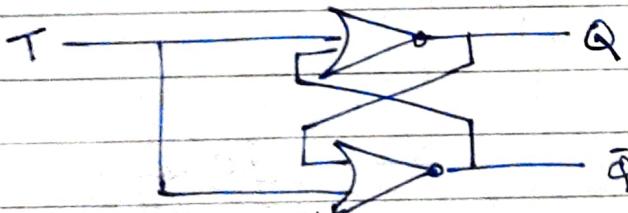

A: Gated SR Latch

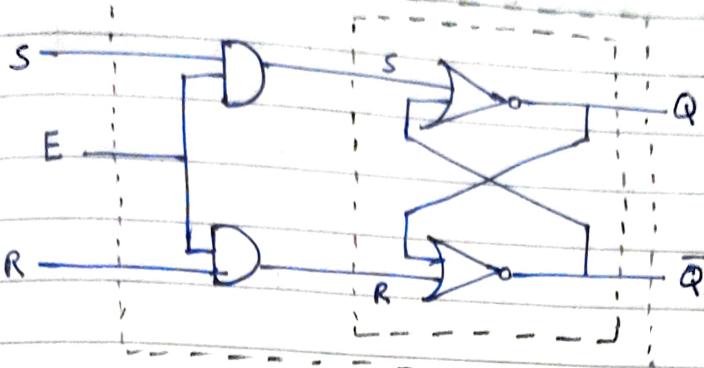

E	S	R	Q_n	Q_{n+1}
---	---	---	-------	-----------

0

No change

1

]

- * Latches are level triggering
- * Flip Flops are edge triggering

E	S	R	Q_n	Q_{n+1}
0	X	X	X	N.C

1st September, 2023

dataflow and structural programming of 2.0 Mezz

10 days feed:

6

6

4th September, 2023

(Refer Morris Mano book)

Gated D-latch (level triggered)

(levels of clock)

E/Clk D Q_n Q_{n+1}




0 X 0/1 0/1

NC { Transient

1 0 0/1 1
1 1 0/1 0


set { Not
reset Transient

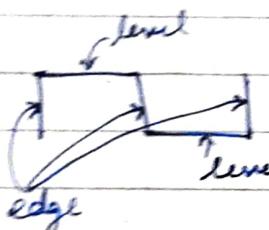

0 → 1 pos edge
1 → 0 neg edge

→ D - F/F

(+ve edge)

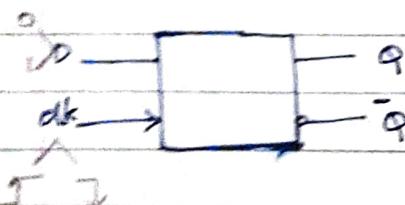


		Q _{n+1}	Q _n				
		D	Q _n				
E	0	00	01	11	10	01	00
	1	4	5	0 ₇	0 ₆	0 ₇	0 ₆

$$Q_{n+1} = E \bar{D} + \bar{E} Q_n$$

characteristic of D-latch

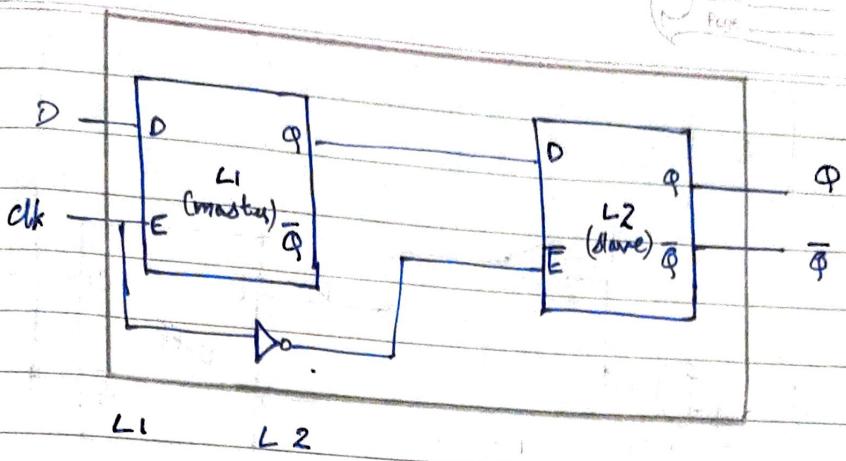* No change = transparent $\Rightarrow i/p = o/p$



\uparrow	0	Transparent	Not Transparent
\downarrow	1	Not-Transparent	Transparent
0	T	N	T

Clk D Q_{slave}

\uparrow	0/1	0/1
\downarrow	0/1	S/R

order: (Verilog implementation)

\rightarrow Bistable \rightarrow SR (not) \rightarrow D latch \rightarrow D-FF \rightarrow JK-FF \rightarrow T - FF


\rightarrow JK FF

J	K	Q_n	Q_{n+1}
---	---	-------	-----------

0	0	0/1	0/1
0	1	0/1	1
1	0	0/1	0
1	1	0/1	1/0

\rightarrow
pos edge

\rightarrow
neg edge

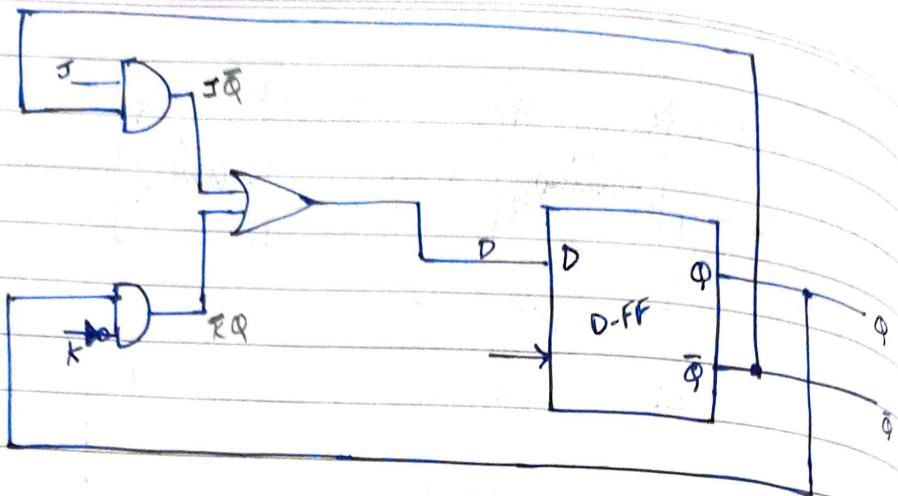

$$D = J\bar{Q} + \bar{K}Q$$

① If $J=0 ; K=0$

$$D = 0 + Q = Q$$

② If $J=0 ; K=1$

$$D = 0 + 0 = 0 \quad (\text{set}) \text{ at } Q$$

③ If $J=1 ; K=0$


$$D = \bar{Q} + Q = 1 \quad (\text{reset}) \text{ at } Q$$

④ If $J=1 ; K=1$

$$D = \bar{Q} + 0 = \bar{Q} \quad (\text{Toggle})$$

* D-FF if clk is +ve it will hold memory for 1 clk period.

→ T-FF

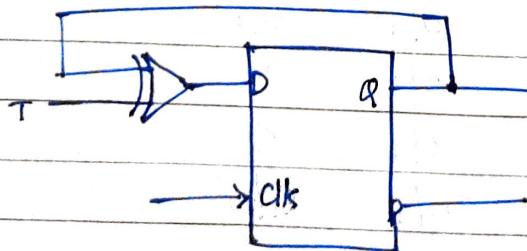

$$D = T \oplus Q$$


$$= TQ' + T'Q$$

(from D-FF)

Can also be built from JK
by shorting J & K

shifting data towards right $\Rightarrow \div$
shifting data towards left $\Rightarrow \times$

4-bit registers in sequence

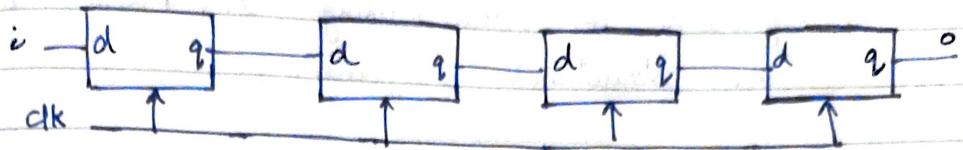


	clk	i	Q_3	Q_2	Q_1	Q_0	
①	↑	1	1	0	0	0	$(8)_d$
②	↑	0	0	1	0	0	$(4)_d$
③	↑	0	0	0	1	0	$(2)_d$
④	↑	0	0	0	0	1	$(1)_d$

		8	4	2	1	
↑	1	1	0	0	0	(8)
↑	1	1	1			(12)
↑	1	1	1	1		(14)
↑	1	1	1	1	1	(15)

5th September, 2023

Flip-Flop with "Enable"

case study: D-FF

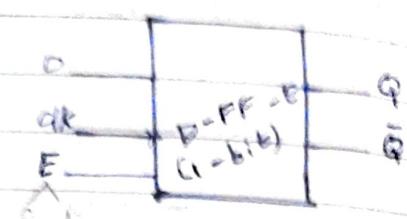

T-T clk D Q

(flip follow)	↑	0	0
	↑	1	1

T-T E clk D Q

0	↑	0	0
0	↑	1	1
1	↑	0	Q _{prev}
1	↑	1	Q _{prev}

* Universal shift register


1. Right (÷) → logical: cascading MSB with 0s
→ Arithmetic:
1_a (sign)

2. Left (x)

3. Rotate → left
→ right


4. Nop

→ D-FF with Enable

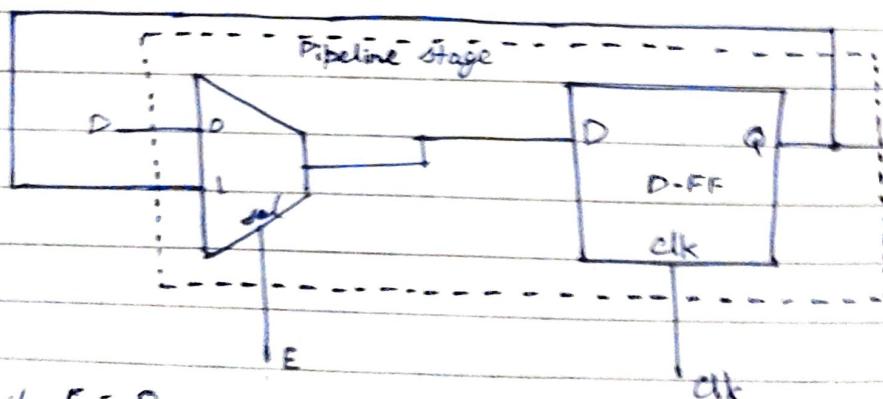

if $E = 0$; $Q = D$
 $E = 1$; $Q = \text{prev. value}$

→ 4-bit D-FF with E

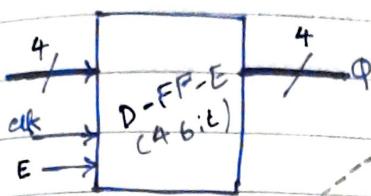

4-bit shifting reg
(Shift right, NOP)


$D_3 D_2 D_1 D_0$

$Q_3 Q_2 Q_1 Q_0$

$$\downarrow \quad \downarrow \quad \downarrow \quad \downarrow$$

$Q_3 Q_2 Q_1 Q_0$
D $D_3 D_2 D_1$

LSR | ASR

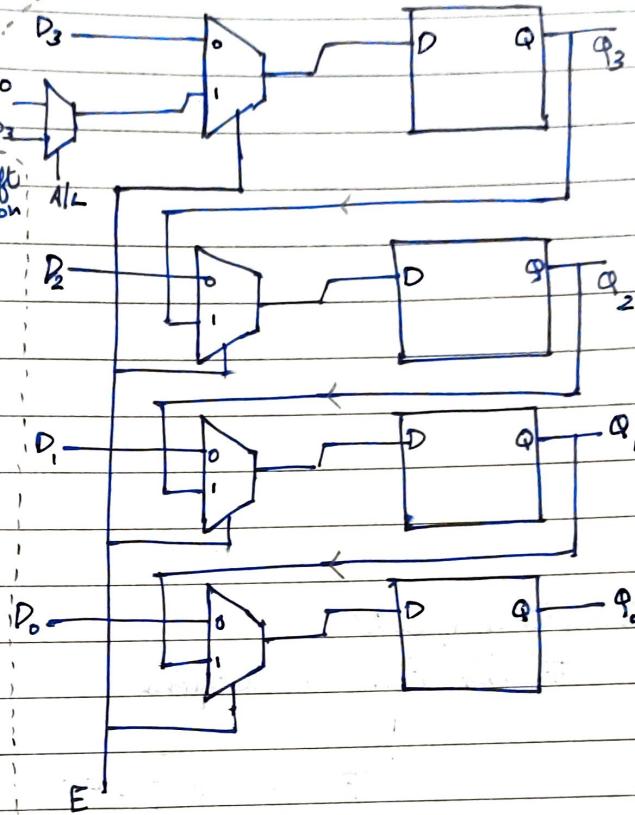

→ Shift left, NOP


$Q_3 \ Q_2 \ Q_1 \ Q_0$

$$\begin{matrix} \downarrow & \downarrow & \downarrow & \downarrow \\ D_3 & D_2 & D_1 & D_0 \end{matrix}$$

$Q_3 Q_2 Q_1 Q_0$

$P \quad P \quad P \quad O$

no arithmetic

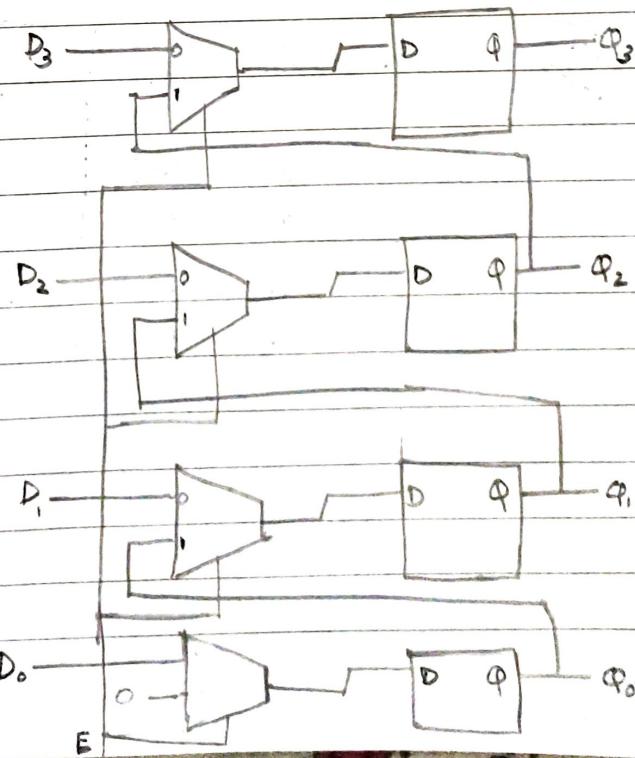

q. Implement $y = ax^3$ using less no. of hardware resources .
 a : 4 bit binary value
 x : 2 bit binary value

7th September, 2023

Flip-Flop conversions

SR - FF \longrightarrow D - FF
 (available) (Target)

T.T SR-FF

	S	R	Q_n	Q_{n+1}				
P.S	0	0	X	N.C	0	0	0	X
N.S	0	1	X	D	0	1	1	0
	1	0	X	I	1	0	0	I
	1	1	X	?	1	1	X	0

excitation Table of S-R-FF mandatory

Step 1: T-T of target device (D-FF)

D Q_n Q_{n+1}

0	0	0
0	1	0
1	0	1
1	1	1

Step 2: Excitation Table of source (SR-FF)

Q_n Q_{n+1} S R



0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Step 3: Conversion Table


D Q_n Q_{n+1} S R

0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0

Step 4.

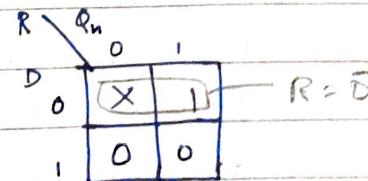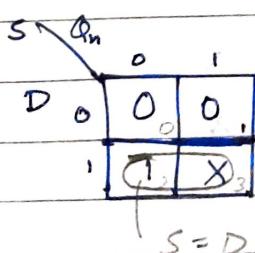

Step 5

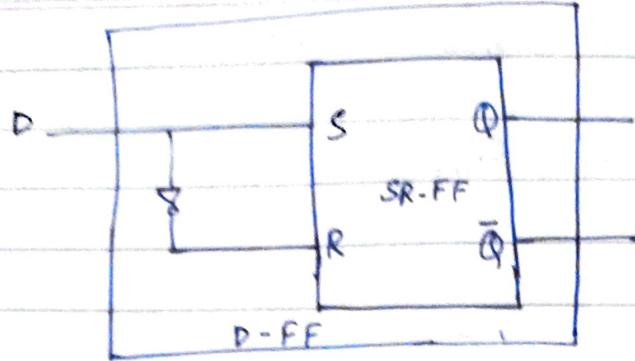

q2 Convert SR-FF to T-FF

Step 1 TR of T-FF

T	Q_n	Q_{n+1}	
0	0	0	g N.C
0	1	1	
1	0	1	$\therefore Q_{n+1} = \bar{Q}_n$
1	1	0	

Step 2 excitation table of source (SR-FF)

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0


Step 3 conversion table

T	Q_n	Q_{n+1}	S	R
0	0	0	0	X
0	1	1	X	0
1	0	1	1	0
1	1	0	0	1

Step 4:

S	Q_n
T	0 1
R	X 0
$S = T \bar{Q}_n$	1 0

R	Q_n
T	0 1
S	X 0
$R = T \bar{Q}_n$	0 1

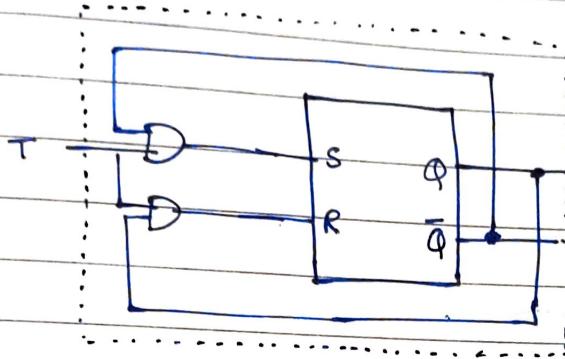

q3. Convert D-FF to JK-FF

Step 1: TT of JK-FF

J	K	Q_n	Q_{n+1}
0	0	0/1	0/1
0	1	0/1	1
1	0	0/1	0
1	1	0/1	1/0

Step 2: excitation table of source (D-FF)

Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1


Step 3 conversion table

D	Qn Qn+1	J	K
1	1	1	1
2	2	2	2
3	3	3	3
100	100	100	100

11th September, 2023

Q late
Q early

FSM: Finite State Machine

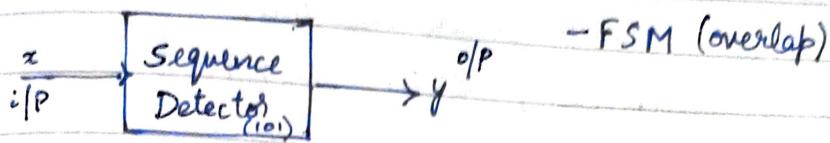


$x \quad \underline{1010} \quad \underline{1110}$

$y \quad 1 \quad 1 \quad 1$
(overlapped)

$y \quad 1 \quad \quad \quad 1$
(non-overlapped)

① State Diagrams

ip/o/p (a) x/y

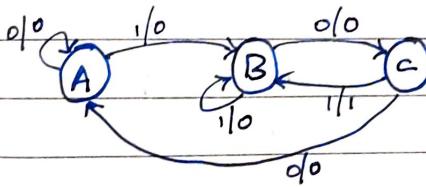

A is initial state

@ B $\begin{cases} 10 \\ 11 \end{cases}$

@ C $\begin{cases} 100 & \text{c to A} \\ 101 & \text{c to B} \end{cases}$

② State Table

	x		y
PS	ip	NS	o/p

A	0	A	0
	1	B	0
B	0	C	0
	1	B	0
C	0	A	0
	1	B	1

$\oplus \Rightarrow$ next value

③ Conversion Table

(with Binary Encoding)

A: 00, B: 01, C: 10

PS	ip	NS	op	F-F ip eqn.
Q_1, Q_0	x	Q_1^+, Q_0^+	y	$D_1 \quad D_0$
00	0	00	0	0 0
00	1	01	0	0 1
01	0	10	0	1 0
01	1	01	0	0 1
10	0	00	0	0 0
10	1	01	1	0 - 1

TT of D-FF

clk	D	$Q_n(Q)$	$Q_{n+1}(Q^+)$
↑	0	0	0
		1	0
↑	1	0	1
		1	1

excitation table of D-FF

Q_0	Q_0^+	D_0
0	0	0
0	1	1
1	0	0
1	1	1

$D = Q^+$

④ K-map

ip variable : Q_1, Q_0, x

op variable : y, D_1, D_0

$D_1, Q_0 \bar{x}$

		00	01	11	10	
		0	0 ₀	0 ₁	0 ₃	1 ₂
Q ₁		0	0 ₄	0 ₅	X ₇	X ₆
		1	0 ₁	1	X	X

$D_1 = Q_0 \bar{x}$

$D_0, Q_0 \bar{x}$

		00	01	11	10	
		0	0	1	1	0
Q ₁		0	0	1	X	X
		1	0	1	X	X


$D_0 = x$

$y, Q_0 \bar{x}$

		00	01	11	10
		0	0	0	0
Q ₁		0	0	1	X
		1	0	1	X


$y = Q_1 x$

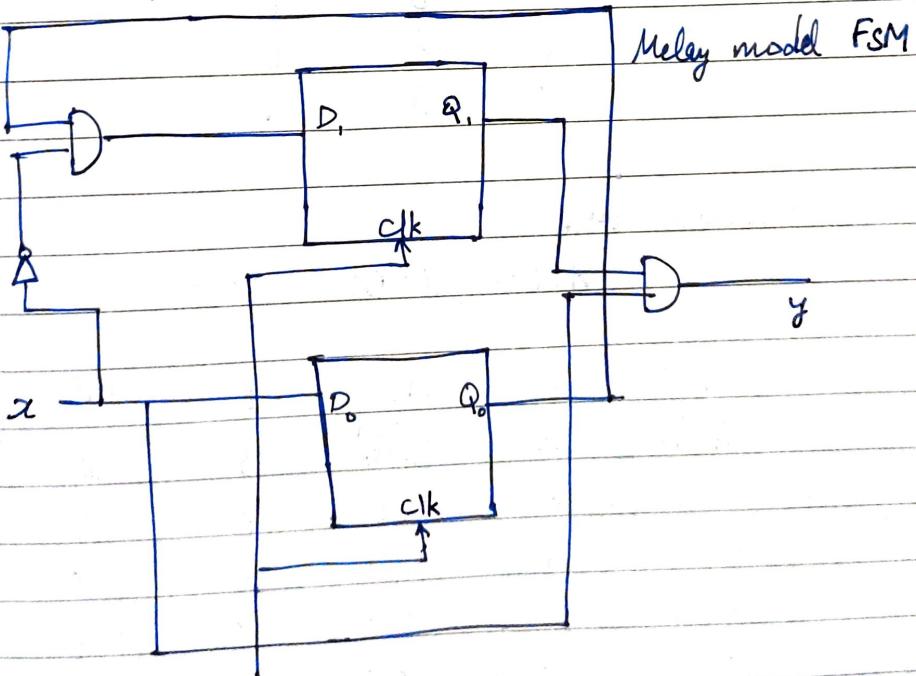⑤ Hardware implementation / External view



— FSM (non-overlap)

1. State Diagram

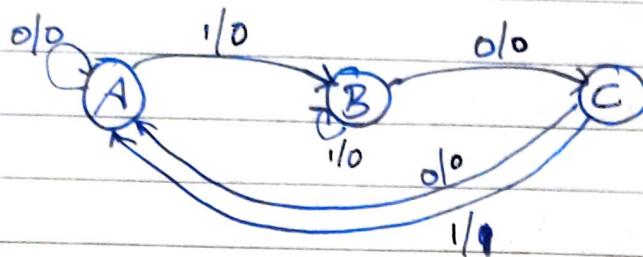

2. State Table

PS	IP	NS	OP
----	----	----	----

A	0	A	0
	1	B	0
B	0	C	0
	1	B	0
C	0	A	0
	1	A	1

3. Conversion Table

A: 00, B: 01, C: 10

PS	IP	NS	OP	FF _{IP eqn.}
Q ₁ , Q ₀	x	Q ₁ ⁺ , Q ₀ ⁺	y	D ₁ , D ₀
00	0	00	0	0 0
00	1	01	0	0 1
01	0	10	0	1 0
01	1	01	0	0 1
10	0	00	0	0 0
10	1	00	1	0 0

D_1	$\Phi_0 x$	
0	00	00
1	01	01
2	10	10
3	11	11
4	X	X
5	X	X
6	X	X

$$D_1 = \Phi_0 \bar{x}$$

D_0	$\Phi_0 x$	
0	00	00
1	01	01
2	10	10
3	11	11
4	X	X
5	X	X
6	X	X

$$y = Q_1 x \quad (\text{same as } D_0)$$

q 10111

12th September, 2023

Moore Model FSM

* reset = 1 \Rightarrow triggered for FSM
marks the initial state

Melage

N states


ip / op

Moore

N+1 states

of associated with
labels of states

e.g: 101 (overlap)

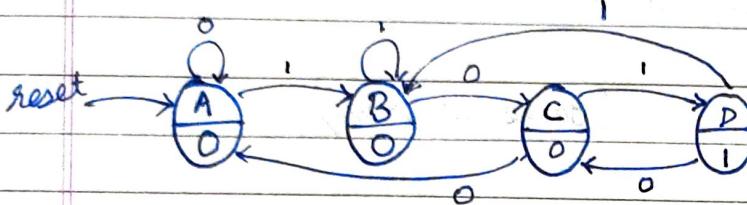

A is initial state

B $1 \xrightarrow{10}$
 $\xrightarrow{11}$

if no overlap
(only last 2 states will change)

C $10 \rightarrow 100$
101

D $101 \rightarrow 1010$
 $\xrightarrow{1011}$

$$\begin{aligned} \text{TT: } Q &= D \\ \text{ET: } D &= Q^+ \end{aligned}$$

P.S		N.S		Y	D ₁ , D ₀	
Q_1, Q_0		Q_1^+, Q_0^+				
00	A	0	A	00	0	0 0
1	B	01			0	1
01	B	1	B	01	0	1
0	C	10			1	0
10	C	1	D	11	0	1 1
0	A	00			0	0
11	D	0	C	10	1	0
1	B	01			0	1

P_1

P_0


P_1	P_0	00	01	11	10
P_1	0	0 0	0 1	1 1	1 0
1	0	1 0	0 1	0 1	0 0
		4 5	6 7	8 9	10 11


Date _____
Page _____

$$D_1 = P_0 \bar{z} + P_1 \bar{P}_0 z$$


$$D_0 = z \quad (\text{from Table})$$

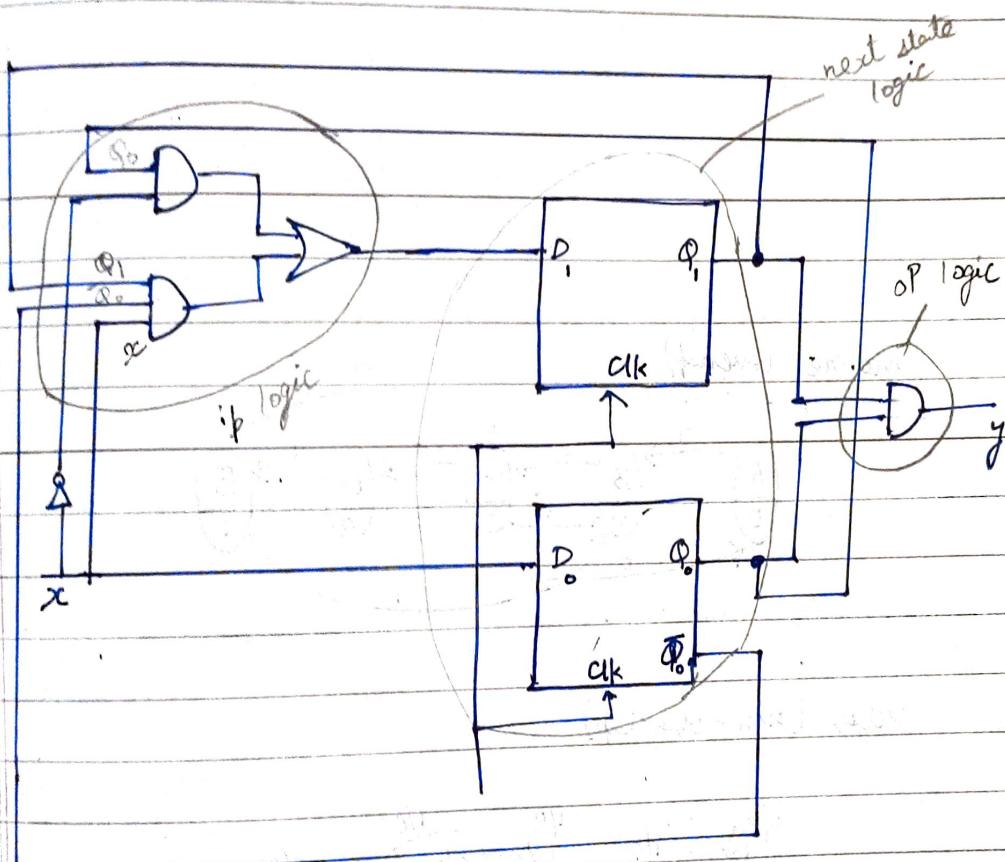$y = Q_1 Q_0$ (depends only on Present state)
(independent of x)




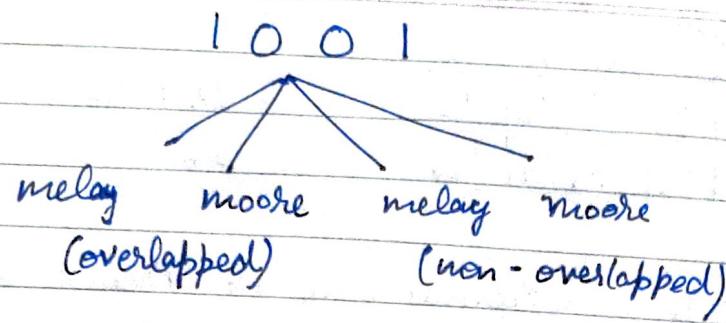


~~moore~~
melay (overlap)

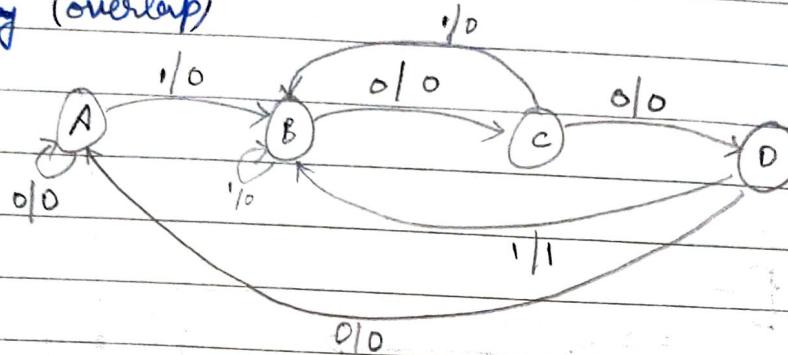


moore (overlap)

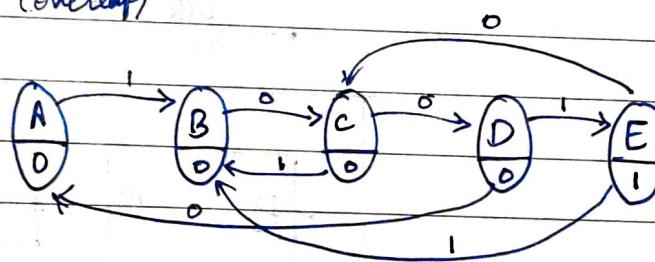

melay (non-overlap)

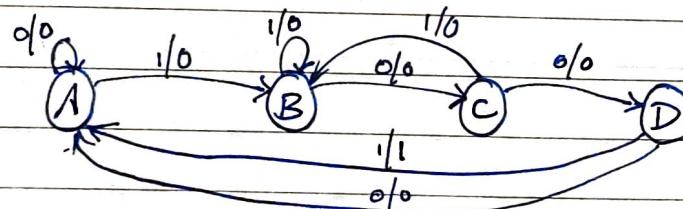

moore (non-overlap)

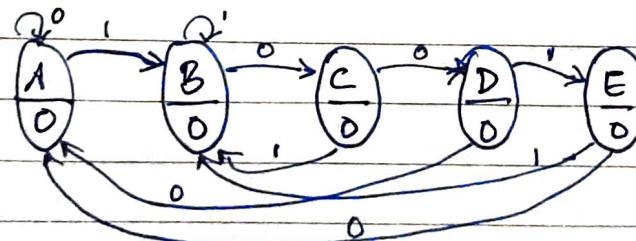

September, 2023
reset



one hot
coding

P.S	N.S	
$Q_2 Q_1 Q_0$	$Q_2^+ Q_1^+ Q_0^+$	$D_2 D_1 D_0$
0 0 1		
0 1 0		
1 0 0		

This increases complexity (3 FFs)
hardware decoder but still it's better

State Table :

P.S	N.S	y
S_0	S_1	1
S_1	S_2	0
S_2	S_0	0

Binary encoding : (2 FFs)

P.S	N.S	y
00	01	1
01	10	0
10	00	0

One Hot coding :

P.S	N.S	y	$D_2 D_1 D_0$
$Q_2 Q_1 Q_0$	$Q_2^+ Q_1^+ Q_0^+$		$(D = Q^+)$
S_0 : 0 0 1	0 1 0	1	0 1 0
S_1 : 0 1 0	1 0 0	0	1 0 0
S_2 : 1 0 0	0 0 1	0	0 0 1

we use $Q_1 Q_0 \chi$ & $y D_1 D_0$ k-map but here we don't need k-maps, D can be represented in terms of Q


$$D_2 = Q_1 \quad i/p eqn.$$

$$D_1 = Q_0 \quad \text{of D-FF}$$


$$D_0 = Q_2$$

$$y = Q_0$$

3/2

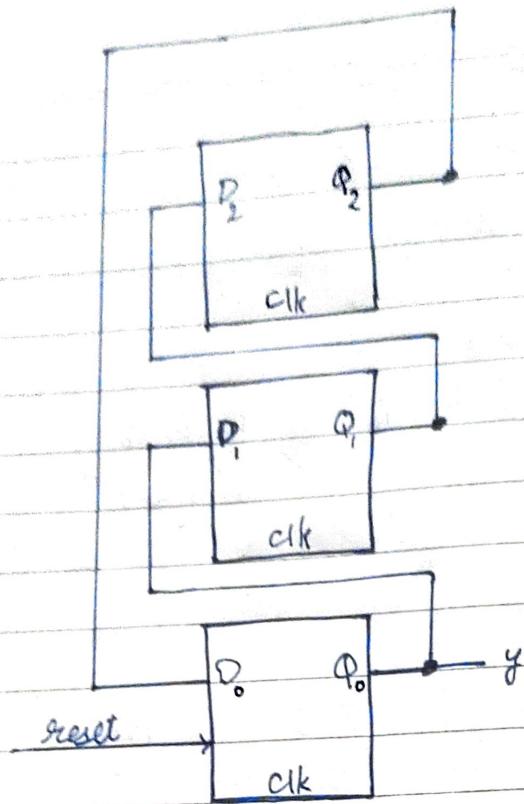

clk	reset	
↑	1	
↑	0	
↑	0	
↑	0	S_0

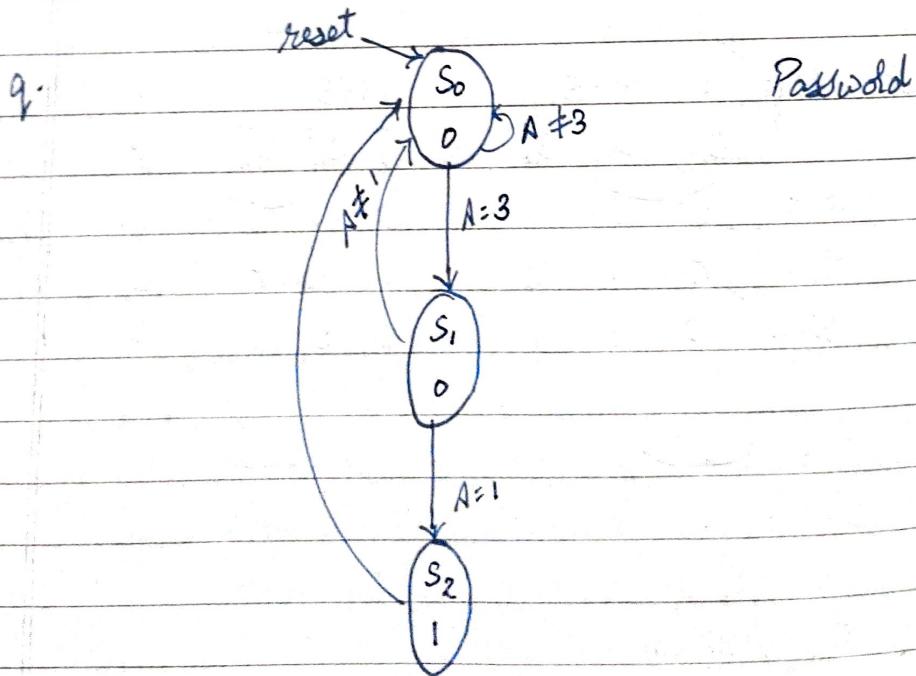

A is 2bit

$[1:0]$

0, 1, 2, 3

State Table:

	P.S	I/P	N.S	y
S_0	0		S_0	0
	1		S_0	
	2		S_0	
	3		S_1	
S_1	0		S_0	0
	1		S_2	
	2		S_0	
	3		S_0	
S_2	0		S_0	1
	1		S_0	
	2		S_0	
	3		S_0	

Conversion Table

	P.S	I/P	N.S	y	$(D = Q^+)$
Q_1, Q_0	A_1, A_0		Q_1^+, Q_0^+		D_1, D_0
S_0	00		00		00
00	01		00	0	00
	10		00		00
	11		01		01
S_1	00		00		00
01	01		10	0	10
	10		00		00
	11		00		00
S_2	00		00		00
10	01		00	1	00
	10		00		00
	11		00		00

12, 13, 14, 15 don't care

K-map
A-variable
 $(A \times 4 = 16)$

I/P : $Q_1 Q_0 \quad A, \bar{A}$

$D_1 \quad A, \bar{A}$

$Q_1 Q_0$

$Q_1 Q_0$	00	01	11	10
D_1	0	1	2	3
$Q_1 Q_0$	4	5	6	7
$\bar{Q}_1 \bar{Q}_0$	X	X	X	X
\bar{D}_1	8	9	11	10

$\bar{Q}_1 \bar{Q}_0 \bar{A}, \bar{A}$

$\bar{Q}_1 \bar{Q}_0 \bar{A}, \bar{A}$


$D_1 = \bar{Q}_1 Q_0 \bar{A}, \bar{A}$ (without don't cares) ✓

$D_1 = Q_1 \bar{Q}_0 \bar{A}, \bar{A}$ (with don't cares) X

we cannot give don't care as it is password

$D_0 = \bar{Q}_1 \bar{Q}_0 A, \bar{A}$ (we don't need K-map as there is only one 1)

q: Traffic Light Control

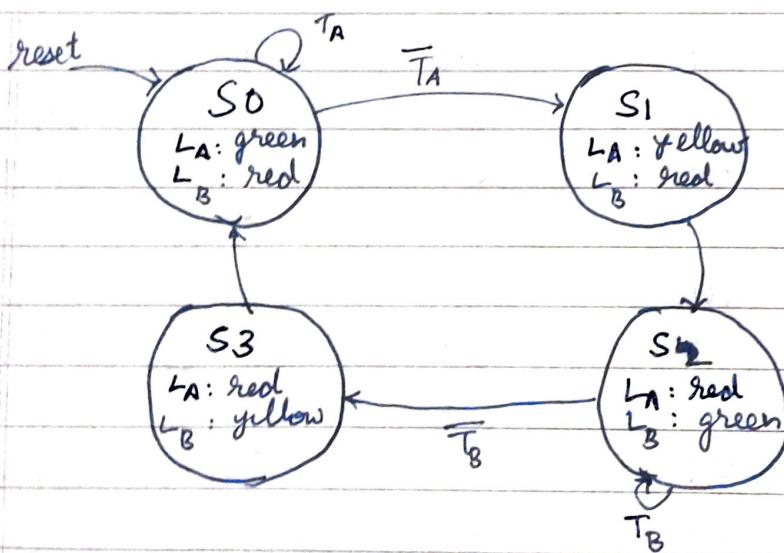

PS I/P NS

S_0	$\overline{T_A}$	S_1
	T_A	S_0
S_1	-	S_2


S_2	$\overline{T_B}$	S_3
	T_B	S_2
S_3	-	S_0

15th September, 2023

Counters

$\text{reset} = 1 \Rightarrow \text{start from } 00$


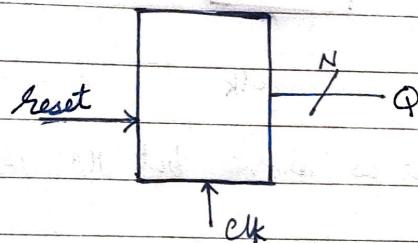
$\text{reset} = 0 \Rightarrow \text{take prev. value then } +1.$




$$Q_{n+1} = Q_n + 1$$

eg: $N = 2$ bit

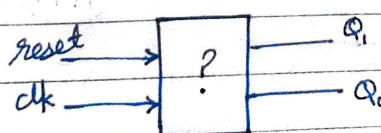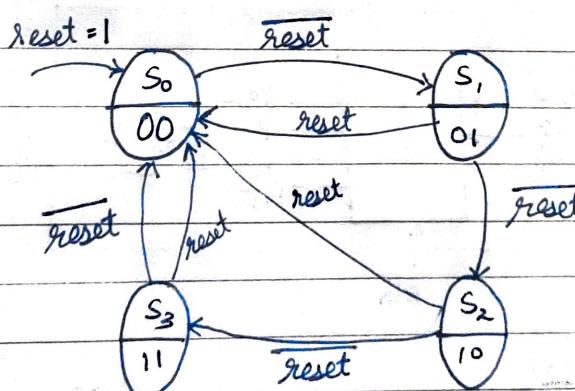$0 \rightarrow 1 \rightarrow 2 \rightarrow 3$




→ internal view

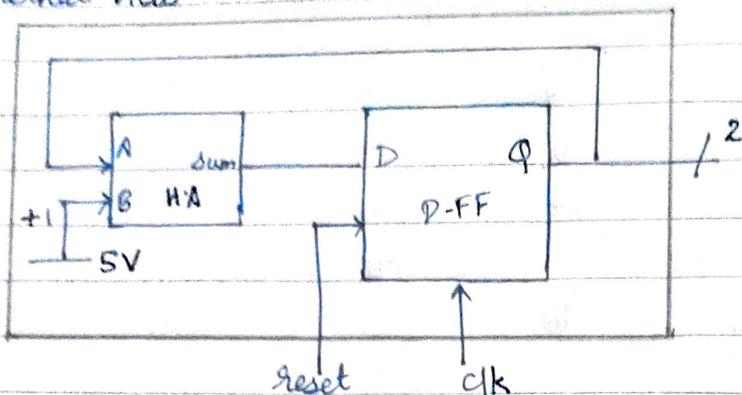



(it has no user ip)

① With Enable, Reset

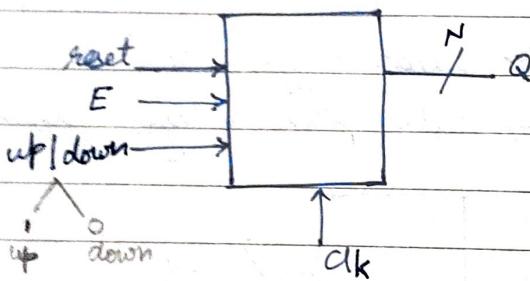

(internal view as above but FA with add/sub)

② Terminal counter

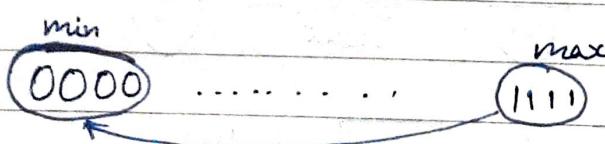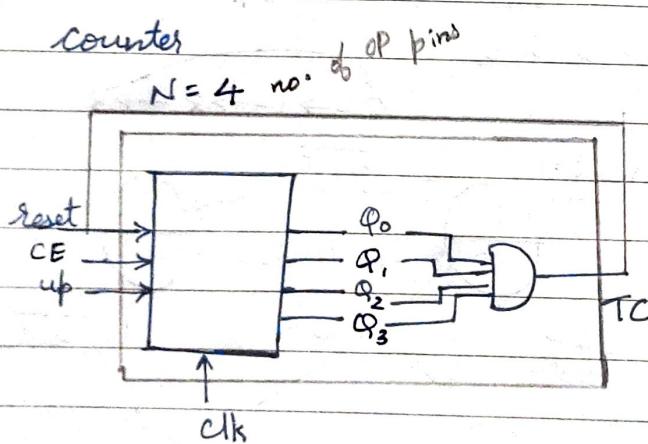


③ modulus $(\text{os}) \bmod N$


$$N = 10$$

$$0 - 9$$

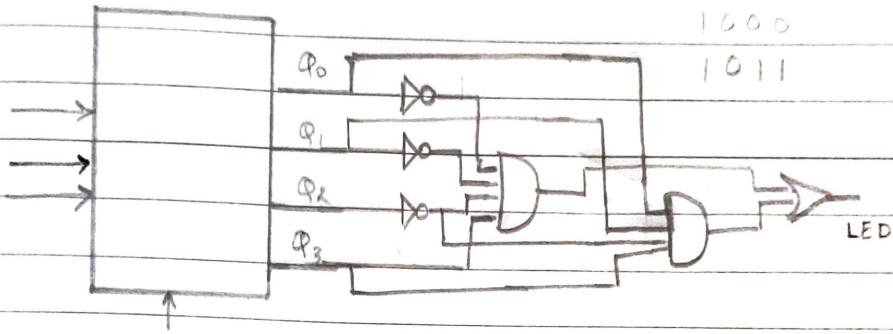q: Design a 4-bit counter, activate LED as final OP once counter reaches 9th clock cycle of 12th clock cycle.



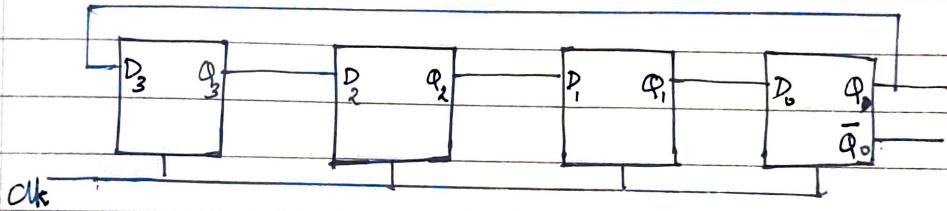q: Design a 4-bit ring counter, considering initial state as 1000



Ring Counter

Clk	Q_3	Q_2	Q_1	Q_0
↑	1	0	0	0
↑	0	1	0	0
↑	0	0	1	0
↑	0	0	0	1

$Q_3 = Q_0$ Ring counter
1-iteration of 4-bit ring counter

arithmetic right shift

1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1
0	0	0	0

1-iteration of 4-bit Johnson counter

logical right shift

0	1	1	1
0	0	1	1
0	0	0	1
0	0	0	0

Johnson counter

$Q_3 = \bar{Q}_0$ Johnson counter