

18th April, 2023

Unit - 3

Three Phase AC

Definition: 3 phases

1 neutral (shared)

R-Y-B colour coding


Voltage lags w.r.t each other by 120°

20th April, 2023

$$V_R = V \angle 0^\circ$$

$$V_Y = V \angle -120^\circ$$

$$V_B = V \angle -240^\circ$$

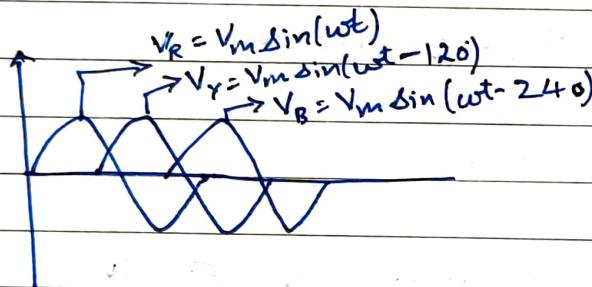

Balanced System



Balanced Source

Balanced Load



$$|V_R| = |V_Y| = |V_B|$$

$$|Z_R| = |Z_Y| = |Z_B|$$

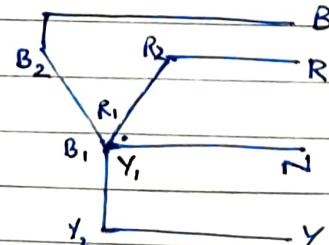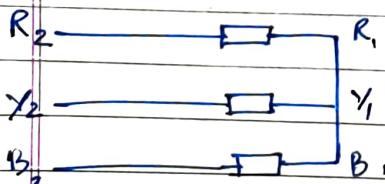1. Star Connection (Y / W_{yc}) - similar ends are tied together



2. Delta Connection -

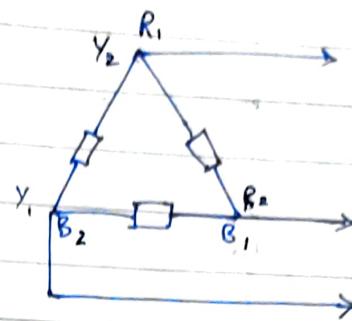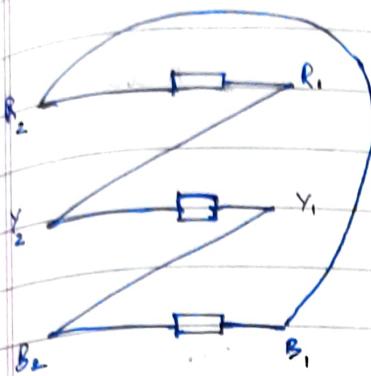

26th April, 2024

→ 3-Φ AC

- Advantages of 3-Φ over 1-Φ (4-6M)
- Generation of 3-Φ
- Phase sequence RYB
RBY

e.g.: In a 3-Φ balanced AC system 415V, 50Hz is loaded with $5+j10 \Omega$

$$Z_R = 5+j10 = Z_Y = Z_B$$

$$V_R = 415 \angle 0^\circ$$

$$V_Y = 415 \angle -120^\circ$$

$$Z_R = 5+j10 = 11.78 \angle 63.4^\circ$$

$$V_B = 415 \angle -240^\circ$$


$$I_R = 2 \angle -63.4^\circ$$

$$I_Y = 2 \angle -63.4 - 120^\circ$$

$$I_B = 2 \angle -63.4 - 240^\circ$$

- Derivation $V_L = \sqrt{3} V_{ph}$ stat (4M)
- Derivation $I_L = \sqrt{3} I_{ph}$ Delta
- Derivation $P = \sqrt{3} V_L I_L \cos \phi$ (8M) (X)
- Derivation $\phi = \tan^{-1} \left[\frac{\sqrt{3}(\omega_2 - \omega_1)}{\omega_2 + \omega_1} \right]$ (2M)

Star/Y/WYE connection

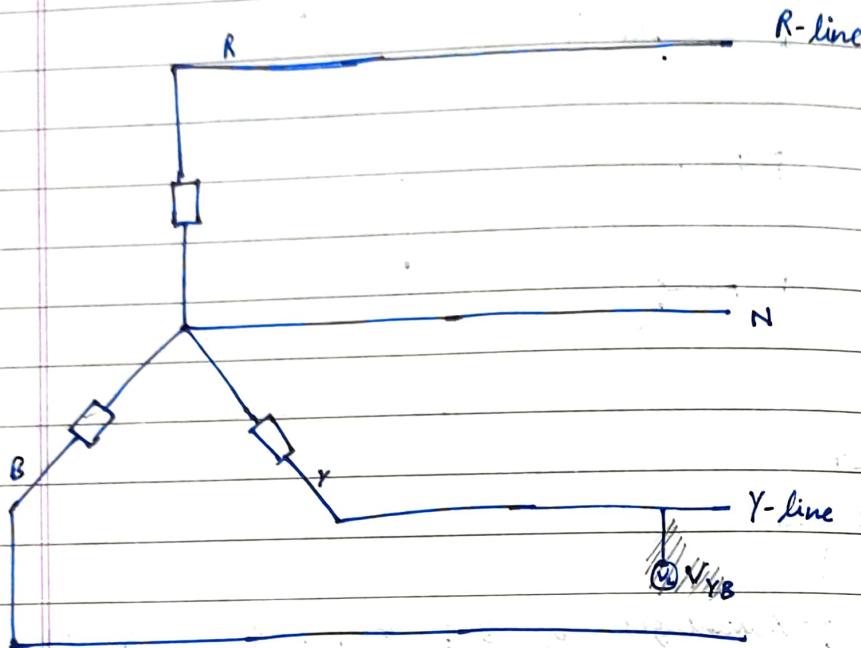

Line Voltage
 V_L I_L

&
 Phase Voltage
 V_{ph} I_{ph}

$V_L \rightarrow$ Line voltage : voltage b/w two lines.

$I_L \rightarrow$ Line current : current flowing through a line

$V_{ph} \rightarrow$ Phase voltage : Voltage across a phase

(b) Voltage b/w a line & neutral

$I_{ph} \rightarrow$ Phase current : current flowing through a phase


$$Y \rightarrow \begin{cases} I_L = I_{ph} \\ V_L \neq V_{ph} ; V_L = \sqrt{3} V_{ph} \end{cases}$$

$$\Delta \rightarrow \begin{cases} V_L = V_{ph} \\ I_L \neq I_{ph} ; I_L = \sqrt{3} I_{ph} \end{cases}$$

25th April, 2023

Date _____
Page _____

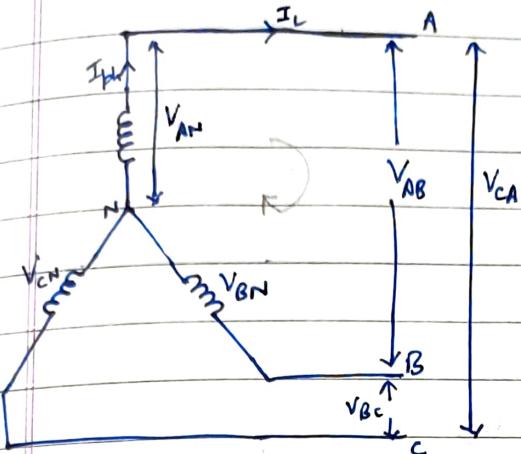→ To prove that $V_L = \sqrt{3} V_{ph}$ in star connection



From circuit diagram $I_L = I_{ph}$

$$\text{Let } \vec{V}_{AN} = V_{ph} \angle 90^\circ \quad (\text{assumption})$$


$$\vec{V}_{BN} = V_{ph} \angle 90 - 120^\circ = V_{ph} \angle -30^\circ$$

$$\vec{V}_{CN} = V_{ph} \angle 90 - 240^\circ = V_{ph} \angle -150^\circ$$

$$\text{KVL : } -\vec{V}_{AB} - \vec{V}_{BN} + \vec{V}_{AN} = 0$$

$$\vec{V}_{AB} = \vec{V}_{AN} - \vec{V}_{BN}$$

$$\text{let } |V_{AB}| = |V_{BC}| = |V_{CA}| = V_L$$

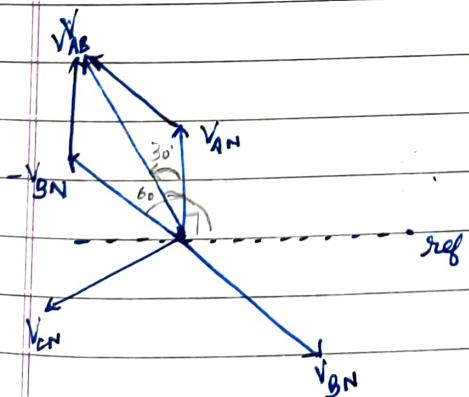

$$|V_{AB}|^2 = |V_{AN}|^2 + |V_{BN}|^2 + 2 |V_{AN}| |V_{BN}| \cos(\text{angle b/w } V_{AN} \text{ & } V_{BN})$$

$$V_L^2 = V_{ph}^2 + V_{ph}^2 + 2 V_{ph} \cdot V_{ph} \cos(60^\circ)$$

$$V_L^2 = 2 V_{ph}^2 + 2 V_{ph}^2 \cdot \left(\frac{1}{2}\right)$$

$$V_L^2 = 3 V_{ph}^2$$

$$V_{AB} = V_L \angle 120^\circ$$


$$V_{BC} = V_L \angle 0^\circ$$

$$V_{CA} = V_L \angle -120^\circ$$

$$V_L = \sqrt{3} V_{ph}$$

* Line voltage leads corresponding phase voltage by 30°

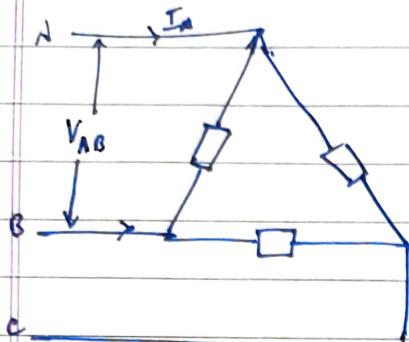→ To prove that $I_o = \sqrt{3} I_{ph}$ in Δ connection,



From circuit diagram,

$$|V_L| = |V_{ph}|$$

$$\text{Let } \vec{V}_{AB} = V_L \angle 120^\circ$$


$$\therefore \vec{V}_{BC} = V_L \angle 0^\circ$$

$$\vec{V}_{CA} = V_L \angle -120^\circ$$

$$\vec{I}_{AB} = \frac{\vec{V}_{AB}}{Z_0} = \frac{V_L \angle 120^\circ}{Z_0} = \frac{V_{ph}}{Z_0} \angle 120^\circ$$

$$\vec{I}_{BC} = I_{ph} \angle 0^\circ$$
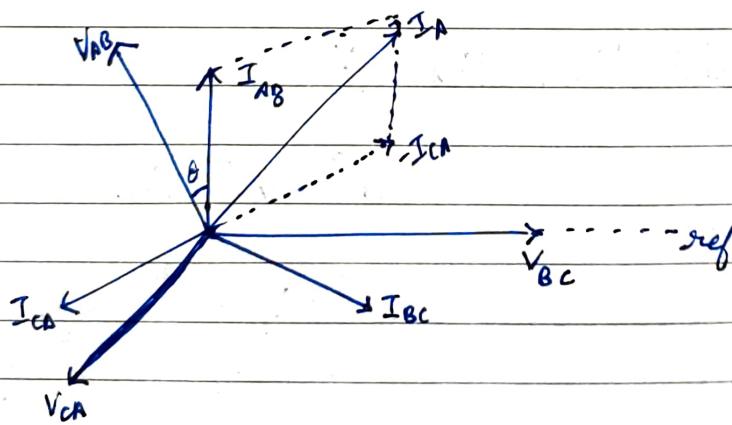
$$I_{CA} = I_{ph} \angle 0^\circ - 120^\circ$$



KCL at node m

$$\vec{I}_A - \vec{I}_{AB} + \vec{I}_{CA} = 0$$


$$\vec{I}_A = \vec{I}_{AB} - \vec{I}_{CA}$$

26th April, 2023




Power Measurement

Wattmeter

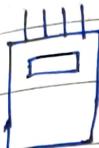


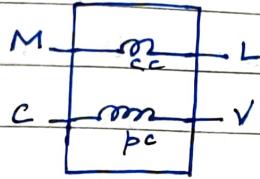M current coil
C pressure coil/potential coil



M → mains
L → Load
C → common
V → voltage

1- ϕ Power

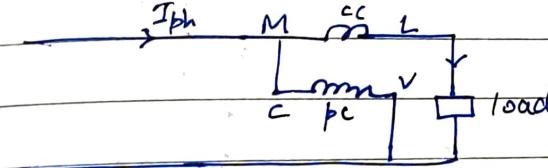

$$P = \cos \phi = V_{ph} I_{ph} \cos \phi$$

3- ϕ Power

$$\Phi_{3\phi} = P_R + P_Y + P_B$$

$$= V_{ph} I_{ph} \cos \phi + V_{ph} I_{ph} \cos \phi + V_{ph} I_{ph} \cos \phi$$

$$\boxed{P_{3\phi} = 3 V_{ph} I_{ph} \cos \phi}$$

$$Y \text{ connected } V_{ph} = \frac{V_L}{\sqrt{3}} \rightarrow I_{ph} = I_L ; \Delta \text{ connected } V_{ph} = V_L$$

$$I_{ph} = \frac{I_L}{\sqrt{3}}$$

$$P_{3-\phi} = \frac{3 V_L I_L \cos \phi}{\sqrt{3}}$$

$$P_{3-\phi} = \sqrt{3} V_L I_L \cos \phi$$

$$P_{3-\phi} = \frac{3 V_L I_L \cos \phi}{\sqrt{3}}$$

$$P_{3-\phi} = \sqrt{3} V_L I_L \cos \phi$$

Power measurement


→ One Wattmeter method

→ Two Wattmeter method ✓ (in syllabus)

→ Three Wattmeter method

are enough

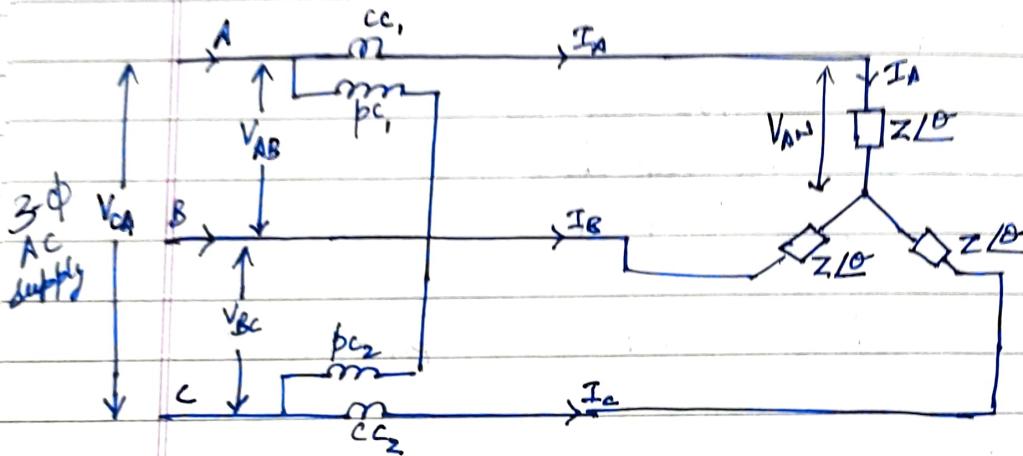→ Prove that 2 wattmeters to measure power, in a 3-φ system, when a load is star connected.



$$\text{Let } \overrightarrow{V_{AB}} = V_L \angle 0^\circ$$

$$\overrightarrow{V_{BC}} = V_L \angle 0^\circ$$

$$\overrightarrow{V_{CA}} = V_L \angle -120^\circ$$

$$\overrightarrow{V_{AN}} = V_{ph} \angle 90^\circ$$

$$\overrightarrow{V_{BN}} = V_{ph} \angle -30^\circ$$


$$\overrightarrow{V_{CN}} = V_{ph} \angle -150^\circ$$

I_A lags V_{AN} by θ

I_B lags V_{BN} by θ

I_C lags V_{CN} by θ

P-39 Delta \rightarrow B/w

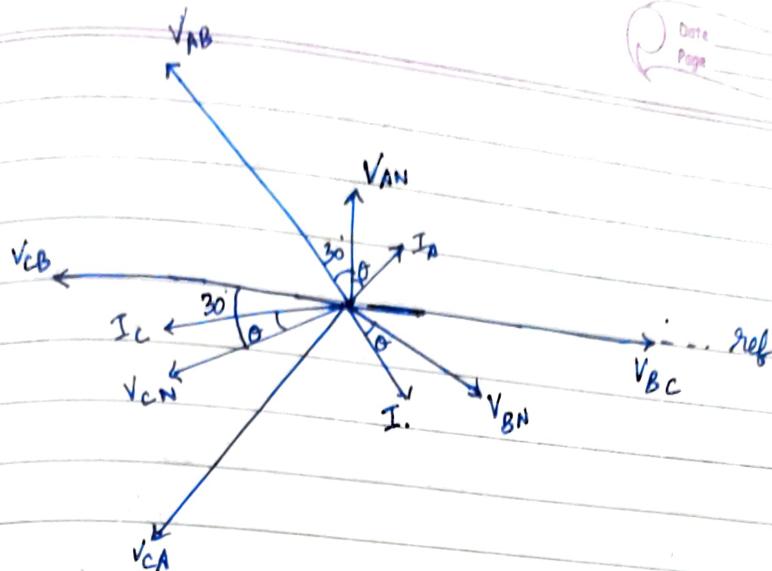

Wattmeter reading W_1

$$W_1 = \left| \text{current through } c.c. \right| \times \left| \text{voltage across } p.c. \right| \times \cos(\text{angle b/w } I_{cc} \text{ & } V_{pc})$$

$$\begin{aligned} W_1 &= |I_A| |V_{AB}| \cos(30 + \theta) \\ &= I_L V_L \cos(30 + \theta) \\ \therefore W_1 &= I_L V_L \cos(30 + \theta) \quad \text{--- (1)} \end{aligned}$$

Wattmeter reading W_2

$$\begin{aligned} W_2 &= |I_C| |V_{CB}| \cos(\text{angle b/w } I_C \text{ & } V_{CB}) \\ &= V_L I_L \cos(30 - \theta) \quad \text{--- (2)} \end{aligned}$$

$$\begin{aligned} W_1 + W_2 &= V_L I_L \cos(30 + \theta) + V_L I_L \cos(30 - \theta) \\ &= \sqrt{3} V_L I_L \cos \theta = P_3 - \phi \end{aligned}$$

hence Proved

$$W_2 - W_1 = V_L I_L \sin \theta$$

$$\therefore \frac{W_2 - W_1}{W_2 + W_1} = \frac{V_L I_L \sin \theta}{\sqrt{3} V_L I_L \cos \theta}$$

$$\therefore \tan \theta = \frac{\sqrt{3} (W_2 - W_1)}{W_2 + W_1}$$

$$\theta = \tan^{-1} \left[\frac{\sqrt{3}(w_2 - w_1)}{w_2 + w_1} \right]$$


$$\therefore P.F = \cos \theta = \cos \left[\tan^{-1} \left[\frac{\sqrt{3}(w_2 - w_1)}{w_2 + w_1} \right] \right]$$

28th April, 2023 RC

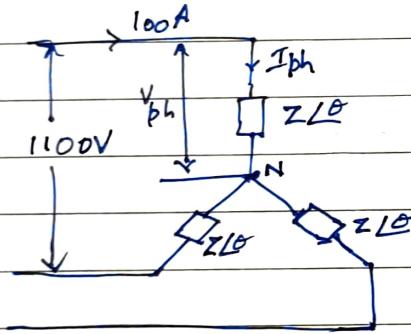q.1. Balanced star connected load of 150 kW takes a leading current of 100 A with a line voltage of 1100 V, 50 Hz. Find circuit constants of the load per phase.

R, L, C

Sol. * In 3-φ by default parameters mentioned is line (line current).



$$P_{3-\phi} = 150 \times 10^3 \text{ W}$$

$$150 \times 10^3 = \sqrt{3}(1100)(100) \cos \theta$$

$$\theta = 38^\circ$$

$$I_{ph} = 100 / 38^\circ$$

$$Z = \frac{V_{ph}}{I_{ph}} = \cancel{\text{---}}$$

$$V_L = 1100 \text{ V} / 10^\circ \quad (\text{we can either assume } V_L \text{ at } 10^\circ / V_{ph} \text{ at } 0^\circ)$$

$$V_{ph} = \frac{1100}{\sqrt{3}} = 635 \cancel{X}^{30^\circ}$$

Date _____
Page _____

here we assumed
 $V_{ph} 12^\circ$


$$Z = \frac{V_{ph}}{I_{ph}} = \frac{635 \angle 0^\circ}{100 \angle 35^\circ} = 6.35 \angle -35^\circ \Omega$$

$$Z = R + jX_C$$

$$X_C = \frac{1}{2\pi f C} \Rightarrow C = 81.9 \mu F$$

Q.2. A balanced star connected load $(8+j6)$ ohm is connected to a balanced 3-phase 400 V supply. Find line current, power factor, power and total volt-amperes.

Sol.

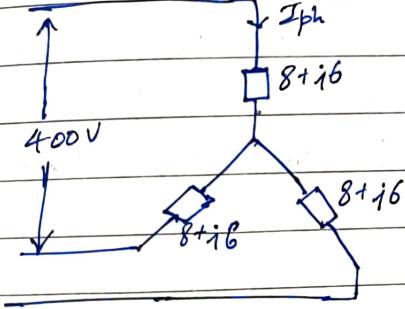

$$8+j6 = 10 \angle 36.86^\circ$$



$$\text{Let } V_{ph} = \frac{400}{\sqrt{3}} \angle 0^\circ = 230.9 \angle 0^\circ$$

$$\therefore I_{ph} = \frac{V_{ph}}{Z}$$

$$I_{ph} = \frac{230.9 \angle 0^\circ}{10 \angle 36.86^\circ} = 23.09 \angle -36.86^\circ$$

$$Y \text{ connection } I_L = 23.09 \text{ A}$$
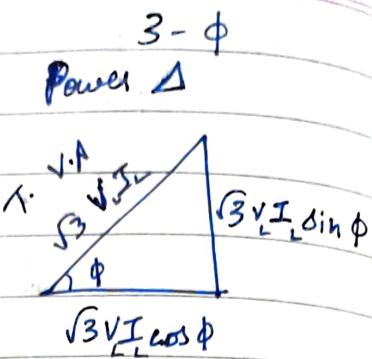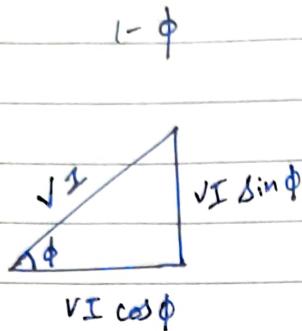
$$P.F = \cos(36.86) \approx 0.8 \text{ lag}$$




$$P_{3-\phi} = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} (400) (23.09) (0.8) = 12.79 \text{ kW}$$

$$T \cdot V \cdot A = \sqrt{3} V_L I_L = \sqrt{3} (400) (23.09) = 16.21 \text{ kVA}$$

q.3. Three equal star connected inductors take 8 kW at a power factor 0.8 when connected across a 460 V, 3- ϕ , 3-wire supply. Find circuit constants of load per phase.

Sol

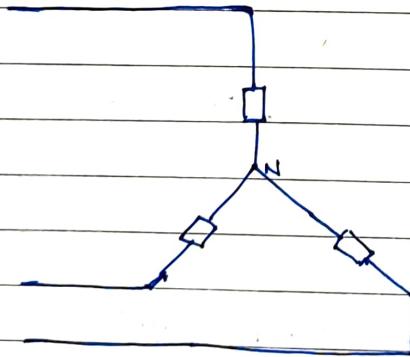

Sol. $P = \sqrt{3} V_L I_L \cos \phi$

$$8000 = \sqrt{3} \times 460 \times I_L \times 0.8$$

$$I_L = 12.55 \text{ A}$$

$$I_{ph} = 12.55 \text{ A}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{460}{\sqrt{3}} = 265 V$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{265}{12.55} = 21.1 \Omega$$

$$R_{ph} = Z_{ph} \cos \phi = 21.1 \times 0.8 = 16.9 \Omega$$

$$X_{ph} = Z_{ph} \sin \phi = 21.1 \times 0.6 = 12.66 \Omega$$

$$L = 40.39 \text{ mH}$$

Q4 A balanced delta connected load of $(8+6j)$ Ω /phase is connected to a balanced 3- ϕ 230V phase supply.

Find line current, power factor, power and reading volt-amperes, total volt-amperes.

Sol: Δ connection $V_L = V_{ph}$ ans: $I_L = 39.83 A$ ✓
 $I_L = \sqrt{3} I_{ph}$ $b-f = 0.8 \text{ lag}$ ✓

$$Z = 8 + 6j = 10 \angle 36.86^\circ$$

$$P \cdot V \cdot A = 9.521 \text{ kVAR}$$

$$V_L = V_{ph} = 230 V$$

$$T \cdot V \cdot A = 15.86 \text{ kVA}$$

$$I_{ph} = \frac{V_{ph}}{Z} = 23 \angle -36.86^\circ$$

$$I_L = \sqrt{3} I_{ph} = \sqrt{3} (23) = 39.83 A$$

$$P_f = \cos(36.86) = 0.80 (\text{lag})$$

$$P = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} (230) (39.83) (0.80) = 12.69 \text{ kW}$$

$$T \cdot VA = \sqrt{3} V_L I_L = 15.86 \text{ kV.A}$$

$$R \cdot VA = \sqrt{3} V_L I_L \sin \phi = 9.518 \text{ kVAR}$$

2nd May, 2023

- q5. Two wattmeters are connected to measure power in 3-φ balanced circuit. What would be its rating of each wattmeter. If
- i) $\theta = 60^\circ$ ii) $\theta = 30^\circ$ iii) $\theta = 0^\circ$ iv) $\theta = 90^\circ$

Sol. i) $\theta = 60^\circ$

$$W_1 = V_L I_L \cos(30 + \theta)$$
$$= V_L I_L \cos(90)$$

$$W_1 = 0$$

$$W_2 = V_L I_L \cos(30 - \theta)$$
$$= V_L I_L \cos(-30)$$
$$= \frac{\sqrt{3}}{2} V_L I_L$$

W_1 reads 0 & W_2 reads +ve values

ii) $\theta = 30^\circ$

$$W_1 = V_L I_L \cos(30 + \theta)$$
$$= \frac{\sqrt{3}}{2} V_L I_L$$

$$W_2 = V_L I_L \cos(30 - \theta)$$
$$= V_L I_L$$

W_1 reads $1/2 W_2$

iii) $\theta = 0^\circ$

$$W_1 = V_L I_L \cos(30 + \theta)$$
$$= \frac{\sqrt{3}}{2} V_L I_L$$

$$W_2 = V_L I_L \cos(30 - \theta)$$
$$= \frac{\sqrt{3}}{2} V_L I_L$$

Both read equal

iv) $\theta = 90^\circ$

$$W_1 = V_L I_L \cos(30 + 90)$$
$$= -\frac{1}{2} V_L I_L$$

$$W_2 = V_L I_L \cos(30 - 90)$$
$$= \frac{1}{2} V_L I_L$$

W_1 & W_2 read equal

W_1 is -ve

either current / pressure coil is connected in reverse. Pointer goes below 0, kickback action

q6. Each of two wattmeters are connected to measure the input to a 3- ϕ circuit draws 10kW on a balanced load, when the $P.F$ is unity what does each instrument read when the $P.F$ falls to 0.866 (lag), the total 3- ϕ power remaining unchanged.


Sol. $W_1 = 10\text{ kW}$ $\cos \phi = 1$

$$W_2 = 10\text{ kW}$$

$$W_1 + W_2 = 20$$

$$W_1 + W_2 = 20$$

$$\cos \phi = 1$$

 

$$\cos \phi = 0.866$$

$$\theta = 30^\circ$$

$$\tan 30 = \frac{\sqrt{3}(W_2 - W_1)}{20 \times 10^3}$$

$$W_2 - W_1 = 6666.67$$

$$2W_1 = 26666.67$$

$$W_1 = 13333.33 \quad W_2 = 6666.67$$

q7. In a 3- ϕ delta connection wattmeter 100kW taking a lagging current of 200A at a line voltage of 400V, 50Hz. Find circuit parameters of each phase. What could be the power consumed if the load was star connected.

Sol. $I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{200}{\sqrt{3}} = 115.47 \quad V_L = V_{ph} = 400V$

$$100 \times 10^3 = \sqrt{3} V_L I_L \cos \phi$$

$$10^5 = \sqrt{3} (400) (200) \cos \phi$$

$$\phi = 43.80$$

$$\text{Let } V_{ph} = 400 \angle 0^\circ$$

$$I_{ph} = 115.4 \angle -43.8^\circ$$

$$Z = \frac{V_{ph}}{I_{ph}} = \frac{400 \angle 0^\circ}{115.4 \angle -43.8^\circ} = 3.46 \angle 43.8^\circ$$

$$Z = \underbrace{2.5}_{R} + j \underbrace{2.4}_{X_L}$$

$$L = 7.63 \text{ mH}$$

ii) V_L & Z remain same
(source)

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94$$

$$I_L = I_{ph} = \frac{V_{ph}}{Z} = \frac{230.94}{3.46 \angle 43.8^\circ} = 66.75 \text{ A}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} (400) (66.75) \cos (43.8^\circ)$$

$$= 33.37 \text{ kW}$$

3rd May, 2023

- q8. A 5HP, 400V, 3-φ, induction motor is working at full load with an efficiency of 90% at a power factor of 0.866. Determine the power input and line current.

Sol.



$$\text{O/P of I.M} = 5 \text{ H.P}$$

$$\eta = \frac{\text{O/P Power}}{\text{I/P Power}}$$

$$0.9 = \frac{5 \times 746}{\text{I/P power}}$$

$$\text{I/P Power} = 4.14 \text{ kW}$$

$$P_{3-\phi} = \sqrt{3} V_L I_L \cos \phi$$

$$4144 = \sqrt{3} (400) I_L (0.866)$$

$$I_L = 6.9 \text{ A}$$

Q9. Two wattmeters are connected to measure input of a 15 HP, 50Hz, 3-φ I.M at full load. The full load η and pf are 0.9 and 0.8 (lag) respectively. Find the readings of two wattmeters

$$0.9 = \frac{15 \times 746}{\text{I/P power}}$$

$$\text{I/P power} = 12.433 \text{ kW} = W_1 + W_2$$

$$\tan 36.86 = \frac{\sqrt{3} (W_2 - W_1)}{W_1 + W_2} \quad \phi = 36.86^\circ$$

$$W_2 - W_1 = 5.381$$

$$2W_2 = 17.814$$

$$W_2 = 8.9 \text{ kW}$$

$$W_1 = 3.526 \text{ kW}$$

q.10. Two wattmeters readings were 3400W & -1200W
 calculate Total Power and Power factor of circuit

Sol. Total Power = $W_1 + W_2$
 $= 2200\text{W}$

$$P_f = \cos \left(\tan^{-1} \left(\frac{\sqrt{3}(W_2 - W_1)}{W_1 + W_2} \right) \right)$$

$$P_f = 0.266$$

q.11. Two wattmeters are connected to measure power in a 3- ϕ circuit read 5kW , 1kW
 the second reading is obtained after reversing the current coil, calculate power factor, power consumed in circuit

Sol. $W_1 = 5\text{kW}$ $W_2 = -1\text{kW}$

$$\text{Power consumed} = W_1 + W_2
= 4\text{kW}$$

$$P_f = 0.359$$

q.12. Three coils each of impedance $20\angle 60^\circ$ are star connected to a $400\text{V}, 50\text{Hz}$ 3- ϕ supply. Find the reading of each of two wattmeters connected to measure the input.

Sol.

$$Z = 20\angle 60^\circ \quad V_L = 400\text{V} \quad V_{ph} = \frac{400}{\sqrt{3}} = 230.94\text{V}$$

$$I_{ph} = \frac{V_{ph}}{Z} = \frac{230.94}{20} = 11.547\text{A} = I_L$$

$$\begin{aligned}W_1 &= V_L I_L \cos(30 + \theta) \\&= 400 (11.547) \cos(30 + 60) \\&= 0 \text{ W}\end{aligned}$$

$$\begin{aligned}W_2 &= V_L I_L \cos(30 - \theta) \\&= 400 (11.547) \cos(30 - 60) \\&= 3999.99 \text{ W}\end{aligned}$$

Advantages of AC