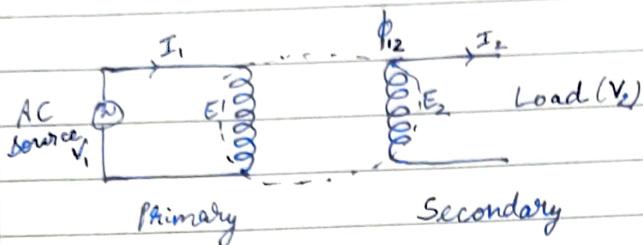


1st June, 2023

UNIT-5

Transformer



LV - Low Voltage

HV - High Voltage

1-Φ Transformer


- Step Up
 - Step down
 - Isolation
- Peri Sec

Step up $\rightarrow 220\text{V} / 440\text{V}$ - without change in freq.
 bri \rightarrow LV sec \rightarrow HV


Step Down \rightarrow 440 / 220
 peri sec



Isolation transformer (1:1) $\rightarrow 220 / 220$

Construction: Core Type:

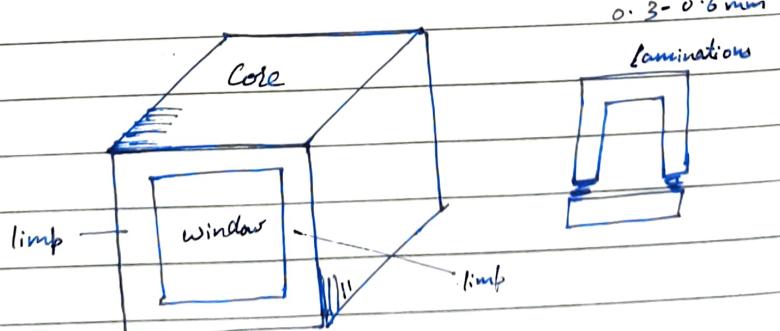

Shell Type

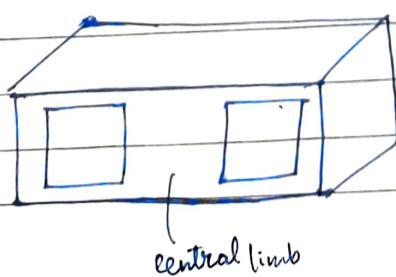

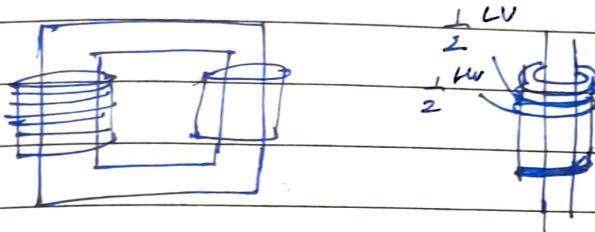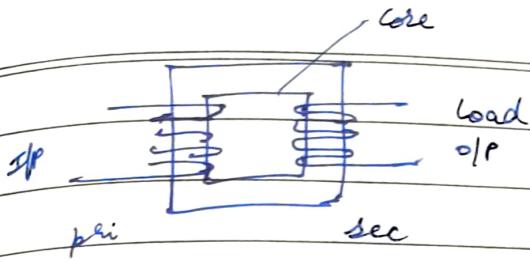

Parts of Transformer

Core

Winding

Transformer Tank

Transformer oil


Bush rings

Relay conservator

→ Core Type Transformer

→ EMF equation

DERIVATION:

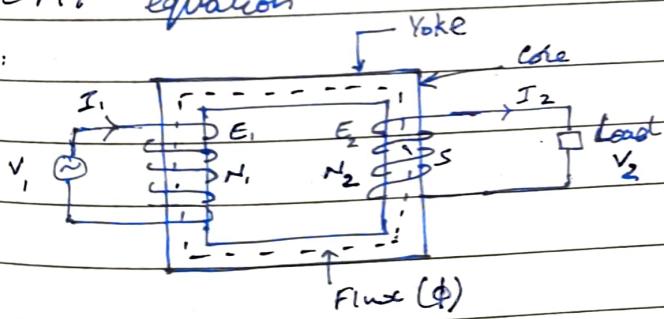

Let V_1 be the input voltage


E_1 be the emf induced in primary

N_1 be the no. of turns in primary

N_2 be the no. of turns in secondary

E_2 be the emf induced in secondary

ϕ be the flux in the core.

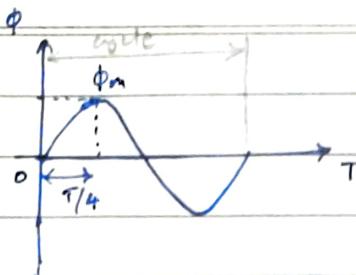

Let $\phi_m \rightarrow$ final flux

initial flux $\rightarrow 0$

Time taken is $T/4$

\therefore EMF induced in 1 turn = $\frac{\text{final flux} - \text{initial flux}}{\text{time taken}}$

$$= \frac{\phi_m - 0}{T/4}$$

$$= \frac{4\phi_m}{T}$$

$$= 4\phi_m f$$

EMF induced in primary $E_1 = 4\phi_m f N_1$

wkt $E_{\text{rms}} = 1.11 E_{\text{avg.}}$

$$\therefore [E_1 = 4.44 \phi_m f N_1] - \textcircled{1}$$

$$\text{By } [E_2 = 4.44 \phi_m f N_2] - \textcircled{2}$$

Ideal transformer ,

$$kVA_o/P = kVA I/P$$


$$V_2 I_2 = V_1 I_1$$

$$E_1 = V_1 \quad \& \quad E_2 = V_2$$

$$K = \frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{V_2}{V_1} = \frac{I_1}{I_2}$$

Transformer ratio

→ Losses in Transformer

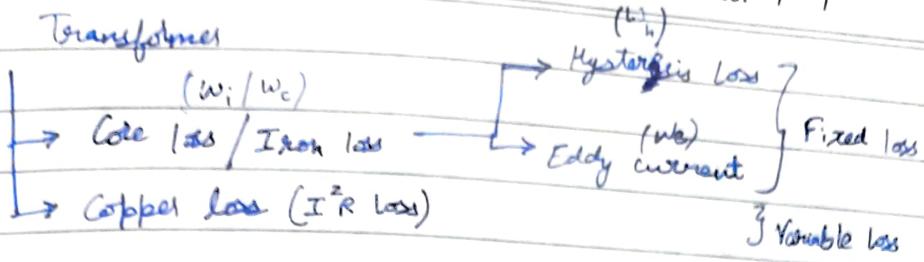

q1: A single phase transformer has 400 primary turns and 1000 secondary turns. The net cross section area of the core is 60 sq.cm . If primary winding to be connected to a 50Hz supply at 500V. Calculate peak value of flux density in the core and voltage induced in the secondary windings.

$$\text{Sol. } N_1 = 400, N_2 = 1000 \quad f = 50 \text{ Hz}$$

$$A = 60 \times 10^{-4} \text{ m}^2 \quad V_1 = 500 \text{ V}$$

$$B_m = \frac{\phi_m}{A}$$

flux density

$$E_1 = 4.44 \phi_m f N_1$$

$$E_1 = 4.44 B_m (A) f N_1$$

$$500 = 4.44 B_m (60 \times 10^{-4}) \times 50 \times 400$$

$$B_m = 0.94 \text{ Wb/m}^2$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} \Rightarrow E_2 = \frac{1000 \times 500}{400} = 1250 \text{ V}$$

q2: The required no load ratio in a single phase 50Hz core type transformer is $6000/250 \text{ V}$. Find the no. of turns in each winding if the flux is to be about 0.06 Wb

$$\text{Sol. } E_1 = V_1 = 6000 \text{ V} \quad f = 50 \text{ Hz}$$

$$E_2 = V_2 = 250 \text{ V} \quad \phi = 0.06 \text{ Wb}$$

$$N_1 =$$

$$E_1 = 4.44 \Phi_m f N_1$$

$$6000 = 4.44 (0.06) 50 N_1$$

$$N_1 = 450 \text{ turns}$$

$$250 = 4.44 (0.06) 50 N_2$$

$$N_2 = 19 \text{ turns}$$

Q3. A 5kVA, 50Hz single phase transformer has primary and secondary turns 120 and 80. At certain flux density the induced emf per turn in primary is 2.5V. Determine primary and secondary voltage. Also calculate current in both the windings.

Sol. $N_1 = 120$ $E_1 = 2.5 \times 120 = 300 \text{ V}$

$$N_2 = 80$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} \Rightarrow E_2 = \frac{80}{120} \times 300 = 200 \text{ V}$$

$$O/P = 5 \times 10^3 \text{ VA} = V_2 I_2$$

$$V_2 I_2 = 5000$$

$$I_2 = \frac{5000}{200} = 25 \text{ A}$$

$$\frac{E_2}{E_1} = \frac{I_1}{I_2}$$

$$I_1 = \frac{200 \times 25}{300}$$

$$= 16.66 \text{ A}$$

2nd June, 2023

- Q4. A 125 kVA transformer has a primary voltage of 2000V at 50Hz. If the no. of turns on primary equals 182 and the secondary equals 40
 Find : a) secondary no load voltage
 b) flux in the core
 c) full load primary and secondary currents. Neglect losses

[4M]

$$V_2 I_2 = 125 \times 10^3 \text{ VA}$$

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$E_2 = V_2 \quad V_2 = V_1 \times \frac{N_2}{N_1} = 2000 \times \frac{40}{182} = 439.56 \text{ V}$$

$$V_1 = 4.44 \Phi_m f N_1$$

$$2000 = 4.44 \Phi_m (50) (182)$$

$$\Phi_m = 0.0495 \text{ Wb}$$

$$125 \times 10^3 = V_2 I_2$$

$$I_2 = \frac{125 \times 10^3}{439.56} = 284.4 \text{ A}$$

$$\frac{I_2}{I_1} = \frac{V_1}{V_2}$$

$$I_1 = I_2 \frac{V_2}{V_1} = 284.4 \times \frac{439.56}{2000}$$

$$I_1 = 62.5 \text{ A}$$

- Q5. Find no. of turns of primary and secondary of a 415/240 V, 50Hz transformer if area of the core is 50 sq.cm and max. value of flux density in the core is 1.3 Wb/sq.m

Sol.

$$N_1 = ? \quad N_2 = ?$$

$$\begin{matrix} 415 & / & 240 \\ \downarrow & & \downarrow \\ V_1 & & V_2 \end{matrix}$$

$$V_1 = 4.44 \Phi_m f N_1$$

$$415 = 4.44 \times 1.3 \times 50 \times 10^{-4} \times N_1$$

$$N_1 = 288 \text{ turns}$$

$$N_2 = N_1 \times \frac{V_2}{V_1} = \frac{288 \times 240}{415} = 167 \text{ turns}$$

- 9.6. The primary winding of a single phase transformer is connected to 240V, 50Hz. The secondary winding has 1500 turns. If the maximum value of the core flux is 0.002 wb. Determine : a) no. of turns on primary windings
 b) secondary induced voltage
 c) net cross sectional core area if the max. flux density is 0.465 T. [4M]

$$\text{Sol. } 240 = 200 \quad | N_1 = 541 \text{ turns}$$

$$V_1 = 4.44 \Phi_m f N_1$$

$$240 = 4.44 (0.002) (50) N_1$$

$$N_1 = 541$$

$$| V_2 = 666 \text{ V}$$

$$| A = 4.8 \times 10^{-3} \text{ m}^2$$

$$\frac{N_2}{N_1} = \frac{V_2}{V_1} \Rightarrow V_2 = \frac{1500}{541} \times 240 = 666 \text{ V}$$

~~$$240 = 4.44 \Phi_m = B_m A$$~~

$$A = \frac{\Phi_m}{B_m} = 0.0043 \text{ m}^2$$

- 9.7. A 3000/300 V, 50Hz single phase transformer has an emf per turn of 15V and the maximum flux density of 1.5 T. Find no. primary and secondary turns and cross sectional area of the core.

$$\text{Sol. } V_1 = 3000$$

$$V_2 = 300$$

$$3000 = 4.44 (1.5) (50) N_1$$

$$3000 = N_1 (V)$$

$$\frac{3000}{15} = N_1$$

$$N_1 = 200$$

$$N_2 = N_1 \times \frac{V_2}{V_1} = 20$$

Paperism,
Date: / /

$$V_1 = 4.44 (B_m A) f N_1$$

$$A = 0.045 \text{ m}^2$$

Ques. 1 (100 kVA), 6000/400V, 50Hz, 1-phi transformer has 100 turns in secondary. Calculate the stated primary and secondary currents, the no. of primary turns and max. value of flux in core.

$$V_1 = 6000$$

$$V_2 = 400$$

$$P = V \times I$$

$$100 \times 10^3 = 6000 \times I_1$$

$$I_1 = 16.67 \text{ A}$$

$$100 \times 10^3 = 400 \times I_2$$

$$I_2 = 250 \text{ A}$$

$$N_1 = N_2 \times \frac{V_1}{V_2} = 1500$$

$$V_1 = 4.44 \Phi_m f N_1$$

$$\Phi_m = \frac{6000}{4.44 \times 50 \times 1500} = 0.018 \text{ Wb}$$

9. June, 2023

Energy Calculation

$$1 \text{ kWh} = 1 \text{ unit}$$

q1: Find the total no. of units consumed in a month for the following consumption tables assuming 30 days a month with a sanction load of 5kW

Name	Wattage	avg consumption hours per day	units consumed per day
1. Geyser	2000 W	1 hour	$2000 \times 1 = 2000 \text{ Whs}$ $= 2 \text{ kWh} = 2 \text{ units}$
2. T.V	50 W	6 hours	$50 \times 6 = 300 \text{ Whs} = 0.3 \text{ units}$
3. 4 LED bulb	20W each bulb	6 hours each bulb	$4 \times 20 \times 6 = 480 \text{ Whs}$ $= 0.48 \text{ units}$
4. 3 Fan	75W each fan	8 hours each bulb	$3 \times 75 \times 8 = 1800 \text{ Whs}$ $= 1.8 \text{ units}$
5. Fridge	100W	24 hours	2.4 units
6. Water pump	1500W	20 mins	0.5 units

Total units consumed per day = 7.48 units

Total units consumed per month = 224.4 units

Units	Rs
0 - 50	4.15
51 - 100	5.6
101 - 200	7.15
200 >	8.2

0 - 50 4.15

51 - 100 5.6

101 - 200 7.15

200 > 8.2

FAC \rightarrow NIL

Tax \rightarrow 9%

Type of charges

Charges

1. Fixed charges for sanctioned load per month

$$100 \times 1 + 110 \times 4 = \text{Rs } 540$$

2. Energy consumption charges

$$50 \times 4.15 + 50 \times 5.56 + 100 \times 7.15 \\ + 24 \times 8.2 = \text{Rs } 1399.3$$

3. Fuel adjustment charges

NIL

4. Tax

Rs 125.937

$$\frac{399.3 \times 3}{100}$$

$$\text{Monthly Bill} = \text{Rs } 2065.237$$

6th June, 2023

Q2 A list of loads and avg. consumption per day is given below. Considering 30 days a month determine:

- Total no. of units consumed in a month
- Monthly Bill for above consumption considering domestic connection of 3 kW sanctioned load with the tariff details listed in table 2

Table 1

	Appliance	Wattage	avg. consumption per day	units (kWh)
1.	4 bulbs	60 W/bulb	10 hr each	2.4
2.	4 fans	75 W/bulb	12 hr each	3.6
3.	Geysers	1 kW	1 hr	1
4.	Fridge	100 W	16 hr	1.6
5.	T.V	50 W	10 hr	0.5
6.	Mixer	750 W	1 hr	0.75
				9.85

Consider Tax 7.3%.

Table 2: Type of charge

Tariff

Q.

1. Fixed charge for same load Rs. 50 for 1st kW
 Rs. 60 for every additional

2. Energy consumption

units

Rs

0 - 30 3.50

4.95

31 - 100 6.5

101 - 200 7.55

201 - 300 7.6

301 - 400 7.65

401 & above 7.65

$$\text{Sol: units consumed /day} = 9.85 \text{ units}$$

$$\text{units consumed in a month} = 295.5 \text{ units}$$

$$F.C. = 1(50) + 2(60) = 170 \text{ Rs}$$

$$E.C. = 30(3.5) + 70(4.95) + 100(6.5) + 95.5(7.55) \\ = 1822.55 \text{ Rs}$$

$$\text{Tax} = 1822.55 \times \frac{1}{100} = 133.04$$

$$\text{Total Bill} = 170 + 1822.55 + 133.04 \\ = \text{Rs} 2125.59$$

Q3) Following table gives typical consumption for household

1.	4 LED bulbs	20W/bulb	8hrs each	5.64
2.	TV	60W	6hrs	0.36
3.	AC	2000W	2hrs	4
4.	Fridge	100W	24hrs	2.4
5.	Water pump	750W	30min	0.375
6.	3 Fans	75W/Fan	10hrs each	2.25
				10.525

Considering 30 days a month Find :

- i) Total no. of units consumed in a month 300.75
- ii) Monthly Bill considering 5kW base load

T2.

1.	FC	Rs 70 for first kWh Rs 80 for next kWh
2.	EC	0 - 30 units Rs 4 31 - 100 5.45 101 - 200 7 201 & above 8.05
3.	FAC	8 paise/unit
4.	Tax only on EC	9%

Sol.

$$FC = 1(70) + 4(80) = 390$$

$$EC = 30(4) + 70(5.45) + 100(7) + 100 \frac{8.05}{75} = 2012.54$$

$$FAC = 24.06$$

$$\text{Tax} = 181.1286$$

$$\text{Monthly Bill} = \text{Rs } 2607.7286$$

7th June, 2023

94

1. AC	2000W	1 hr	2
2. TV	50 W	8 hrs	0.4
3. 3 LEDs	20W each	6 hrs each	0.36
4. 3 Fans	75W each	8 hrs each	1.2
5. Fridge	100W	24 hrs	2.4
6. Water pump	750W	30 mins	0.375
			6.735

Considering 30 days a month

- Total no. of units consumed in a month
- Monthly Bill for the above consumption considering a domestic connection of 5kW sanc. load with tariff details as given below

1. Fixed charge for sanc. load Rs 8.5 for first kW
 Rs 9.5 for every additional kW

2. Energy consumption charges 0 - 50 Rs 4.1 per unit
 51 - 100 Rs 5.55 per unit
 101 - 200 Rs 7.1 per unit
 above 200 Rs 8.15 per unit

3. Fuel adjustment charges 14 paise per unit energy consumed

Consider overall tax 9% on energy consumption charges

Sol. no. of units /day = 6.735 units

Total no. of units consumed in a month = 202.05 = 202 units

sanc. load = 5kW

$$FC = 1(8.5) + 4(9.5) = 46.5$$

$$E.C = 50(4.1) + 50(5.55) + 100(7.1) + 2(8.15)$$

$$= \text{Rs } 1209.20$$

$$F.A.C = 202 \times 0.14$$

$$= \text{Rs } 28.28$$

$$\text{Tax} = 1209.2 \times \frac{9}{100} = 108.8$$

$$\text{Total Bill} = 46.5 + 1209.2 + 28.28 + 108.8$$

$$= \text{Rs } 1811.28$$

q5

1. 3 LEPS	15W per bulb	10 hours each	0.25
2. 2 Fans	75W per fan	8 hours each	1.2
3. water pump	750W	1 hour	0.75
4. Fridge	100W	24 hours	2.4
5. T.V	50W	60 hours	0.5
6. Geysers	1 kWh	1 hour	1
			6.3

Considering 30 days a month

- i) Total no. of units consumed in a month 189 units
ii) Monthly Bill, 3kW base load

1. Fixed charge for base load Rs 50 for first kW
 $F.C = 1(50) + 2(60) = 170$ Rs 60 for every additional kW

2. Energy consumption charges	0 - 30	Rs 3.50 per unit
$E.C = 30(3.5) + 70(4.95) + 89(6.5)$	31 - 100	4.55
= 1030	101 - 200	6.50
	201 - 300	7.55

3% on total charge
 $= (170 + 1030)(0.03) = 96$



ans: 1296

$$\text{Total bill} = 170 + 1030 + 96 = 1296$$

8th June, 2023

Power Factor Improvement

Power Δ

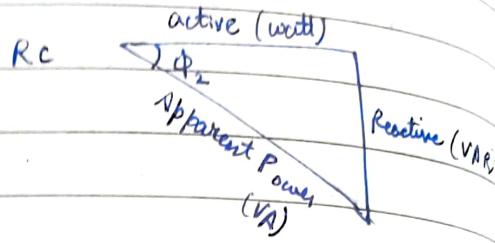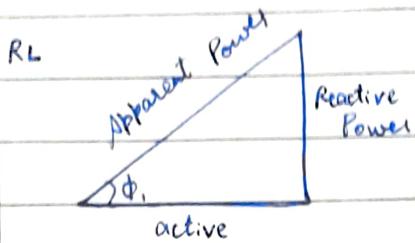


- * Add a capacitor in parallel to improve power factor when ϕ goes near 0, pf improves

- q. The power consumed in the inductive load is 5kW at 0.6 lagging power factor. The input voltage is 230V, 50Hz. Find the value of the capacitor C that must be placed in parallel, such that the resultant p.f of input current improves to 0.9 lagging. [4M]

$$\text{Sol. } P = 5 \text{ kW}$$

$$\text{Case 1: } \text{pf} = 0.6$$

$$\cos^{-1}(0.6) = 53.33^\circ$$

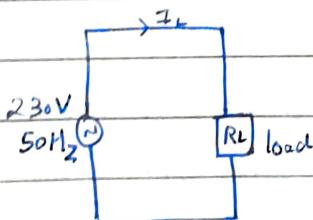


$$5 \times 10^3 = 230 I_L (0.6)$$

$$I_L = 36.23 \angle -53.33^\circ \text{ A}$$

$$\text{Case 2: } \text{pf} = 0.9$$

$$\cos^{-1}(0.9) = 25.6^\circ$$

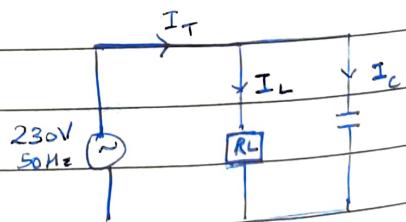

$$5 \times 10^3 = 230 I_T (0.9)$$

$$I_T = 24.15 \angle -25.8^\circ \text{ A}$$

$$\vec{I}_T = \vec{I}_L + \vec{I}_C$$

$$4 \cdot 65 \times 10^{-3} + 18 \cdot 473i = i I_c$$

Date: / /

$$24 \cdot 15 \cancel{+ 25 \cdot 8} = 36 \cdot 23 \cancel{- 53 \cdot 13} + I_c \cancel{+ 190}$$

$$I_c = 18.47 \cancel{+ 190}, V = 230V$$

$$X_C = 12.44 \Omega$$

$$C = 255.87 \mu F$$

$$4 \cdot 65 \times 10^{-3} + 18 \cdot 473i = I_c$$

paperism.

Date: / /

$$24 \cdot 15 / -25 \cdot 8 = 36 \cdot 23 / -53 \cdot 13 + I_c / 90$$

$$I_c = 18 \cdot 47 / 90, V = 230V$$

$$X_C = 12 \cdot 44 \Omega$$

$$C = 255 \cdot 87 \mu F$$


9th June, 2023

q2. The power consumed in inductive load is 5kW at 0.6 lagging p.f. The input voltage is 230V, 50Hz (single phase). Find the value of capacitor C which must be placed in parallel such that resultant p.f of input current will be 0.95 lagging.

Sol. $P = 5 \text{ kW}$

Case 1: $\text{p.f.} = \cos \phi_1 = 0.6 \text{ lag} \Rightarrow \phi_1 = 53 \cdot 13^\circ$

$$V = 230V, 50\text{Hz}$$

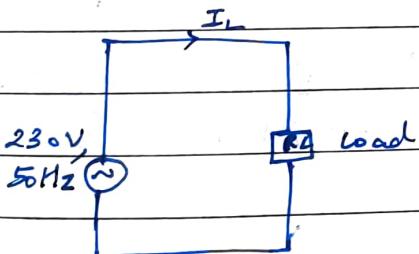


$$5 \times 10^3 = 230 I_L (0.6)$$

$$I_L = 36 \cdot 23 / -53 \cdot 13 A$$

Case 2: $\text{p.f.} = 0.95$

$$\cos^{-1}(0.95) = 18 \cdot 19^\circ$$

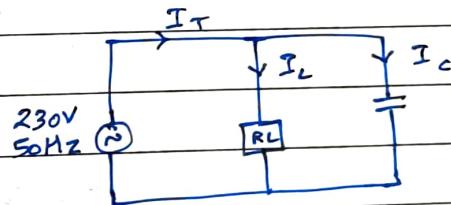

$$5 \times 10^3 = 230 I_T (0.95)$$

$$I_T = 22 \cdot 88 / -18 \cdot 19$$

$$\vec{I}_T = \vec{I}_L + \vec{I}_C$$

$$22 \cdot 88 / -18 \cdot 19 = 36 \cdot 23 / -53 \cdot 13 + I_C$$

$$21 \cdot 74 + i(-7 \cdot 14) = 20 \cdot 71 + i(-29 \cdot 72) + I_C$$

q3: The load connected across a single phase AC supply consists of a heating load of 1.5 kW, a motor load of 2 kVA at a power factor 0.6 lag and a load of 2 kW at a power factor 0.8. Calculate the total power drawn from the supply in kW & kVA and overall power fact of the system.

What must be the kVAR rating of a capacitor to bring the power factor of above system to unity.

Sol.

 L_1

$$P_1 = 1.5 \text{ kW}$$



$$\text{kVAR}_1 = 0$$

 L_2

$$2 \text{ kVA}, 0.6 \text{ lag}$$

 L_3

$$P_3 = 2 \text{ kW}, 0.8 \text{ lag}$$

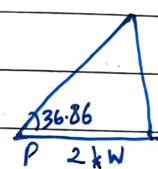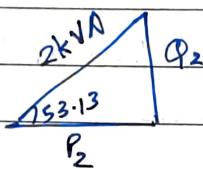

$$P_2 = 2 \cos(53.13) = 1.2 \text{ kW}$$


$$Q_2 = 2 \sin(53.13) = 1.6 \text{ kVAR}$$

$$S_2 = 2.5 \text{ kVA}$$

$$Q_3 = 1.5 \text{ kVAR}$$


$$\text{Total Real Power} = 1.5 + 1.2 + 2 = 4.7 \text{ kW} \quad (P)$$
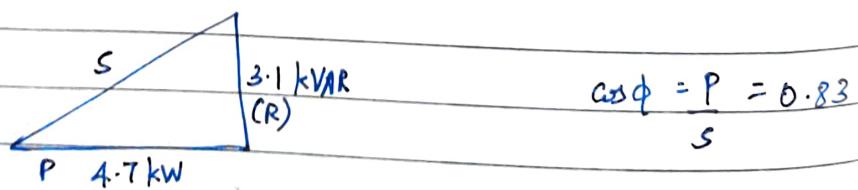
$$\text{Total Reactive Power} = 0 + 1.6 + 1.5 = 3.1 \text{ kVAR}$$



$$\text{Total Apparent Power} = \sqrt{4.7^2 + 3.1^2} = 5.63 \text{ kVA} \quad (S)$$

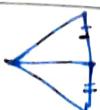3.1 kVA capacitor rating needs to be added in parallel to make p.f 1



Q4. Three loads are connected across a single phase AC supply with particulars as:

Load 1: Heating load of 5kW

Load 2: Inductive load of 5kVA at 0.8 lagging p.f

Load 3: Inductive load of 3kW at 0.6 lagging p.f

Determine:

- i) Total active Power and Reactive Power
- ii) Total apparent Power
- iii) Overall p.f

What must be kVAR rating of capacitor to be connected in || to make p.f unity.

Sol.

 L_1

$$P_1 = 5 \text{ kW}$$

 L_2

$$S_2 = 5 \text{ kVA}$$

 L_3

$$P_3 = 3 \text{ kW}$$

$$\text{p.f} = 0.8 \Rightarrow \phi = 36.86^\circ$$

$$P_2 = 4 \text{ kW}, Q_2 = 3 \text{ kVAR}$$

$$\text{p.f} = 0.6 \Rightarrow \phi = 53.13^\circ$$

$$P = S(\cos\phi)$$

$$S_3 = 5 \text{ kVA}$$

$$Q_3 = 4 \text{ kVAR}$$

$$\text{Total active power} = 5 + 4 + 3 = 12 \text{ kW}$$

$$\text{Total apparent power} = 7 \text{ (P)}$$

$$S = \sqrt{12^2 + 7^2} = 13.89$$

$$\phi = \cos^{-1}(P/S) = 36.23^\circ$$